
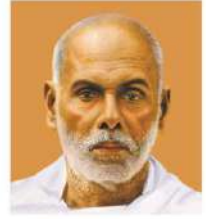


Sree Narayana Guru College of Engineering & Technology

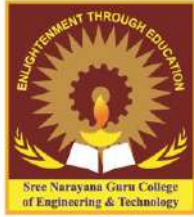CHALAKKODE P.O., KOROM, PAYYANUR, KANNUR-670 307




SAMPLES OF LAB RECORDS



Sree Narayana Guru College of Engineering & Technology

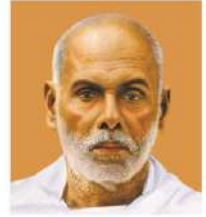CHALAKKODE P.O., KOROM, PAYYANUR, KANNUR-670 307



DEPARTMENT OF CIVIL ENGINEERING

SREE NARAYANA GURU
COLLEGE OF ENGINEERING & TECHNOLOGY
PAYYANUR – 670 307



CERTIFICATE

Name.....PRANAV A.K.....
Semester.....5..... Branch.....CIVIL.....
Roll No.....16..... Uni. Reg. No.....SN19LE014.....

Certified that this is a Bonafide Record of the work done in the ...ENVIRONMENTAL
ENGINEERING LAB..of Sree Narayana Guru College of Engineering & Technology, Payyanur by
Mr. / Miss.PRANAV A.K.....

Place : PAYYANUR

Date :

Internal Examiner

Maheep
HOD



Staff Member Incharge

External Examiner

Leena
Dr. LEENA A. V.
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY, PAYYANUR
KANNUR

INDEX

Sl. No.	NAME OF EXPERIMENT	DATE	PAGE No.	INITIAL OF TEACHER
1.	DETERMINATION OF HARDNESS	27/9/22	2	
2.	DETERMINATION OF ALKALINITY	27/9/22	5	
3.	DETERMINATION OF CHLORIDE	11/10/22	9	
4.	DETERMINATION OF ACIDITY	11/10/22	11	
5.	DETERMINATION OF pH	19/10/22	13	
6.	DETERMINATION OF TURBIDITY	19/10/22	15	
7.	DETERMINATION OF BOD	1/11/22	17	
8.	DETERMINATION OF AVAILABLE CHLORINE IN SAMPLE OF BLEACHING POWDER	1/11/22	19	
9.	DETERMINATION OF DO	1/11/22	22	
10.	BREAKPOINT CHLORINATION	1/11/22	25	
11.	DETERMINATION OF ELECTRICAL CONDUCTIVITY	1/11/22	27	
12.	DETERMINATION OF TS, TDS, TSS TVS	15/11/22	29	
13.	DETERMINATION OF CHEMICAL OXYGEN DEMAND	29/11/22	32	
14.	DETERMINATION OF OPTIMUM COAGULATION DOSAGE	29/11/22	34	
15.	DETERMINATION OF COLIFORM	6/12/22	36	

Leena

Dr. LEENA A. V.
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY, PAYANUR
KANNUR

May 14

HOD

EXPT NO: 1

27/9/22

2

DETERMINATION OF HARDNESS

AIM

To determine the hardness of given water sample

PRINCIPLE

Ethylene diamine tetra acetic (EDTA) method of determination of hardness, involves the use of solutions of EDTA or its sodium salt as the titrating agent. The complexes usually represented as EDTA or its sodium salt as the chelating agents and form extensively stable complex ions with Ca^{2+} and Mg^{++} and other divalent ions causing hardness as shown in equation

$\text{M}^{++} + \text{EDTA} \rightarrow \text{M} \cdot \text{EDTA complex}$

The dye, called Eriochrome black T (EBT) serves as excellent indicator to show when all the hardness producing ions have been complexed. When EBT is added to the aqueous solution containing small calcium & magnesium ions at a pH of 10 ± 0.1 , the solution becomes wine red, Higher the pH sharper the end point. However above pH 10, there is a danger of precipitation of calcium carbonate, and magnesium hydroxide. When a small amount of EBT having blue colour is added to hard water with a pH of about 10 it combines with a few of the Ca^{++} & Mg^{++} ions to form a weak complex ions which is wine red in colour

OBSERVATION AND CALCULATION

Vol of Sample	Burette reading		Vol of EDTA (V)	Hardness of CaCO_3 (mg/l)
	Initial	Final		
20	0	9		
20	9	11.2	2.2	110
20	11.2	13.2		

Hardness in mg/l as Calcium Carbonate

$$= \frac{V_1 \times S \times 1000}{V} = \frac{2.2 \times 1 \times 1000}{20}$$

$$= 110 \text{ mg/l}$$

V_1 = ml of titrant used

V = Vol of sample

S = mg of CaCO_3 equivalent to 1ml of EDTA.

$M^{++} + EBT \rightleftharpoons M \cdot EBT$ complex

During the titration with EDTA all free hardness ions are complexed. Finally the EDTA disrupts the red EBT because it is capable of forming a more stable complex with the hardness ions. This action frees EBT indicator and the wine red colour changes to a distinct blue colour, indicating the end of the titration. An accurate method of determining hardness is calculation based upon concentration of divalent ion.

APPARATUS

1. Burette
2. Pipette
3. Erlenmeyer flask

REAGENTS

1. 0.01 M EDTA
2. Ammonium buffer solution.
3. Eriochrome black T (EBT)
4. Litmus paper

PROCEDURE

1. A sample volume, V which requires less than 15 ml. EDTA titrant is chosen
2. One or two ml. of buffer solution is added. Care is taken to bring the pH to 10 ± 0.1
3. One or two drops of the indicator solution are added. If there is Ca or Mg hardness, solution turns to wine red.

4. EDTA titrant is added from the burette with vigorous shaking till the wine red colour just turns to blue.
5. The volume of the titrant added is noted down (V_1)
6. Procedure is repeated for concordant values.

RESULT

Hardness of given water sample = 110 mg/l

INFERENCE

As per IS-10500-1991 desirable limit of hardness is 300 mg/l in potable water. The obtained value of water sample is 110 mg/l. It indicates water is moderately hard.

28/9/22

26/30

May 24
HOD

Procedure	5
Conduction	10
Result	4
Viva	3
Record	4

EXPT NO : 2

27/9/22

5


DETERMINATION OF ALKALINITY

AIM

To determine the alkalinity in the given water sample

PRINCIPLE

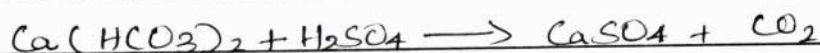Alkalinity can be obtained by neutralizing OH^- , CaCO_3^{2-} & HCO_3^{3-} with standard H_2SO_4 . Titration to pH 8.3 or decolourisation of Phenolphthalein indicators will show complete neutralization of OH^- and $\frac{1}{2} \text{CO}_3^{2-}$ while to pH 4.4 or sharp change from yellow to pink of methyl orange indicators total alkalinity.



APPARATUS

Burettes, Volumetric flasks, conical flasks, Measuring cylinder and beakers.

REAGENTS

0.05 N standard sodium carbonate solution: Dry 310.8g of sodium carbonate, Na_2CO_3 at 250°C for 4 hrs and cool in a desiccator. Accurately weigh $2.5 \pm 0.2\text{g}$ to the nearest mg, dissolve in distilled water and make to 1 L.

0.1 N standard H_2SO_4 solution: Dilute 2.8 ml conc. sulphate acid to 1 L. Standardise against 40.00 mL 0.05 N Na_2CO_3

OBSERVATION AND CALCULATION

Titration 1 (for phenolphthalein alkalinity)

Burette sol : H_2SO_4

Pipette sol : Sample

Indicator : phenolphthalein

End point : Dis appearance of pink colour

Sample No	Vol of Sample (V)	Burette reading		Vol of H_2SO_4 (V)
		Initial	Final	
1	25	0	7.5	7.5
2	25	0	7.5	

Titration 2 (For total alkalinity)

Burette sol : H_2SO_4

Pipette Sol : sample

Indicator : mixed indicator

End point : Appearance of pink colour

Sample No	Vol of Sample	Burette reading		Vol of H_2SO_4
		Initial	Final	
1	25	0	3.8	3.8
2	25	0	3.8	

Phenolphthalein alkalinity (P) as $CaCO_3$

$$P = \frac{V_1 \times N \text{ of } H_2SO_4 \times 50000}{\text{Vol of Sample}}$$

$$= \frac{7.5 \times 0.02 \times 50000}{25} = 300 \text{ mg/l}$$

$$\text{Total alkalinity} = \frac{3.8 \times 0.02 \times 50000}{25} = 154 \text{ mg/l}$$

with about 60 mL distilled water, in a beaker by titrating potentiometrically to pH 5. Lift out electrodes, rinse into the same beaker and boil gently for 3 to 5 min under a watch glass cover.

$$\text{Normally, } N = (A \times B) / (S \times C)$$

where,

A = g Na_2CO_3 weighed into the 1L flask for the Na_2CO_3

B = mL Na_2CO_3 solution taken for standardisation titration

C = mL acid used in standardised titration.

0.02 N standard sulphuric acid solution: Dilute the approximate 0.1 N solution to 1L

$$\text{Volume (mL)} = N/20$$

where N = exact normality of the approximate 0.1 N sol.

Phenolphthalein indicator solution (alcoholic, pH 8.3)

Dissolve 8g phenolphthalein in 500 mL of 95% ethyl alcohol. Add 500 mL distilled water.

Mixed indicator (methyl orange indicator) - Dissolve 20g of methyl red, 100 mg of bromo crystal green in 100 mL ethyl or isopropyl alcohol.

PROCEDURE

Phenolphthalein alkalinity

1. Take 25 to 50 mL sample in a conical flask.
2. Add 2 to 3 drops of phenolphthalein indicators. If it turns pink ($\text{pH} > 8.3$), titrate with 0.02N H_2SO_4 till the pink colour disappears. Record volume (mL) of titrant used.

Total alkalinity:

1. Add a drop of mixed indicators to the solution in which the phenolphthalein alkalinity is determined.

$$\text{phenolphthalein alkalinity (P) (as CaCO}_3\text{)} = \frac{V_1 \times N \text{ of H}_2\text{SO}_4 \times 50,000}{\text{Vol. of sample}}$$

$$\text{Total alkalinity (T) (as CaCO}_3\text{)} = \frac{V_2 \times N \text{ of H}_2\text{SO}_4 \times 50,000}{\text{Vol. of sample}}$$

2. Titrate it against 0.02N Sulphuric acid. Appearance of pink colour indicates the end point.

RESULT

Phenolphthalein alkalinity = 300 mg/l

Methyl orange alkalinity = 154 mg/l

total alkalinity = 154 mg/l

INFERENCE

As per IS 10500:1991 the desirable limit of alkalinity in portable water is 200 mg/l. However absence of any alternate source is permissible limit shall be 600 mg/l as CaCO_3 . The total alkalinity of given sample is 154 mg/l hence the sample is not portable.

recd
28/9/22

26/30

M. Jay
HOD

Procedure	5
Conduction	10
Result	4
Viva	3
Record	4

EXPT NO : 3

11/10/22

9

DETERMINATION OF CHLORIDE

AIM


To determine the chloride concentration present in given water sample.

PRINCIPLE

Chloride ion concentration in the water can be determined by titration with silver nitrate. As the silver nitrate solution is slowly added, a precipitate of silver chloride forms.



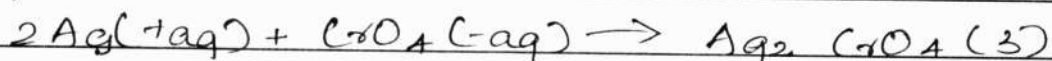The end point of the titration occurs when all the chloride ions are precipitated. Then additional silver ions react with the chromate ions of the indicator, potassium chromate to form a red-brown precipitate of silver chromate.



APPARATUS

Burette, pipette, conical flask, beaker, measuring cylinder, weighing balance, stirrer etc.

REAGENTS

Indicator 5% K_2CrO_4 : 1g of K_2CrO_4 dissolved in

OBSERVATION AND CALCULATION

Trail	Vol of AgNO_3 (ml)		FR - IR
	Initial	Final	
Blank	0	1.4	10.8
1	0	10.8	
2	0	10.8	

$$\text{chloride in mg/L} = \frac{(V_1 - V_2) - \text{No. of } \text{AgNO}_3 \times 33.45}{\times 1000}$$

Vol of Sample

$$= \underline{\underline{177.3 \text{ mg/L}}}$$

20ml of distilled water

AgNO_3 solution

PROCEDURE

1. Take 25ml of sample in the conical flask. Adjust the sample pH b/t to be 7-8 by adding Sulphuric acid or Sodium hydroxide solution.
2. Add 1ml of Potassium chromate to get light yellow colour.
3. Titrate with standard silver nitrate (AgNO_3) solution till the colour change from yellow to brick red. Not down the volume of AgNO_3 solution added (V_1).
4. Repeat the above procedure for the blank sample (distilled water) and note down the vol of AgNO_3 solution added (V_2).

RESULT

Chloride concentration in the given sample = 177.34 mg/l

INFERENCE

The desirable limit of chloride content is 250 mg/l and permissible limit is 1000 mg/l as per IS-10500-1991. The result obtained for sample tested is 177.34 mg/l. Sample has no chloride content.

Procedure	5
Conduction	10
Result	4
Viva	3
Record	4

26/30
12/10/22

May 14
HOD

EXPT NO : 4

11/10/22

11

DETERMINATION OF ACIDITY

AIM

To determine the acidity in the given water and waste sample.

PRINCIPLE

Hydrogen ions present in a sample as a result of dissociation or hydrolysis of solutes are neutralised by titration with standard alkali. The acidity thus depends upon the end point pH or indicator used.

APPARATUS

Burette, pipette, conical flask, Measuring cylinder, volumetric flask and beakers.

REAGENTS

0.02N NaOH solution: Dissolve 0.8g of NaOH in distilled water and dilute to 1000ml.

Me-thyl orange indicator

Phenolphthaleine indicator.

PROCEDURE

1. Pipette out 25ml of sample into conical flask. Add 2 drops of methyl orange indicator to the sample solution.
2. Titrate the sample solution against 0.02N sodium hydroxide solution. The endpoint is noted when the

OBSERVATION AND CALCULATION

Titration 1 (For methyl orange acidity)

Burette sol : NaOH

Pipette sol : Sample

Indicator : Methyl orange

End point : Yellow

Sample No	Vol of Sample	Burette reading		Vol of NaOH
		Initial	Final	
1	25	0	5.4	5.4
2	25	0	5.4	

Titration 2 (For total acidity)

Burette reading : NaOH
sol

Pipette sol : Sample

Indicator : phenolphthalein

End point : Pink

Sample No	Vol of Sample	Burette reading		Vol of NaOH
		Initial	Final	
1	25	0	6.2	6.2
2	25	0	6.2	

methyl orange acidity due to mineral acidity (as CaCO_3)

$$= \frac{V_1 \times N \text{ of NaOH} \times 50000}{\text{Vol of Sample}}$$

$$= \frac{5.4 \times 0.02 \times 50000}{25}$$

$$= 216 \text{ mg/l}$$

phenolphthalein acidity = Total acidity (as CaCO_3)

$$= \frac{V \times N \text{ of NaOH} \times 50000}{\text{Vol of Sample}}$$

$$= \frac{6.2 \times 0.02 \times 50000}{25}$$

$$= 248 \text{ mg/l}$$

colour changes from orange, red to yellow.

3. Add two drops of phenolphthalein indicators and continues the titration till a pink colour formation. Note down the volume of the titrant used.

RESULT

Methyl orange used = 216 mg/l

Phenolphthalein used = 248 mg/l

Total acidity = 248 mg/l

INFERENCE

Range of acidity is specified as the mineral acidity is restricted indirectly by the stipulation of pH in the range of 6.5 - 8.5 and the acidity due to CO_2 is never known to create any public health problems.

~~26/30~~
26/30

~~Mayth~~
HOD

Procedure	5
Conduction	10
Result	4
Viva	3
Record	4

EXPT NO: 5

19/10/22

13

DETERMINATION OF pH

AIM

To determine pH of given water sample

APPARATUS

pH meter, Beakers

PRINCIPLE

The pH electrode used in the pH measurement is a combined glass electrode. It consists of sensing or sensing half cell and reference half-cell, together form an electrode system. The sensing half-cell is a thin pH sensitive semi-permeable membrane, separating two solutions,

PROCEDURE

1. Rinse the probe with distilled water. Calibrate pH meter using reference solution.
2. Rinse the probe with sample and dip the pH measuring probe in the sample and read the value of pH on the screen of the pH meter.
3. Rinse the probe with distilled / deionized water b/w sample.
4. Thoroughly rinse the probe in distilled water after measurement. Keep it in distilled water when not in use.

OBSERVATION AND CALCULATION

Sample No	pH	
	pH meter	pH paper
A	7	6
B	4.2	4
C	9.3	12

RESULT

Sample A : Neutral solution

Sample B : Acid solution

Sample C : Basic solution

INFERENCE

As per IS 10500:1991, the pH value of water is 6.5 to 8.5. Our findings are, for sample the pH of water is neutral. for sample 2 the pH of water is acidic and sample 3 of pH of water is basic in nature.

~~26/30~~
26/30

26/30

~~May 24~~
HOD

Procedure	5
Conduction	10
Result	4
Viva	3
Record	4

EXPT NO: 6

19/10/22

15

DETERMINATION OF TURBIDITY

AIM

To determine the turbidity of given water sample.

PRINCIPLE

Turbidity is measured photo-metrically by determining the percentage of light of a given intensity is scattered or absorbed.

APPARATUS

Turbidity meter, Sample tubes

REAGENTS

Reference standard turbidity solutions (0.2, 10 & 1000 NTU)

PROCEDURE

- 1) Switch on turbidity meter and wait for few minutes till the instrument warms up.
- 2) Shake the standard solution present in the cell/bottle before keeping it in sample chamber / holder & measure the turbidity of the reference standard solution.
- 3) Any deviation in reading of the reference solution, calibrate the instrument using calibration switch.
- 4) Shake the sample before keeping it in sample chamber and note down the turbidity of the sample.

OBSERVATION AND CALCULATION

Sample No	Turbidity (NTU)
1	65

RESULT

Turbidity of given water sample is 65 NTU

INFERENCE

Acceptable limit for turbidity in water as per IS 10500 is 5-10 NTU. Since the water sample taken has turbidity 80 NTU, which is high turbidity.

~~26/30~~
26/30

26/30

~~Maya~~
HOD

Procedure	5
Conduction	10
Result	4
Viva	3
Record	4

EXPT NO: 7

1/11/22

17

DETERMINATION OF BIOCHEMICAL OXYGEN DEMAND

AIM

To determine the BOD of the given sample

PRINCIPLE

The BOD is measured by determining the oxygen consumed from a sample placed in an air-tight container and kept in a controlled environment for a preselected period of time

APPARATUS

BOD bottles, burette, Pipette, conical flask, BOD incubator

REAGENTS

1. Phosphate buffer solution
2. Magnesium Sulphate solution
3. Calcium chloride solution
4. Ferrous chloride solution
5. Dilution water

PROCEDURE

1. Dilute the settled sewage provided to 30-40 times using aerated tap water
2. Fill the BOD bottle with diluted sewage by taking care that no air bubble entraps
3. Determine the DO of the BOD sample and blank

OBSERVATION AND CALCULATION

0th day reading

Sample	Burette reading			DO in mg/l
	Final	Initial	FR-IR	
Blank	3.5	0	3.5	109.35
BOD sample	8	0	4.5	

5th day reading

Sample	Burette reading			DO in mg/l
	Final	Initial	FR-IR	
Blank	6.3	0	6.3	99.9
BOD sample	6	0	6	118.8

4. Incubate both the sample and blank BOD bottles at 20°C.
5. After 5 days take the bottles having sewage and blank from the incubator.
6. measure DO and calculate BOD 5

$$\text{Ultimate BOD, } = L_0 (1 - e^{-kt})$$

L_t = BOD at any time t

L_0 = ultimate BOD

T = Time in days

K = BOD rate constant (0.23/day)

Result :

BOD of the given sample = 109.35 mg/l

Ultimate BOD of the sample = 118.8 mg/l

Inference :

The BOD of effluent should be less than 30 mg/l. If it is to be discharged to the inland surface water. The BOD of effluent should be less than 100 mg/l. If it is to be used for land irrigation. Hence the obtained value is 109.35 mg/l. So it can't be discharged to inland surface water and can't be used for land irrigation.

Process	5
Conduction	10
Result	4
Viva	3
Record	4

May 26/30
HOD

EXPT No : 8

1 / 11 / 22

19

DETERMINATION AVAILABLE CHLORINE IN A SAMPLE OF BLEACHING POWDER

Aim:

To determine the available chlorine in the bleaching powder.

Principle:



Disinfectant capabilities of chlorine depend on its chemical form in water, which in turn is dependent on pH, temperature, organic content of water and other water quality factor. Chlorine is used in the form of free chlorine or as hydrochlorites.

Chlorine applied to water either as free chlorine or hypochlorite initially undergoes hydrolysis to form free chlorine consisting of aqueous molecular chlorine, hypochlorous acid and hypochlorite ion.

Chlorine gas rapidly hydrolyses to hypochlorite hydrolyze to

$$\text{Cl}_2 + \text{H}_2\text{O} \rightleftharpoons \text{HOCl} + \text{H}^+ + \text{Cl}^-$$

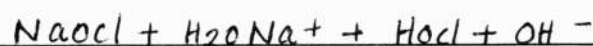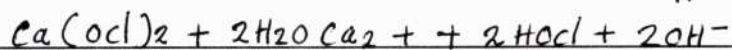Aqueous solutions of sodium or calcium hypochlorite hydrolyze to:



Hypochlorous acid is a weak acid and will disassociate according to:



The two chemical species formed by chlorine in water, hypochlorous acid (HOCl) and hypochlorite ion (OCl^-) are commonly referred to as "free" or "available" chlorine.

OBSERVATION AND CALCULATION

Sl. No	Burette Reading		Vol of titrant (ml)
	Initial	Final	
1	0	1	1

Distilled water x Standard iodine solution (0.025)

Sl. No	Burette Reading		Vol of titrant (ml)
	Initial	Final	
1	0	0.3	0.3

$$\begin{aligned}
 \text{mg of } \text{Cl}_2 (\text{mL } B) &= \frac{(V_1 - A_1) \text{ or } (V_1 + A_4) \times N \times 35.46}{\text{mL of bleaching powder sol/take}} \\
 &= \frac{1 \times 0.025 \times 35.46}{25} \\
 &= 0.035 \text{ mg/L}
 \end{aligned}$$

$$\begin{aligned}
 \% \text{ available chlorine} &= \frac{1000 \times B}{10} \div \frac{1000 \times 0.035}{10} \\
 &= 3.5 \% //
 \end{aligned}$$

Apparatus:

Beakers, conical flasks, burette.

Reagents:

standard chlorine solution, acetic acid, potassium iodide, 0.025 N standard sodium thiosulphate solution, iodine solution (0.025 N), starch indicator.

Procedure:

1. Dissolve 1g bleaching powder in 1 litre of distilled water in a volumetric flask, and stopper the container.
2. place 5ml acetic acid in an Erlenmeyer flask and add about 1g potassium iodide crystals. pour 25ml of bleaching powder solution prepared above and mix with a stirring rod.
3. Titrate with 0.025 N sodium thiosulphate solution until a pale yellow colour is obtained.
4. Add 1ml of starch solution and titrate until the blue color disappears.
5. Note down the volume of sodium thiosulphate solution added (V_1).
6. Take a volume of distilled water corresponding to the sample used.
7. Add 5ml acetic acid, 1g potassium iodide and 1ml starch solution.
8. If blue colour occurs, titrate with 0.025 N sodium thiosulphate solution until the blue colour disappears.
9. Record the volume of sodium thiosulphate solution added (A_1).
10. If no blue colour occurs, titrate with 0.025 N iodine solution until a blue colour appears. Note down the volume of iodine (A_2).

11. Then titrate with 0.025N Sodium thiosulphate solution till the blue color disappears. Record the volume of Sodium thiosulphate solution added (A_3). Note down the difference between the volume of iodine solution and Sodium thiosulphate as A_4 ($A_4 = A_2 - A_3$)

Result:

The available chlorine in given bleaching powder = 3.5%.

Inference:

The commercial bleaching powder normally contains low values of chlorine which vary from 25-30%. The value of available chlorine content continuously decreases if the powder is exposed to atmosphere. Before using the bleaching powder, its strength should first be checked by actual practice in the lab. Here the given bleaching powder sample consists of available chlorine 3.5%.

Resalita
21/12

26/30

	5
Calculation	10
Result	4
Viva	3
Record	4

Maya
HOD

EXPT NO: 9

1/11/22

22

DETERMINATION OF DISSOLVED OXYGEN

AIM


To determine the amount of dissolved oxygen present in the given sample.

PRINCIPLE

It is based on the principle that oxygen present in the sample oxidizes the divalent manganous to its higher valency under alkaline condition and the manganous in higher state of valencies is capable of oxidizing H_2I_2 under acidic conditions. Thus the amount of I_2 released is equivalent to the dissolved oxygen present.



If oxygen is present

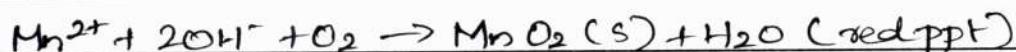

Under low pH



I_2 is rather insoluble in water, but forms a complex with the excess iodide present.



OBSERVATION AND CALCULATION

$$DO \text{ (mg/l)} = \frac{\text{ml of titrant} \times \text{normality of titrant} \times 8000}{\text{Vol of sample titrated.}}$$

Sl. No	Burette reading ($\text{Na}_2\text{S}_2\text{O}_3 \cdot 5\text{H}_2\text{O}$) ml		FR-IR
	Initial	Final	
1	0	6.5	6.5

$$\begin{aligned}\text{Dissolved oxygen of saturated sample} &= \text{Vol of titrant used} \\ &= 6.5 \text{ mg/l}\end{aligned}$$

$$\text{water temperature} = 28^\circ\text{C}$$

$$DO \text{ at water temperature} = 7.3 \text{ mg/l}$$

$$\begin{aligned}\% \text{ saturation of DO of given sample at water} \\ \text{temperature} &= \frac{6.5 \times 100}{7.3} = 89.04\%\end{aligned}$$

APPARATUS

300ml BOD bottle, burette, pipette, conical flask etc

REAGENTS

Manganous Sulphate solution

Alkaline-iodide - Sodium azide solution

Starch indicator solution

Solution thiosulphate standard solution, 0.025 ml.

PROCEDURE

- 1) Collect the sample to be tested in a 300ml BOD bottle taking special care to avoid adding air to the liquid being collected. Fill bottle completely and add stopper.
- 2) Remove bottle stopper and add 2 ml of manganous sulphate solution at the surface of the liquid. Add 2 ml of the alkaline iodide sodium azide sol at the surface of the liquid.
- 3) Repeat shaking after floc has settled halfway. Allow floc to settle a second time.
- 4) Add 2 ml of concentrated sulfuric acid and close the bottle with stopper. Rinse the top of the bottle to remove any acid and shake well until the ppt is completely dissolved.
- 5) Take 200 ml of sample from the BOD bottle into a conical flask and titrate with 0.025N sodium thiosulphate until the solution is a pale yellow colour.

RESULT :

DO of given sample = 6.5 mg/L

INFERENCE :

As per IS 2296-1982, the drinking water source should contain a DO level more than 5 mg/l. The total sample has DO 6.5 mg/l hence the sample tested is potable which is conventionally treated and disinfected.

~~26/30~~
26/30

26/30

~~May 14~~
HOD

	5
	10
Result	4
Viva	3
Record	4

BREAKPOINT CHLORINATION

AIM:

Determination of the breakpoint with a graph by reacting chlorine and ammonia at different molar ratios.

THEORY:

Disinfection of pathogenic microorganisms is called disinfection. In order to prevent waterborne diseases, disinfection is applied to drinking water. While disinfectants should not adversely affect human beings and natural habitat, but should be toxic to pathogenic microorganisms.

MATERIALS USED:

- 1) A chemical containing free chlorine
- 2) Ammonia
- 3) Residual chlorine measurement reagents.

PROCEDURE:

- 1) Both chlorine and ammonia are added to a water sample to observe the breakpoint that the molar ratio of the samples will be 1 to 11.
- 2) 1 hour reaction time is waited. Then the residual chlorine is measured.

OBSERVATION AND CALCULATIONS


Vol of sample (ml)	Burette reading		Vol of thiosulphate (ml)
	Initial	Final	
200	0	0	0
200	0	1	1
200	0	1.5	1.5
200	0	2.9	2.9
200	0	3.3	3.3
200	0	3	3
200	0	2.9	2.9
200	0	2.1	2.1

$$\text{Residual chlorine (mg/l)} = \frac{(A - B) \times N \times 35450}{\text{ml of sample}}$$

A = The amount of $\text{Na}_2\text{S}_2\text{O}_3$ used for sample

B = The amount of $\text{Na}_2\text{S}_2\text{O}_3$ used for blank

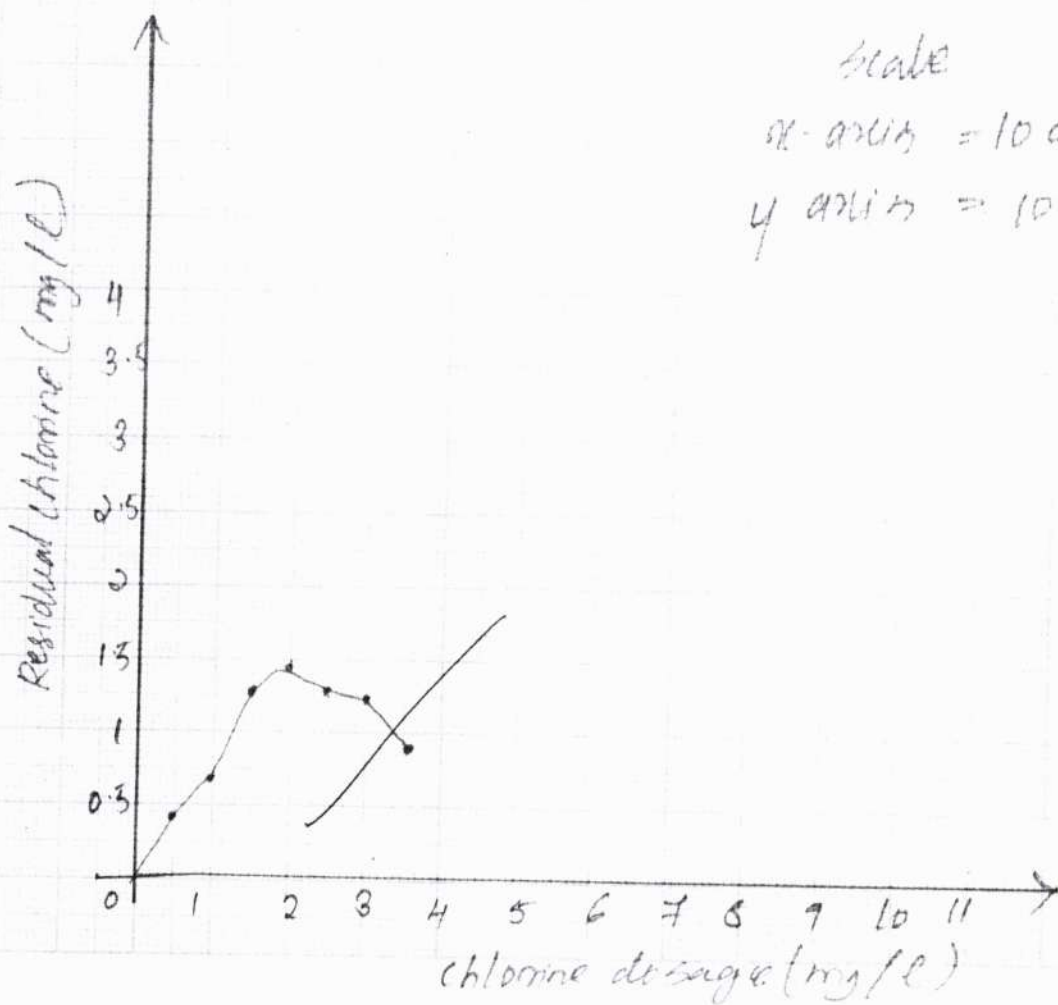N = Normality of $\text{Na}_2\text{S}_2\text{O}_3$



scale

x-axis = 10 div = 1 mg/l

y-axis = 10 div = 0.5 mg/l

$$= \frac{0.025 \times 1 \times 3545}{200}$$

$$= 0.443 //$$

ie dosage mg/l	Titration value ml	Residual chlorine (mg/l)
0	0	0
0.5	1	0.443
1	1.5	0.664
1.5	2.9	1.28
2	3.3	1.462
2.5	3	1.329
3	2.9	1.285
3.5	2.1	0.930

Sample calculation

$$\begin{aligned}
 \text{Residual chlorine} &= \frac{\text{Normality} \times \text{Vol} \times 3545}{\text{Vol of sample taken}} \\
 &= \frac{0.025 \times 1 \times 3545}{200} \\
 &= 0.443 //
 \end{aligned}$$

- 3.) Add concentrated acetic acid to each sample to bring the pH to 3-4.
- 4.) 1g of potassium iodide (KI) is added.
- 5.) The resulting colour is titrated with sodium thiosulphate until the yellow color, consumption is recorded.
- 6.) Add 1ml of starch solution.
- 7.) All these procedures applied to blank sample.
- 8.) Residual chlorine is calculated.

RESULT:

Breakpoint chlorine of water sample = 3.5 mg/l
 chlorine demand of water sample = 0.930 mg/l

INFERENCE:

Permissible limit of residual chlorine in water is 0.2 mg/l to 0.5 mg/l. The water sample given residual chlorine value = 3.5 mg/l, so it's not applicable for drinking purpose.

21/12/22

27/30

Maya
 HOD

Procedure	5
Conduction	10
Result	5
Viva	3
Record	4

EXPT NO : 11

29/11/22

27

DETERMINATION OF ELECTRICAL CONDUCTIVITY

AIM:

To determine the conductivity of the given sample of water.

PRINCIPLE:

Conductivity is determined using the distance b/t the electrodes and their surface area. According to ohm's law the current through conductors b/t 2 points is directly proportional to the potential difference across the 2 points.

APPARATUS:

Conductivity meter, Small beakers.

REAGENTS:

Distilled water or de-ionized water.

0.01 M Standard Potassium chloride solution (KCl)

PROCEDURE:

- 1) Rinse conductivity cell the 0.01 M KCl solution. Calibrate the conductivity meter using the KCl reference solu to obtain cell constant.
- 2) Measure the electrical conductivity of 0.01 M KCl solu at room temperature.

CALCULATIONS

$$C = KG$$

For 0.01 N KCl solution the 'K' value is 1410

$$EC = G_1 \times (Mmho/cm)$$

where G_1 = measured conductance of the given sample

The TDS of an unknown sample is calculated using the following relationship:

$$TDS (mg/L) = C \times EC (Mmho/cm)$$

where C is empirical constant

- 3) Rinse cell with sample and measure the electrical conductivity of the sample.
- 4) Rinse the cell with deionized water b/t samples.
- 5) Thoroughly rinse the cell in distilled water after measurement, keep it in distilled water when not in use.

RESULT:

Electrical conductivity = 217 (ms/cm, PPM)

INFERENCE:

The conductivity value gives us a rapid and inexpensive way of determining the ionic strength of the solution. This is an easy measurement to make and closely to the total dissolved solids content of water.

*gentle
slurp*

28/30

May 14
HOD

Procedure	5
Conduction	10
Result	4
Viva	3
Record	4

EXPT NO : 12

15/11/22

29

DETERMINATION OF TS, TDS and TSS, TVS

Aim:

To find the total, suspended, dissolved, volatile, fixed settleable solids present in the given sample.

APPARATUS:

Evaporating dishes/ Porcelain dish or crucible, drying oven, desiccator, weighing balance, wattman filter paper, muffle furnace.

PROCEDURE:

Total solids :

- 1) Dry evaporating dish at $104 \pm 1^\circ\text{C}$ for 1 hour, cool and store in a desiccator.
- 2) weigh the dish immediately before use. Note down the weight as B.
- 3) Stir sample with a magnetic stirrer. while stirring, pipette a measured vol into the preweighed evaporating dish
- 4) Evaporate the sample to dryness in an oven at $104 \pm 1^\circ\text{C}$ if necessary add successive portions to the same dish after evaporation.

Total dissolved Solids :

- 1) Measure the empty weight of porcelain dish and note down the reading as B.

OBSERVATION AND CALCULATION

1.) Total solids, $\text{mg/L} = \left(\frac{A - B}{V} \right) \times 1000$

$A = 38.630 \text{ g}$

$B = 38.560 \text{ g}$

$V = \text{Vol of sample (ml)} = 25 \text{ ml}$

2.) Total dissolved solids, $\text{mg/L} = \left(\frac{A - B}{V} \right) \times 1000$

$A = \text{Final weight of dish} = 38.070 \text{ mg}$

$B = 38.06$

$V = 25 \text{ ml}$

3.) Total suspended solids, $\text{mg/L} = \left(\frac{C - D}{V} \right) \times 1000$

$C = 0.670$

$D = 0.650$

$V = 25 \text{ ml}$

4.) Total volatile solids $\text{mg/L} = \left(\frac{A - B}{V} \right) \times 1000$

$A = 38.630$

$B = 36$

$V = 25 \text{ ml}$

- i) Total Solids $\text{mg/l} = 2.8 \text{ mg/l}$
ii) Total dissolved Solids, $\text{mg/l} = 0.4 \text{ mg/l}$
iii) Total suspended Solids, $\text{mg/l} = 1.6 \text{ mg/l}$
iv) Total volatile Solids = 105.2 mg/l

	Concentration (mg/l)
TS	2.8
TDS	0.4
TSS	1.6
TVS	105.2

- 2) Take known quantity of sample and pass it through the filter paper and collect the filtrate.
- 3) Dry the filtrate sample in oven at 103°C and cooled in a desiccator and note down the final weight as A.

Total Suspended Solids.

- 1) Measure the empty weight of filter paper and note down reading as B.
- 2) Dry the filter paper with filtered sample in oven at 103°C . Then cool it in a desiccator and note down the weight as C.

Total volatile Solids.

- 1) keep the sample which is oven dried in muffle furnace at a temp 600°C for 1 hr.
- 2) cool the sample and note down the final weight as D. This will give volatile solids.

RESULT:

- 1) Total Solids (TS) = 2.8 mg/l
- 2) Total dissolved solids (TDS) = 0.4 mg/l
- 2) Total Suspended Solids (TSS) = 1.6 mg/l
- 4) Total volatile Solids (TVS) = 105.2 mg/l

INFERENCE:

As per IS 10500: 1991 the desirable limit of total dissolved solids is 500 mg/l and permissible limit is 2000 mg/l . The obtained sample contains

dissolved solids in very low amount 0.4 mg/l. The sample can be used for conventional purpose.

~~20/11/22~~
16/11/22

27/30

~~May 14~~
HOD

Procedure	5
Conduction	10
Result	5
Viva	3
Record	4

EXPT NO : 13

29/11/22

32

DETERMINATION OF CHEMICAL OXYGEN DEMAND (COD)

AIM:

To determine the chemical oxygen (COD) of the given sample.

APPARATUS:

COD digestion vessel, COD digester, burette, pipette and beaker.

REAGENTS:

Standard potassium dichromate solution

Sulphuric acid reagent

Ferric indicator solution

Standard ferrous ammonium Sulphate (FAS)

PROCEDURE:

- 1) Take 2.5 ml of the sample in digestion vessel and add 1.5 ml of 0.25 N $K_2Cr_2O_7$ solution and 3.5 ml of H_2SO_4 & H_2SO_4 solⁿ.
- 2) Reflux the mixture on a hot plate/digester for 2 hrs at $150^\circ C$ and cool the mixture to room temperature.
- 3) Titrate mixture against ferrous ammonium Sulphate solⁿ using ferric indicator till blue green colour turns to reddish brown colour. Note down the volume of FAS used as 'A' ml.

CALCULATION AND OBSERVATION

Sample	Burette Reading		Dilution factors	Vol of FAS consumed
	Initial	Final		
Hot blank	0	21.1	—	380
Diluted sample	0	17.3	—	380
Hot blank	0	21.1	—	380
Diluted sample	0	17.3	—	380

$$\text{COD (mg/l)} = \frac{[(B - A) \times M \times 8000]}{\text{Vol of sample}}$$

A = FAS used for sample

B = FAS used for blank

M = Normality of FAS

$$\text{COD} = \frac{[(21.1 - 17.3) \times 0.25 \times 8000]}{20}$$

$$= 380 \text{ ml} //$$

EXPT NO : 14

29/11/22

34

DETERMINATION OF OPTIMUM COAGULATION DOSAGE:

AIM:

To find the optimum amount of coagulant required to treat given water sample.

APPARATUS:

Jar test apparatus, Turbid Meter, beakers, pipette and pH meter.

REAGENTS:


Alum, Ferric chloride

PROCEDURE:

- 1) Measure the initial turbidity of the given sample.
- 2) Find the pH of the sample and adjust it to 6 to 8.5.
- 3) Take 6 jars of 1L capacity & take 0.5 L of sample in each jar and add varying doses of alum to each one of them.
- 4) Keep the sample in jar test apparatus and put it for rapid mixing at 100 rpm for 1 min and then to slow mixing at 20 rpm for 20 min.
- 5) Stop the motor and allow the sample to settle for 30 min. Collect the supernatant from each jar and fill out the turbidity.

OBSERVATION AND CALCULATION

Concentration (ppm)	Turbidity (NTU)
1 ml alum	3.3
2 ml alum	5.8
3 ml alum	7.3
4 ml alum	4.6
5 ml alum	5.1

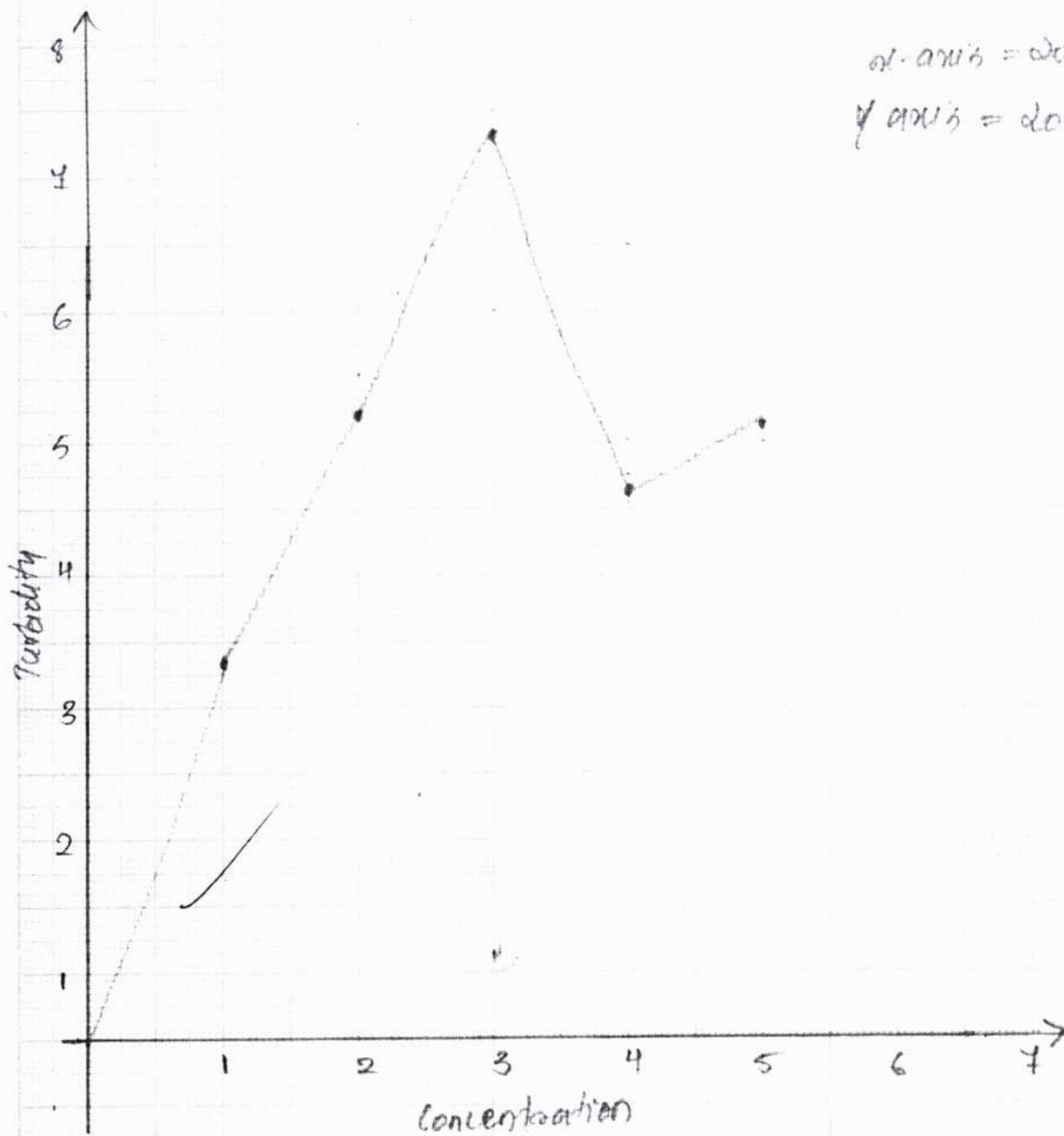

x-axis = $\text{NaOH} = 1 \text{ ppm}$
y-axis = $\text{NaOH} = 1 \text{ NTU}$

6.) Plot a graph with alum dosage along x-axis and turbidity along y-axis.

RESULT:

Optimum coagulant dosage = 3mg/l

INFERENCE:

The obtained coagulant dosage for given water sample is 3 having turbidity 4.3 NTU is 3 ml alum. This shows that water is not highly turbid.

27/11/22

27/30

Mayth
HOD

Procedure	5
Conduction	10
Result	4
Viva	3
Record	5

RESULT:

The COD of the given water sample = 380 ml

INFERENCE:

As per ELP rules the COD of effluent should be less than 250 mg/l. If it is discharged to the inland water surface, Here the COD of sample is within the limit. So it can be discharged to the inland water surface.

~~29/11/2022~~

26/30

~~May 14~~
HOD

Procedure	5
Conduction	10
Result	4
Viva	3
Record	4

EXPT NO: 15

6/12/22

86

DETERMINATION OF TOTAL COLIFORMS

Aim:

To determine the MPN content of the given water sample.

APPARATUS:

Test tubes of various capacities, Durham tube, pipette, incubator, measuring cylinder, beaker, dropper etc.

REAGENTS:

Appropriate culture medium.

PRINCIPLE:

Water to be tested is diluted serially and inoculated in lactose broth. Coliforms if present in water, utilize the lactose present in the medium to produce acid and gas. The presence of acid is indicated by colour change of the medium to produce and the presence of gas is detected as gas bubbles collected in the inverted Durham tube present in the medium.

PROCEDURE:

Presumptive test:

- 1) Inoculate a series of fermentation tubes with appropriate

OBSERVATION AND CALCULATIONS

3 of distilled water	3 of 10 ml each	3 of 1 ml each	3 of 0.1 ml each	mpn/100ml
1	2	1	0	15
2	0	0	0	3
3	3	3	0	240

$$\text{mpn/100ml} = \frac{\text{No of Positive test tube} \times 10}{\text{ml of sample in negative tubes} \times \text{ml of sample in all tubes}}$$

quantity of culture medium. Mix 5.36 g of Lauryl Typpose in 50 ml of distilled water to prepare double strength medium and 3.45 g in 150 ml to prepare single strength solution.

- 2) Take 12 test tubes and sterilize all the glass wares to be used. Add 10 ml of single strength solution in other tubes.
- 3) Put Durham tubes in inverted position and remove the air bubble in it if any by slightly tilting the test tube after capping it with sterilized cotton.

Confirmed test:

- 1) Brilliant green lactose broth is used for the confirmed test. BGLB media is prepared by dissolving 8 g of BGLB in 100 ml of distilled water.
- 2) Add 1 ml of distilled water in 3rd 3 tubes which is taken as control. Then transfer the medium in the positive tubes of the presumptive test to the BGLB tubes.
- 3) Incubate the inoculated tubes for 48 ± 3 hrs at 37°C .

RESULT:

The value of mpn/100 ml is = 240

Procedure	5
Conduction	10
Result	4
Viva	3
Record	4

26/30

May 24
HOD

completed All experiments


Staff in charge : Revathi - P
2000/11/15

May 14

HOD


Leena
Dr. LEENA A. V.
PRINCIPAL

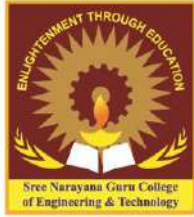SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY, PAYANUR
KANNUR




Sree Narayana Guru College of Engineering & Technology

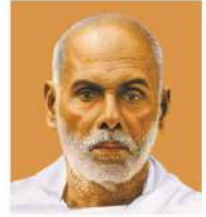CHALAKKODE P.O., KOROM, PAYYANUR, KANNUR-670 307



DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

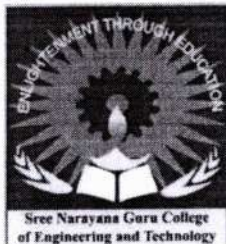**SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY,
PAYYANUR**



DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

**THIRD SEMESTER
LAB RECORD**

**CSL203 OBJECT ORIENTED PROGRAMMING LAB
(IN JAVA)**

[Handwritten Signature]
HOD/USE

[Handwritten Signature]

**Dr. LEENA A. V.
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY, PAYYANUR
KANNUR**

**SREE NARAYANA GURU COLLEGE OF ENGINEERING & TECHNOLOGY,
A P J ABDUL KALAM TECHNOLOGICAL UNIVERSITY, KERALA.**

LAB RECORD

CSL203 OBJECT ORIENTED PROGRAMMING LAB (IN JAVA)

Name: UTHARA M.V.

Semester: 3

Registration No. SNL21LS044

Certified that this is the bonafide record of the work done in "CSL203 Object Oriented Programming Laboratory in java" of Department of Computer Science and Engineering at Sree Narayana Guru College of Engineering and Technology, Payyanur, Kannur by

Mr./Ms. Uthara M.V.

for the award of the Degree of Bachelor of Technology in Computer Science & Engineering of A P J Abdul Kalam Technological University, Kerala

Staff in-charge

Head of the Department

Place: Payyanur

Date: 3/12/22

Internal Examiner

Leena
Dr. LEENA A. V.
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY, PAYANUR
KANNUR

External Examiner

DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

VISION OF THE DEPARTMENT

To be a centre of excellence in Computer Science and Engineering to produce competent professionals and entrepreneurs capable of exploring and assimilating latest technological advancements for the betterment of the society.

MISSION OF THE DEPARTMENT

- To facilitate transformative education in computer science and engineering.
- To build competent professionals and entrepreneurs by introducing new technologies.
- To accomplish higher education, induce ethical values and spirit of social commitment.

S. S. S. S. S.
HOD/USE

Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

PROGRAM EDUCATIONAL OBJECTIVES (PEOs)

PEO1: To prepare students to excel in Computer Science and Engineering programme through quality education enabling them to succeed in computing industryprofession.

PEO2: To provide students with core competencies by strengthening their mathematical, scientific and basic engineering fundamentals.

PEO3: To design & develop novel products and innovative solutions for real life problems in Computer Science & Engineering field and related domains by broad based knowledge.

PEO4: To inculcate professionalism among students by providing technical, entrepreneurial skills and soft skills with ethical standards.

PEO5: To encourage students for higher studies by adapting to new technologies through interactive quality teaching and organizing symposiums, conferences, seminars, workshops and technical discussions.

S. Sankar
HOD/UE

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROGRAMME OUTCOMES (POs)

Engineering Graduates will be able to:

1. **Engineering Knowledge:** Apply the knowledge of mathematics, science, engineering Fundamentals, and an engineering specialization to the solution of complex engineering problems.
2. **Problem Analysis:** Identify, formulate, review research literature, and analyze complex engineering problems reaching substantiated conclusions using first principles of mathematics, natural sciences, and engineering sciences.
3. **Design/ Development of Solutions:** Design solutions for complex engineering problems and design system components or processes that meet the specified needs with appropriate consideration for the public health and safety, and the cultural, societal, and environmental considerations.
4. **Conduct Investigations of Complex Problems:** Use research-based knowledge and research methods including design of experiments, analysis and interpretation of data, and synthesis of the information to provide valid conclusions.
5. **Modern Tool Usage:** Create, select, and apply appropriate techniques, resources, and modern engineering and IT tools including prediction and modeling to complex engineering activities with an understanding of the limitations.
6. **The Engineer and Society:** Apply reasoning informed by the contextual knowledge to assess societal, health, safety, legal and cultural issues and the consequent responsibilities relevant to the professional engineering practice.
7. **Environment and Sustainability:** Understand the impact of the professional engineering solutions in societal and environmental contexts, and demonstrate the knowledge of, and need for sustainable development.
8. **Ethics:** Apply ethical principles and commit to professional ethics and responsibilities and norms of the engineering practice.
9. **Individual and Team Work:** Function effectively as an individual, and as a member or leader in diverse teams, and in multidisciplinary settings.
10. **Communication:** Communicate effectively on complex engineering activities with the engineering community and with society at large, such as, being able to comprehend and write effective reports and design documentation, make effective presentations, and give and receive clear instructions.
11. **Project Management and Finance:** Demonstrate knowledge and understanding of the engineering and management principles and apply these to one's own work, as a member and leader in a team, to manage projects and in multidisciplinary environments.
12. **Life-long learning:** Recognize the need for, and have the preparation and ability to engage in independent and life-long learning in the technology and its associated changes.

Dr. Leena A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

PROGRAM SPECIFIC OUTCOMES (PSOs)

PSO1: Computer Science Specific Skills: The ability to identify, analyze and design solutions for complex engineering problems in multidisciplinary areas by understanding the core principles and concepts of computer science.

PSO2: Programming and Software Development Skills: The ability to acquire programming efficiency by designing algorithms and applying standard practices in software project development to deliver quality software products.

S. Sankar
HOD/USE

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

SYLLABUS

CSL203	OBJECT ORIENTED PROGRAMMING LAB (IN JAVA)	CATEGORY	L	T	P	CREDIT	YEAR OF INTRODUCTION
		PCC	0	0	3	2	2019

Preamble: The aim of the course is to provide hands-on experience to the learners on various object-oriented concepts in Java Programming. This course helps the learners to enhance the ability to design and implement various Java applications for real world problems.

Prerequisite: Topics covered under the course Programming in C (EST 102)

Course Outcomes:

After the completion of the course the student will be able to

CO1	Implement the Object-Oriented concepts - constructors, inheritance, method overloading & overriding and polymorphism in Java (Cognitive Knowledge Level: Apply)
CO2	Implement programs in Java which use data types, operators, control statements, built in packages & interfaces, Input/output streams and Files (Cognitive Knowledge Level: Apply)
CO3	Implement robust application programs in Java using exception handling (Cognitive Knowledge Level: Apply)
CO4	Implement application programs in Java using multithreading and database connectivity (Cognitive Knowledge Level: Apply)
CO5	Implement Graphical User Interface based application programs by utilizing event handling features and Swing in Java (Cognitive Knowledge Level: Apply)

Santhosh
HOD/ISE

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Mapping of course outcomes with program outcomes


	PO1	PO2	PO3	PO4	PO5	PO6	PO7	PO8	PO9	PO10	PO11	PO12
CO1	✓	✓	✓	✓	✓			✓		✓		✓
CO2	✓	✓	✓	✓	✓			✓		✓		✓
CO3	✓	✓	✓	✓	✓			✓		✓		✓
CO4	✓	✓	✓	✓	✓			✓		✓		✓
CO5	✓	✓	✓	✓	✓			✓		✓		✓

Abstract Pos defined by National Board Of Accreditation

PO #	Broad PO	PO #	Broad PO
PO1	Engineering Knowledge	PO7	Environment and Sustainability
PO2	Problem Analysis	PO8	Ethics
PO3	Design/Development of solutions	PO9	Individual and teamwork
PO4	Conduct investigations of complex problems	PO10	Communication
PO5	Modern tool usage	PO11	Project Management and Finance
PO6	The Engineer and Society	PO12	Lifelong learning

Assessment Pattern:

Bloom's Category	Continuous Assessment Test (Internal Exam) Markin Percentage	End Semester Marks in percentage
Remember	20	20
Understand	20	20
Apply	60	60
Analyze		
Evaluate		
Create		

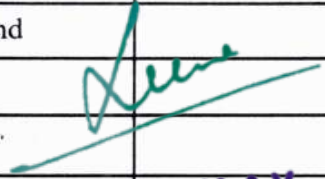
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

Mark Distribution

Total Marks	CIE Marks	ESE Marks	ESE Duration
150	75	75	3 hours

Continuous Internal Evaluation Pattern:

Attendance	:	15
Marks Continuous Evaluation in Lab	:	30
Marks Continuous Assessment Test	:	15
Marks Viva Voce	:	15

Internal Examination Pattern: The marks will be distributed as Algorithm 30 marks, Program 20 marks, Output 20 marks and Viva 30 marks. Total 100 marks which will be converted out of 15 while calculating Internal Evaluation marks.


End Semester Examination Pattern: The marks will be distributed as Algorithm 30 marks, Program 20 marks, Output 20 marks and Viva 30 marks. Total 100 marks will be converted out of 75 for End Semester Examination.

Operating System to Use in Lab: Linux

Compiler/Software to Use in Lab: gcc, javac, jdk, jre, Eclipse, NetBeans, MySQL/PostgreSQL.

Programming Language to use in Lab: Java


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

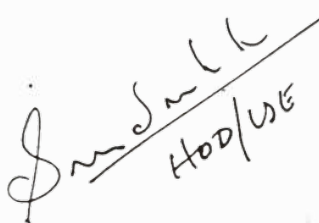
HOD/USE

LIST OF EXPERIMENT

CYCLE - 1

1. Write a Java Program to find the frequency of a given character in a string.
2. Write a Java program to multiply two given matrices.

CYCLE - 2

3. Write a Java program which creates a class named 'Employee'
4. Write a java program to create an abstract class.
5. Write a Java program that read from a file and write to file by handling all file related exceptions.
6. Write a Java program that reads a line of integers, and then displays each integer, and the sum of all the integers.
7. Write a Java program that shows the usage of try, catch, throws and finally.
8. Write a Java program that shows thread synchronization.
9. Write a Java program that works as a simple calculator.
10. Write a Java program that simulates a traffic light.

CYCLE - 3


11. Write a Java program for doubly linked list operations.
12. Write a Java program that implements Quick sort algorithm

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

[Signature]
HOD/USE

PRACTICE QUESTIONS

- 1) Write a Java program to reverse an given string.
- 2) Write a Java program to display the transpose of a given matrix.
- 3) Write a Java program to find the second smallest element in an array.
- 4) Write a Java program to check whether a given number is prime or not.
- 5) Write a Java program to calculate the area of different shapes namely circle, rectangle, and triangle using the concept of method overloading.
- 6) Write two Java classes Employee and Engineer. Engineer should inherit from Employee class. Employee class to have two methods display() and calcSalary(). Write a program to display the engineer salary and to display from Employee class using a single object in- stantiation (i.e., only one object creation is allowed).
 - display() only prints the name of the class and does not return any value. Ex. " Name of class is Employee."
 - calcSalary() in Employee displays "Salary of employee is 10000" and calcSalary() in Engineer displays "Salary of employee is 20000."
- 7) Write a Java program to illustrate Interface inheritance.
- 8) Write a Java program that shows how to create a user-defined exception.
- 9) Write a Java program to create two threads: One for displaying all odd number between 1 and 100 and second thread for displaying all even numbers between 1 and 100.
- 10) Write a Java program that shows thread priorities.
- 11) Write a Java program that reads a file and displays the file on the screen, with a line number before each line.
- 12) Write a Java program that displays the number of characters, lines and words in a text file.

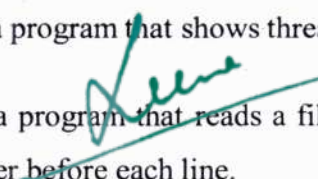
Dr. LEENA A V
PRINCIPAL
SREE NARAYANAGURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

- 13) Write a Java program for handling mouse events.
- 14) Write a Java program for handling key events using Adapter classes (general).
- 15) Write a Java program that allows the user to draw lines, rectangles and ovals.
- 16) Write a Java Swing program to print a wave form on the output screen.
- 17) Write a program to accept roll no, name, CGPA of "n" students and store the data to a database using JDBC connectivity. Display the list of students having CGPA greater than (Use MySQL /PostgreSQL).
- 18) Write a Java program to implement Heap sort algorithm using array.
- 19) Write a Java program that checks whether a given string is a palindrome or not. Ex: MALAYALAM is palindrome.
- 20) Write a Java program to demonstrate the use of garbage collector.
- 21) Write a file handling program in Java with reader/writer Write a Java program that implements a multi-threaded program which has three threads. First thread generates a random integer every 1 second. If the value is even, second thread computes the square of the number and prints. If the value is odd the third thread will print the value of cube of the number.
- 22) Write a Java program to display all records from a table using Java Database Connectivity (JDBC).
- 23) Write a Java program that implements the binary search algorithm.

Santhosh
HOD/WE


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

INDEX					
Sl No.	Experiment	Date	Page No.	Mark	Remarks
1	Java Program to find the frequency of a given character in a string.	14/09/22	3	48	Vad 16/9/22
2	Java program to multiply two given matrices.	14/09/22	11	47	Vad 16/9/22
3	Java program which creates a class named 'Employee'	15/09/22	21	46	Vad 16/9/22
4	Java program to create an abstract class.	29/09/22	29	46	Vad
5	Java program that read from a file and write to file by handling all file related exceptions	16/10/22	37	47	Vad 21/10/22
6	Java program that reads a line of integers, and then displays each integer, and the sum of all the integers.	26/10/22	45	46	Vad 26/10/22
7	Java program that shows the usage of try, catch, throws and finally.	26/10/22	53	46	Vad 26/10/22
8	Java program that shows thread synchronization.	27/10/22	61	47	Vad 27/10/22
9	Java program that works as a simple calculator.	3/11/22	69	45	Vad 3/11/22
10	Java program that simulates a traffic light.	10/11/22	77	47	Vad 10/11/22
11	Java program for doubly linked list operations.	17/11/22	87	46	Vad 17/11/22
12	Java program that implements Quick sort algorithm	30/11/22	95	47	Vad 21/12/22

Dr. Leena A. V.
HOD/USE

Dr. LEENA A. V.
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY, PAYANUR
KANNUR

PROGRAM & OUTPUT

PROGRAM :-

```
import java.util.Scanner;
public class Frequency
{
    public static void main(String[] args)
    {
        Scanner sc=new Scanner (System.in);
        System.out.println("Enter The String:");
        String str=sc.nextLine();
        System.out.print("Enter The Character:");
        char ch=sc.nextLine().charAt(0);
        int count=0;
        for(int i=0;i<str.length();i++)
        {
            if(str.charAt(i)==ch)
            {
                count++;
            }
        }
        System.out.println("Count Of Occurance Of "+ch+"="+count );
    }
}
```

OUTPUT :-

```
Enter The String:
hello world
Enter The Character: o
Count Of Occurance Of o=2
```

Program No: 1

Date: 14/09/22

Java Program to find the frequency of a given character in a string

AIM

Write a java programs to find the frequency of a given character in a string using data types, operators, and control statements in Java.

ALGORITHM / PROCEDURE

- Step 1:- start
- Step 2:- import java utility package including Scanner class
- Step 3:- Defining class frequency
- Step 4:- Define main function
- Step 5:- int i=0, count=0, char ch, string str;
- Step 6:- Create an instance for scanner to read input
- Step 7:- print "Enter the word".
- Step 8:- Read the string and assign to str.
- Step 9:- print "Enter the character to check".
- Step 10:- Read the character and assign it to ch
- Step 11:- If (i < length of string str) go to step 12 else go to step 15.
- Step 12:- If (str.charAt(i) == ch) go to step 13, else go to step 14
- Step 13:- count ++
- Step 14:- i ++, go to step 11
- Step 15:- print count of occurrence of " + ch + "
- Step 16:- Stop.


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

SCORING SHEET

No.	Performance criteria	Excellent-10	Good-8	Satisfactory-5	Poor-3	Total
1.	Algorithm / Procedure	The algorithm is precise, logically correct and is computable in minimum time.	The algorithm is logically correct. But it is not completely precise and the computation time is not minimum.	The algorithm is logically correct. But not fully precise and takes large amount of time to compute.	The algorithm is just logically correct.	10
2.	Program	The code is well organized, easy to follow and logically correct.	The code is fairly organized.	The code is readable only by someone who knows its logic.	The code is poorly organized.	10
3.	Output	Accurate results have been achieved for all possible inputs and well formatted.	Accurate results have been achieved for the majority of the inputs.	Program produces accurate results but output is not properly formatted.	The program is free of errors but produces in accurate results.	10
4.	Record	Well kept, strong characterize, standardized and finished within time.	Well kept, attempt is somewhat standardized and finished.	Record is somewhat standardized but not well kept.	Not standardized and well kept also. Some entries are imperfect.	10
Total Marks						40

CRITERIA		MARKS
Performance	40	40
Viva	10	8
Total	50	48

Leena
Dr. LEENA A V
PRINCIPAL

**SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR**

r-3	Total
gorithm	
lly t	10
code is rly nized.	10
program ee of rs but duces in urate alts.	10
t ndardized l well kept o. Some ries are perfect.	10
tal Marks	40

RESULT

Output obtained successfully and verified

[Signature]
16/7/22

[Signature]
HOD/USE

[Signature]
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

PROGRAM :-

```
import java.util.Scanner;
class Matrix
{
    public static void main(String args[])
    {
        Scanner sc=new Scanner(System.in);
        System.out.print("Enter the order-m1:");
        int m1=sc.nextInt();
        System.out.print("Enter the order-n1:");
        int n1=sc.nextInt();
        System.out.print("Enter the order-m2:");
        int m2=sc.nextInt();
        System.out.print("Enter the order-n2:");
        int n2=sc.nextInt();
        if(n1!=m2)
        {
            System.out.println("Matrix Multiplication not possible");
            return;
        }
        int A[][]=new int[m1][n1];
        int B[][]=new int[m2][n2];
        int C[][]=new int[m1][n2];
        System.out.println("Read Matrix A");
        for(int i=0;i<m1;i++)
        {
            for(int j=0;j<n1;j++)
            {
                System.out.print("A["+i+""]["+j+""]=");
                A[i][j]=sc.nextInt();
            }
        }
        System.out.println("Read Matrix B");
        for(int i=0;i<m2;i++)
        {
            for(int j=0;j<n1;j++)
            {
                System.out.print("B["+i+""]["+j+""]=");
                B[i][j]=sc.nextInt();
            }
        }
        for(int i=0;i<m1;i++)
        {
            for(int j=0;j<n2;j++)
            {
                C[i][j]=0;
                for(int k=0;k<n1;k++)
                {
                    C[i][j]+=A[i][k]*B[k][j];
                }
            }
        }
    }
}
```


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Program No: 2

Date: 14/09/22

Java Program to multiply two given matrices

AIM

Write a Java program to multiply two given matrices using data types, operators, and control statements in Java.

ALGORITHM / PROCEDURE

- Step 1:- Start
- Step 2:- Import java utility package including scanner class
- Step 3:- Defining class TestMatrix
- Step 4:- Define main function
- Step 5:- Initialize integer k, i, j, m₁, m₂, n₁, n₂, a[i][j], b[i][j], c[i][j]
- Step 6:- create an instance for the Scanner to read the input
- Step 7:- Print 'Enter order m1'
- Step 8:- Read value to m1
- Step 9:- Print "Enter order n1"
- Step 10:- Read value to n1
- Step 11:- Print 'Enter order m2'
- Step 12:- Read value to m2
- Step 13:- Print 'Enter order n2'
- Step 14:- Read value to n2
- Step 15:- if (n₁ ≠ m₂) print "operation not possible" then go to step else go to step 16
- Step 16:- Assign
A[i][j] = new int[m₁][n₁]
B[i][j] = new int[m₂][n₂]
C[i][j] = new int[m₁][n₂]

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR


```

    }
    }
    System.out.println("Matrix A");
    for(int i=0;i<m1;i++)
    {
        for(int j=0;j<m1;j++)
        {
            System.out.print(A[i][j]+"\\t");
        }
        System.out.println();
    }
    System.out.println("Matrix B");
    for(int i=0;i<m2;i++)
    {
        for(int j=0;j<n2;j++)
        {
            System.out.print(B[i][j]+"\\t");
        }
        System.out.println();
    }
    System.out.println("Matrix C");
    for(int i=0;i<m1;i++)
    {
        for(int j=0;j<n2;j++)
        {
            System.out.print(C[i][j]+"\\t");
        }
        System.out.println();
    }
    }
}

```



Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

step 17:- print " Enter elements of matrix A "
 step 18:- $i = 0, j = 0$
 step 19:- if ($i < m$) go to step 20, else goto step 24.
 step 20:- if ($j < n_1$) go to step 21, else goto step 23.
 step 21:- Read $A[i][j]$
 step 22:- $j++$, go to step 20
 step 23:- $i++$, go to step 19
 step 24:- $i = 0, j = 0$
 step 25:- print " Enter element to matrix B "
 step 26:- if ($i < m_2$) go to step 27, else go to step 31
 step 27:- if ($j < n_2$) go to step 28, else go to step 30.
 step 28:- Read $B[i][j]$
 step 29:- $j++$, go to step 27
 step 30:- $i++$, go to step 26.
 step 31:- $i = 0, j = 0, k = 0$
 step 32:- if ($i < m_1$) go to step 33, else go to 40.
 step 33:- if ($j < n_2$) go to step 34, else go to 39.
 step 34:- $C[i][j] = 0$
 step 35:- if ($k < m$) go to step 36, else go to step 40
 step 36:- $C[i][j] = A[i][k] * B[k][j]$
 step 37:- $k++$, go to step 35
 step 38:- $j++$, go to step 33
 step 39:- $i++$, go to step 32
 step 40:- print $C[i][j]$
 step 41:- Stop.


Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PAYYANUR, KANNUR

OUTPUT :-

Enter the order-m1:2
Enter the order-n1:2
Enter the order-m2:2
Enter the order-n2:2
Read Matrix A
A[0][0]=55
A[0][1]=6
A[1][0]=7
A[1][1]=1
Read Matrix B
B[0][0]=5
B[0][1]=4
B[1][0]=88
B[1][1]=324
Matrix A
55 6
7 1
Matrix B
5 4
88 324
Matrix C
803 2164
123 352


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

SCORING SHEET

No.	Performance criteria	Excellent-10	Good-8	Satisfactory-5	Poor-3	Total
1.	Algorithm / Procedure	The algorithm is precise, logically correct and is computable in minimum time	The algorithm is logically correct. But it is not completely precise and the computation time is not minimum.	The algorithm is logically correct. But not fully precise and takes large amount of time to compute	The algorithm is just logically correct	10
2.	Program	The code is well organized, easy to follow and logically correct.	The code is fairly organized.	The code is readable only by someone who knows its logic.	The code is poorly organized.	10
3.	Output	Accurate results have been achieved for all possible inputs and well formatted.	Accurate results have been achieved for the majority of the inputs.	Program produces accurate results but output is not properly formatted.	The program is free of errors but produces in accurate results.	10
4.	Record	Well kept, strong characterize, standardized and finished within time.	Well kept, attempt is somewhat standardized and finished.	Record is somewhat standardized but not well kept.	Not standardized and well kept also. Some entries are imperfect.	10
Total Marks						40

CRITERIA		MARKS
Performance	40	40
Viva	10	7
Total	50	47

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

oor-3	Total
Algorithm tally ct	10
Code is y nized.	10
Program e of ; but ices in ate s.	10
Standardized well kept Some s are fect.	10
Total Marks	40

Result

Output obtained and verified successfully

[Signature]
16/9/22

[Signature]
HOD/WE

[Signature]

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

CYCLE - 2


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROGRAM :-

```
import java.util.Scanner;
class Employee
{
    private String name;
    private int age;
    private long phoneNO;
    private String address;
    private double salary;
    public void setName(String name)
    {
        this.name=name;
    }
    public void setAge(int age)
    {
        this.age=age;
    }
    public void setPhoneNO(long phoneNO )
    {
        this.phoneNO=phoneNO;
    }
    public void setAddress(String address)
    {
        this.address=address;
    }
    public void setSalary(double salary)
    {
        this.salary=salary;
    }
    public double printSalary()
    {
        return salary;
    }
    public String getName()
    {
        return name;
    }
    public int getAge()
    {
        return age;
    }
    public String getAddress()
    {
        return address;
    }
    public long getPhoneNO()
    {
        return phoneNO;
    }
}
```


Program No: 3

Date: 15/09/22

Java Program Which Creates a Class Named 'Employee'

AIM

Write a Java program which creates a class named 'Employee' having the following members: Name, Age, Phone number, Address, Salary. It also has a method named 'print Salary ()' which prints the salary of the Employee. Two classes 'Officer' and 'Manager' inherit the 'Employee' class. The 'Officer' and 'Manager' classes have data members 'specialization' and 'department' respectively. Now, assign name, age, phone number, address and salary to an officer and a manager by making an object of both of these classes and print the same. (Exercise to understand inheritance).

ALGORITHM / PROCEDURE

- Step 1:- start
- Step 2:- import utility package.
- Step 3:- Create a class Employee in that initialize private data variable such as name, age, phone number, address, salary
- Step 4:- Accept data from the user by using methods
- Step 4.1:- Use method setName (String name) to accept the name from user.
- Step 4.2:- Use method setAge (int age) to accept the ^{age} ~~name~~ from user
- Step 4.3:- Use method setphoneNumber (long phone number) to accept phone number from user.
- Step 4.4:- Use method setAddress (String Address) to accept address from user
- Step 4.5:- Use method setSalary (double ^{Salary} ~~Salary~~) to accept the salary from user.
- Step 5:- From step 4.1 to 4.5 accepting data in a syntax format using the key ~~the~~ ^{key} of the current class instance

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR


```

    }
    class Officer extends Employee
    {
        private String specialization;
        private String department;
        public void setSpecialization(String specialization)
        {
            this.specialization=specialization;
        }
        public void setDepartment(String department)
        {
            this.department=department;
        }
        public String getDepartment()
        {
            return department;
        }
        public String getSpecialization()
        {
            return specialization;
        }
    }
    class Manager extends Employee
    {
        private String specialization;
        private String department;
        public void setSpecialization(String specialization)
        {
            this.specialization=specialization;
        }
        public void setDepartment(String department)
        {
            this.department=department;
        }
        public String getDepartment()
        {
            return department;
        }
        public String getSpecialization()
        {
            return specialization;
        }
    }
    class Test{
        public static void main(String[] args)
        {
            Scanner sc=new Scanner(System.in);
            Officer o=new Officer();
            System.out.println("ENTER THE OFFICER'S DETAIL");
            System.out.print("NAME:");
            o.setName(sc.nextLine());
        }
    }

```


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

- Step 6:- Create public double print salary() to return the salary.
- Step 6.1:- public String getName() to return the Name which accept from the user.
- Step 6.2:- public int getAge() to return the Age which is accepted from the user
- Step 6.3:- public String getAddress() to return the address which is accepted from the user.
- Step 6.4:- public long get phoneNumbers() to return the phonenumber which is accepted from the user.
- Step 7:- close the Employee class.
- Step 8:- create a class officer using extends keyword by inheriting the properties for the class employee.
- Step 9:- Initialize private variable such as String Specification and department.
- Step 10:- Use method set specification(String specification) to accept the data from the user.
- Step 10.1:- Use method set department(String department) to accept the data from user.
- Step 11:- Use this keyword to show the current class and initialize both step 10 and step 10.1.
- Step 12:- public String get department() to return the accepted data from the user.
- Step 12.1:- public String get specifications() to return the accepted data from the user.
- Step 13:- close the class officer.
- Step 14:- create class Manager which extends the properties from employee class.
- Step 15:- Initialize private String specification and String department.
- Step 16:- Repeat from step 10 to step 15.

Dr. Leena
DR. LEENA A.V.
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PAYYANUR, KANNUR


```

System.out.print("ADDRESS:");
o.setAddress(sc.nextLine());
System.out.print("SPECIALIZATION:");
o.setSpecialization(sc.nextLine());
System.out.print("DEPARTMENT:");
o.setDepartment(sc.nextLine());
System.out.print("AGE:");
o.setAge(sc.nextInt());
System.out.print("NUMBER:");
o.setPhoneNO(sc.nextLong());
System.out.print("SALARY:");
o.setSalary(sc.nextDouble());
sc.nextLine();
System.out.println("THE OFFICER DETAIL");
System.out.println("NAME:"+o.getName());
System.out.println("AGE:"+o.getAge());
System.out.println("NUMBER:"+o.getPhoneNO());
System.out.println("ADDRESS:"+o.getAddress());
System.out.println("SALARY:"+o.printSalary());
System.out.println("SPECIALIZATION:"+o.getSpecialization());
System.out.println("DEPARTMENT:"+o.getDepartment());

```

```

Manager m=new Manager();
System.out.println("ENTER THE MANAGER'S DETAIL");
System.out.print("NAME:");
m.setName(sc.nextLine());
System.out.print("ADDRESS:");
m.setAddress(sc.nextLine());
System.out.print("SPECIALIZATION:");
m.setSpecialization(sc.nextLine());
System.out.print("DEPARTMENT:");
m.setDepartment(sc.nextLine());
System.out.print("AGE:");
m.setAge(sc.nextInt());
System.out.print("NUMBER:");
m.setPhoneNO(sc.nextLong());
System.out.print("SALARY:");
m.setSalary(sc.nextDouble());
sc.nextLine();

```

```

System.out.println("THE MANAGER'S DETAIL");
System.out.println("NAME:"+m.getName());
System.out.println("AGE:"+m.getAge());
System.out.println("NUMBER:"+m.getPhoneNO());
System.out.println("ADDRESS:"+m.getAddress());
System.out.println("SALARY:"+m.printSalary());
System.out.println("SPECIALIZATION:"+m.getSpecialization());
System.out.println("DEPARTMENT:"+m.getDepartment());
}
}

```

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Step 17:- close the manager class

Step 18:- create new class test which has main function in it

Step 19:- create object

```
Scanner sc = new Scanner(System.in) to read the  
input from user officer o = new officer();  
Manager m = new manager();
```

Step 20:- Display all the necessary statement such as officer details, name, age, phone number, address, specification, department using printing statement for both officer detail and manager detail.

Step 21:- call them using objects to display it

Step 22:- Stop.

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

SCORING SHEET

No.	Performance criteria	Excellent-10	Good-8	Satisfactory-5	Poor-3	Total
1.	Algorithm / Procedure	The algorithm is precise, logically correct and is computable in minimum time	The algorithm is logically correct. But it is not completely precise and the computation time is not minimum.	The algorithm is logically correct. But not fully precise and takes large amount of time to compute	The algorithm is just logically correct	10
2.	Program	The code is well organized, easy to follow and logically correct.	The code is fairly organized.	The code is readable only by someone who knows its logic.	The code is poorly organized.	10
3.	Output	Accurate results have been achieved for all possible inputs and well formatted.	Accurate results have been achieved for the majority of the inputs.	Program produces accurate results but output is not properly formatted.	The program is free of errors but produces in accurate results.	10
4.	Record	Well kept, strong characterize, standardized and finished within time.	Well kept, attempt is somewhat standardized and finished.	Record is somewhat standardized but not well kept.	Not standardized and well kept also. Some entries are imperfect.	10
Total Marks						40

CRITERIA		MARKS
Performance	40	40
Viva	10	6
Total	50	46


Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PAYYANUR, KANNUR

	Total
thm	
	10
is	
	10
am	
n	
	10
ed cept e :	
	10
rks	40

Result

Output obtained and verified successfully

[Signature]
16/9/22

[Signature]
HOD/WE

[Signature]
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROGRAM :-

```
abstract class Shape
{
    public abstract void numberOfSides();
}

class Rectangle extends Shape
{
    public void numberOfSides()
    {
        System.out.println("Number of sides = 4");
    }
}

class Triangle extends Shape
{
    public void numberOfSides()
    {
        System.out.println("Number of sides = 3");
    }
}

class Hexagon extends Shape
{
    public void numberOfSides()
    {
        System.out.println("Number of sides = 6");
    }
}

class Abstractcls
{
    public static void main(String args[])
    {
        Rectangle r = new Rectangle();
        Triangle t = new Triangle();
        Hexagon h = new Hexagon();
        r.numberOfSides();
        t.numberOfSides();
        h.numberOfSides();
    }
}
```

OUTPUT :-

Number Of Sides = 4
Number Of Sides = 3
Number Of Sides = 6


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Hexagon : Hexagon h = new hexagon ();

Step 15 :- call all the method

r.numberofsides()

l.numberofsides()

h.numberofsides()

Step 16 :- close the main function and close the class

Step 17 :- Stop.



Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

SCORING SHEET

No.	Performance criteria	Excellent-10	Good-8	Satisfactory-5	Poor-3	Total
1.	Algorithm / Procedure	The algorithm is precise, logically correct and is computable in minimum time	The algorithm is logically correct. But it is not completely precise and the computation time is not minimum.	The algorithm is logically correct. But not fully precise and takes large amount of time to compute	The algorithm is just logically correct	10
2.	Program	The code is well organized, easy to follow and logically correct.	The code is fairly organized.	The code is readable only by someone who knows its logic.	The code is poorly organized.	10
3.	Output	Accurate results have been achieved for all possible inputs and well formatted.	Accurate results have been achieved for the majority of the inputs.	Program produces accurate results but output is not properly formatted.	The program is free of errors but produces inaccurate results.	10
4.	Record	Well kept, strong characterize, standardized and finished within time.	Well kept, attempt is somewhat standardized and finished.	Record is somewhat standardized but not well kept.	Not standardized and well kept also. Some entries are imperfect.	10
Total Marks						40

CRITERIA		MARKS
Performance	40	40
Viva	10	6
Total	50	46

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Door-3	Total
algorithm it ally ct	10
code is ly nized.	10
program e of rs but lucis in rate lts.	10
dardized well kept . Some ies are erfect.	10
al Marks	40

Result

Output obtained and verified successfully

[Signature]
10/10/22

[Signature]
HOD/WE

[Signature]

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROGRAM & OUTPUT

```
import java.io.File Writer;
import java.io.FileReader;
import
java.io.IOException;

class ReadWriteFile{
    public static void
main(String args[]) throws
IOException {
    int ch;
    FileReader fr = new
FileReader("source.txt");
    FileWriter fw = new
FileWriter("destination.tx
t");

    while((ch = fr.read()) !
= -1){

System.out.print((char)ch)
;
fw.write((char)ch);
    }
    fr.close();
    fw.close();
}
```

OUTPUT

Java is a high level programming l
an object oriented langu

Program No: 5

Date: 16/10/22

Java program that read from a file and write to file by handling all file related exceptions

AIM

Write a Java program that read from a file and write to file by handling all file related exceptions.

ALGORITHM / PROCEDURE

Step 1:- Start

Step 2:- import package

File writer

File reader

Exception

Step 3:- Create class Read Writer File which contains main function.

Step 4:- Initialize integer ch.

Step 5:- Create objects

File Reader fr = new FileReader("Sample.txt");

File Writer fw = new FileWriter("new ^{destination} sample.txt");

Step 6:- While ((char) ch = fr.read()) != -1)

Step 6.1:- print((char) ch);

Step 6.2:- fw.write((char) ch);

Step 7:- close objects fr and fw

Step 8:- Stop


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROGRAM & OUTPUT

```
import java.io.File Writer;
import java.io.FileReader;
import
java.io.IOException;


class ReadWriteFile{
    public static void
main(String args[]) throws
    IOException {
        int ch;
        FileReader fr = new
FileReader("source.txt");
        FileWriter fw = new
FileWriter("destination.tx
t");

        while((ch = fr.read()) !
            = -1){

            System.out.print((char)ch)
                ;
            fw.write((char)ch);
            }
            fr.close();
            fw.close();
        }
    }
```

OUTPUT

Java is a high level programming language. It is
an object oriented language

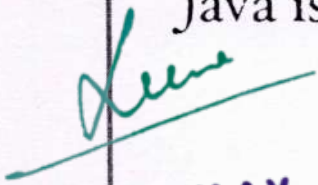
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

SCORING SHEET

No.	Performance criteria	Excellent-10	Good-8	Satisfactory-5	Poor-3	Total
1.	Algorithm / Procedure	The algorithm is precise, logically correct and is computable in minimum time	The algorithm is logically correct. But it is not completely precise and the computation time is not minimum.	The algorithm is logically correct. But not fully precise and takes large amount of time to compute	The algorithm is just logically correct	10
2.	Program	The code is well organized, easy to follow and logically correct.	The code is fairly organized.	The code is readable only by someone who knows its logic.	The code is poorly organized.	10
3.	Output	Accurate results have been achieved for all possible inputs and well formatted.	Accurate results have been achieved for the majority of the inputs.	Program produces accurate results but output is not properly formatted.	The program is free of errors but produces in accurate results.	10
4.	Record	Well kept, strong characterize, standardized and finished within time.	Well kept, attempt is somewhat standardized and finished.	Record is somewhat standardized but not well kept.	Not standardized and well kept also. Some entries are imperfect.	10
					Total Marks	40

CRITERIA		MARKS
Performance	40	40
Viva	10	7
Total	50	47

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

-3	Total
rithm	10
is	10
d.	10
ram	10
t	
in	
ized	
kept	10
ne	
e	
t.	
arks	40

Result

Output obtained and verified successfully

[Signature]
21/10/22

[Signature]
HOD/WE

[Signature]

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

PROGRAM & OUTPUT

PROGRAM :-

```
import java.util.*;

class StringTokenizerDemo
{
    public static void main(String args[])
    {
        int n, sum=0;
        Scanner scan = new Scanner(System.in);
        System.out.println("Enter integers with one space gap :");

        String s = scan.nextLine();
        StringTokenizer st = new StringTokenizer(s, " ");

        while(st.hasMoreTokens())
        {
            String temp = st.nextToken();
            n = Integer.parseInt(temp);
            System.out.println(n);
            sum += n;
        }
        System.out.println("Sum of integers : " + sum);
    }
}
```

OUTPUT :-

Enter integers with one space gap :

159

Sum of integers : 15

Program No: 6

Date: 26/10/22

Java Program that reads a line of integers, and then displays each integer, and the sum of all the integers

AIM

Write a Java program that reads a line of integers, and then displays each integer, and the sum of all the integers (Use String Tokenizer class of java.util).

ALGORITHM / PROCEDURE

Step 1:- Start

Step 2:- Import scanner class

Step 3:- Create class string to tokenizer demo which contain main function

Step 4:- Initialize integer n, sum=0

Step 5:- Create object sc

Scanner sc = new Scanner(System.in);

Step 6:- print Enter integer with one space gap

Step 7:- Read string to strings

Step 8:- Create object st;

String to tokenizer st = new String to tokenizer(st);

Step 9:- While (st has more to tokenize), else go to step 14

Step 10:- String temp = st.next token()

Step 11:- n = (convert to integer type(temp);

Step 12:- print(n);

Step 13:- sum = sum + n, go to step 9

Step 14:- print("Sum of integer is")

Step 15:- close object

Step 16:- Stop

Dr. EENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

SCORING SHEET

No.	Performance criteria	Excellent-10	Good-8	Satisfactory-5	Poor-3	Total
1.	Algorithm / Procedure	The algorithm is precise, logically correct and is computable in minimum time	The algorithm is logically correct. But it is not completely precise and the computation time is not minimum.	The algorithm is logically correct. But not fully precise and takes large amount of time to compute	The algorithm is just logically correct	10
2.	Program	The code is well organized, easy to follow and logically correct.	The code is fairly organized.	The code is readable only by someone who knows its logic.	The code is poorly organized.	10
3.	Output	Accurate results have been achieved for all possible inputs and well formatted.	Accurate results have been achieved for the majority of the inputs.	Program produces accurate results but output is not properly formatted.	The program is free of errors but produces in accurate results.	10
4.	Record	Well kept, strong characterize, standardized and finished within time.	Well kept, attempt is somewhat standardized and finished.	Record is somewhat standardized but not well kept.	Not standardized and well kept also. Some entries are imperfect.	10
Total Marks						40

CRITERIA		MARKS
Performance	40	40
Viva	10	6
Total	50	46

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

-3	Total
orithm	10
e is	10
d.	10
gram f at s in :	10
lized l kept me re ct.	10
larks	40

Result

Output obtained and verified successfully

[Signature]
26/10/22

[Signature]
HOD/WE

[Signature]

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

PROGRAM & OUTPUT

PROGRAM :-

```
import java.util.Scanner;

class exception
{
    public static void main(String args[])
    {
        Scanner sc = new Scanner(System.in);
        try{
            System.out.println("Program to perform Division");
            System.out.print("Enter Number-1:");
            int a = sc.nextInt();
            System.out.print("Enter Number-2:");
            int b = sc.nextInt();
            int c = a/b;
            System.out.println("Result="+c);
        }
        catch(ArithmeticException e)
        {
            System.out.println(e.getMessage());
        }
        finally{
            System.out.println("End of Operation");
        }
    }
}
```


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Program No: 7

Date: 26/10/22


Java Program that shows the usage of Try, Catch, Throws and Finally

AIM

Write a Java program that shows the usage of try, catch, throws and finally.

ALGORITHM / PROCEDURE

- Step 1:- Start
- Step 2:- Import Scanner from util class
- Step 3:- Initiate class exception
- Step 4:- Initiate main function
- Step 5:- Initiate object scan of scanner class
- Step 6:- With try keyword initiate and begin code block to be begin executed.
- Step 6.1:- Read the two number and store in variable a and b
- Step 6.2:- divide a by b and store result in variable c and print result
- Step 7:- With catch keyword look for arithmetic exception and if found store in variable c
- Step 7.1:- In case of exception display message with finally keyword getMessage() method
- Step 8:- With finally keyword display message
• End of program to be executed at end unconditionally
- Step 9:- close exception class
- Step 10:- Stop

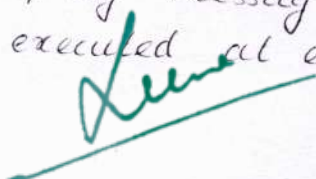
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

OUTPUT :-

Program to perform Division

Enter Number-1:10

Enter Number-2:5

Result =2

End of Operation


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR


SCORING SHEET

No.	Performance criteria	Excellent-10	Good-8	Satisfactory-5	Poor-3	Total
1.	Algorithm / Procedure	The algorithm is precise, logically correct and is computable in minimum time	The algorithm is logically correct. But it is not completely precise and the computation time is not minimum.	The algorithm is logically correct. But not fully precise and takes large amount of time to compute	The algorithm is just logically correct	10
2.	Program	The code is well organized, easy to follow and logically correct.	The code is fairly organized.	The code is readable only by someone who knows its logic.	The code is poorly organized.	10
3.	Output	Accurate results have been achieved for all possible inputs and well formatted.	Accurate results have been achieved for the majority of the inputs.	Program produces accurate results but output is not properly formatted.	The program is free of errors but produces inaccurate results.	10
4.	Record	Well kept, strong characterize, standardized and finished within time.	Well kept, attempt is somewhat standardized and finished.	Record is somewhat standardized but not well kept.	Not standardized and well kept also. Some entries are imperfect.	10
Total Marks						40

CRITERIA		MARKS
Performance	40	40
Viva	10	6
Total	50	46


Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PAYYANUR, KANNUR

Result

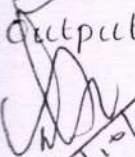Output

 26/10/17

	Total
im	10
	10
m	10
l	
sd ept	10
'ks	40

Result

Output obtained and verified successfully.

[Signature]
26/10/22

[Signature]
HOD/WE

[Signature]
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROGRAM & OUTPUT

PROGRAM :-

```
class Display
{
    public synchronized void print(String msg)
    {
        System.out.print("[ "+msg);
        try
        {
            Thread.sleep(1000);
        }
        catch(Exception e)
        {
            System.out.println(e.getMessage());
        }
        System.out.println("]");
    }
}

class SyncThread extends Thread
{
    private Display d;
    private String msg;
    public SyncThread(Display d,String msg)
    {
        this.d=d;
        this.msg=msg;
    }
    public void run()
    {
        d.print(msg);
    }
}

class Test2
{
    public static void main(String[] args)
    {
        Display d=new Display();
        SyncThread t1=new SyncThread(d,"Hello");
        SyncThread t2=new SyncThread(d,"World");
        t1.start();
        t2.start();
    }
}
```

OUTPUT :-

[Hello]

[World]

AI

AL

Slc

Slc

Slc

Step

Slc

Step

Step

Step

Step

Step

Step

Step

Program No: 8

Date: 27/10/22

Java Program that shows Thread Synchronization

AIM

Write a Java Program that shows Thread Synchronization

ALGORITHM / PROCEDURE

- Step 1:- start
- Step 2:- Define a class Display
- Step 3:- Define a synchronized public function print taking a string parameter message that print the message.
- Step 4:- Within Try block call sleep method of Thread class with parameter as 1000
- Step 5:- catch only exception and return the error message.
- Step 6:- close Display class
- Step 7:- Define a class syncthread inheriting Thread class
- Step 8:- Initialize private objects display it and string message.
- Step 9:- Define a constructor with Display at and string message as parameter and assign their values to defined in step 8.
- Step 10:- Define a method run to print message
- Step 11:- close syncthread class
- Step 12:- Define class Test 2

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Step 13:- Define main function and include instance of display t₁ and t₂ of syncthread with , Hello and d world as parameter respectively.

Step 14:- call start method of t₁ and t₂ respectively

Step 15:- close class Test 2

Step 16:- Stop



Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

SCORING SHEET

No.	Performance criteria	Excellent-10	Good-8	Satisfactory-5	Poor-3	Total
1.	Algorithm / Procedure	The algorithm is precise, logically correct and is computable in minimum time.	The algorithm is logically correct. But it is not completely precise and the computation time is not minimum.	The algorithm is logically correct. But not fully precise and takes large amount of time to compute	The algorithm is just logically correct	10
2.	Program	The code is well organized, easy to follow and logically correct.	The code is fairly organized.	The code is readable only by someone who knows its logic.	The code is poorly organized.	10
3.	Output	Accurate results have been achieved for all possible inputs and well formatted.	Accurate results have been achieved for the majority of the inputs.	Program produces accurate results but output is not properly formatted.	The program is free of errors but produces in accurate results.	10
4.	Record	Well kept, strong characterize, standardized and finished within time.	Well kept, attempt is somewhat standardized and finished.	Record is somewhat standardized but not well kept.	Not standardized and well kept also. Some entries are imperfect.	10
Total Marks						40

CRITERIA		MARKS
Performance	40	40
Viva	10	7
Total	50	47

Dr. LEENA A V
PRINCIPAL

**SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR**

Total
1
10
10
10
10
40

Result

Output obtained and verified successfully.

[Signature]
27/10/22

[Signature]
HOD/USE

[Signature]
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROGRAM & OUTPUT

PROGRAM:-

```
import javax.swing.*;
import java.awt.event.*;
class Calculator extends JFrame implements ActionListener{
private JTextField t1;
private JButton b1;
private JButton b2;
private JButton b3;
private JButton b4;
private JButton b5;
private JButton b6;
private JButton b7;

private JButton b8;
private JButton b9;
private JButton b10;
private JButton b11;
private JButton b12;
private JButton b13;
private JButton b14;
private JButton b15;
private JButton b16;
private Integer res;
private String operation;
public Calculator()
{
setLayout(null);
setSize(640,480);
t1 = new JTextField();
t1.setBounds(100,100,200,30);
b1 = new JButton("1");
b1.setBounds(100,140,50,30);
b2 = new JButton("2");
b2.setBounds(150,140,50,30);
b3 = new JButton("3");
b3.setBounds(200,140,50,30);
b4 = new JButton("+");
b4.setBounds(250,140,50,30);
// Third Row
b5 = new JButton("4");
b5.setBounds(100,170,50,30);
b6 = new JButton("5");
b6.setBounds(150,170,50,30);
b7 = new JButton("6");
b7.setBounds(200,170,50,30);
b8 = new JButton("-");
b8.setBounds(250,170,50,30);
// Fourth Row
b9 = new JButton("7");
b9.setBounds(100,200,50,30);
b10 = new JButton("8");
```


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Progra

Date:

AIM

ALGO

1. Sta
2. Cre
set
key
of
3. No.
mc
our
4. Cr.
we
5. At
act
Att
the
6. Imj
our
Acti
7. Reg
8. In

PROGRAM & OUTPUT

```
b10.setBounds(150,200,50,30);
b11 = new JButton("9");
b11.setBounds(200,200,50,30);
b12 = new JButton("*");
b12.setBounds(250,200,50,30);
// Fourth Row
b13 = new JButton("/");
b13.setBounds(100,230,50,30);
b14 = new JButton("%");
b14.setBounds(150,230,50,30);
b15 = new JButton("=");
b15.setBounds(200,230,50,30);
b16 = new JButton("C");
b16.setBounds(250,230,50,30);

add(t1);add(b1);add(b2);
add(b3);add(b4);add(b5);
add(b6);add(b7);add(b8);
add(b9);add(b10);add(b11);
add(b12);add(b13);add(b14);
add(b15);add(b16);
b1.addActionListener(this);b2.addActionListener(this);
b3.addActionListener(this);b4.addActionListener(this);
b5.addActionListener(this);b6.addActionListener(this);
b7.addActionListener(this);b8.addActionListener(this);
b9.addActionListener(this);b10.addActionListener(this);
b11.addActionListener(this);b12.addActionListener(this);
b13.addActionListener(this);b14.addActionListener(this);
b15.addActionListener(this);b16.addActionListener(this);
}
public void doAction(String op)
{
    if(operation == null)
    {
        operation = op;
        res = Integer.parseInt(t1.getText());
        t1.setText("");
    }
    else{
        switch(operation)
        {
            case "+": res = res + Integer.parseInt(t1.getText());

            break;

            case "-": res = res - Integer.parseInt(t1.getText());

            break;
            case "/": try{

            if(t1.getText().equals("0"))
```

Progi

Date:

AIM

ALGOI

1. Sta
2. Cre
- Set
- lay
- ol
3. Noa
- ma
- our
4. Cre
- we
5. Aft
- act
- Atte
- the
6. Im,
- our
- Acti
7. Reg
8. In


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Program No: 9

Date: 3/11/22

Java Program that works as a Simple Calculator

AIM

Write a Java program that works as a simple calculator. Arrange Buttons for digits and the + - * % operations properly. Add a text field to display the result. Handle any possible exceptions like divide by zero. Use Java Swing.

ALGORITHM / PROCEDURE

1. Start
2. Create an object of the JFrame class and set some of its properties like its title layout property etc. using the method of JFrame class
3. Now create another ^{java} class and inside the main method just create an object of our calculator class
4. Create object of all the components that we want to add.
5. After creating object of all the components set some of the properties of each component. After setting their properties add them to the frame using add() method.
6. Implement the ActionListener interface in our class and override its method ~~ActionListener~~ actionPerformed() in that class.
7. Register ActionListener for all the components.
8. Enter values to perform operations.

Dr. KEENA A V
PRINCIPAL

SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR


```

{
throw new

ArithmeticException("Divide by Zero");

}
res = res / Integer.parseInt(t1.getText());
}
catch(ArithmeticException e)
{
t1.setText(e.getMessage());
operation = null;
res = 0;
}
break;

case "*": res = res * Integer.parseInt(t1.getText());

break;

case "%": res = res % Integer.parseInt(t1.getText());

break;

}
if(op.equals("=")){
t1.setText(res.toString());

res = 0;
operation = null;
}
else{
operation = op;
t1.setText("");
}
}

public void actionPerformed(ActionEvent e){
if(e.getSource()== b1)
t1.setText(t1.getText()+"1");
else if(e.getSource()== b2)
t1.setText(t1.getText()+"2");
else if(e.getSource()== b3)
t1.setText(t1.getText()+"3");
else if(e.getSource()== b5)
t1.setText(t1.getText()+"4");
else if(e.getSource()== b6)
t1.setText(t1.getText()+"5");
else if(e.getSource()== b7)
t1.setText(t1.getText()+"6");

```


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

```

else if(e.getSource()== b9)
t1.setText(t1.getText()+"7");
else if(e.getSource()== b10)
t1.setText(t1.getText()+"8");
else if(e.getSource()== b11)
t1.setText(t1.getText()+"9");
else if(e.getSource()== b16){
t1.setText("");
res =0;
operation = null;
}
else if(e.getSource()== b4){
doAction("+");
}
else if(e.getSource()== b8)
doAction("-");
else if(e.getSource()== b12)
doAction("*");
else if(e.getSource()== b13)
doAction("/");
else if(e.getSource()== b14)
doAction("%");
else if(e.getSource()== b15)
doAction("=");

}
public static void main(String args[]){
new Calculator().setVisible(true);
}

}

```

calce
g sto

✓

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR


calculator
q. stop


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

SCORING SHEET

No.	Performance criteria	Excellent-10	Good-8	Satisfactory-5	Poor-3	Total
1.	Algorithm / Procedure	The algorithm is precise, logically correct and is computable in minimum time	The algorithm is logically correct. But it is not completely precise and the computation time is not minimum.	The algorithm is logically correct. But not fully precise and takes large amount of time to compute	The algorithm is just logically correct	10
2.	Program	The code is well organized, easy to follow and logically correct.	The code is fairly organized.	The code is readable only by someone who knows its logic.	The code is poorly organized.	10
3.	Output	Accurate results have been achieved for all possible inputs and well formatted.	Accurate results have been achieved for the majority of the inputs.	Program produces accurate results but output is not properly formatted.	The program is free of errors but produces in accurate results.	10
4.	Record	Well kept, strong characterize, standardized and finished within time.	Well kept, attempt is somewhat standardized and finished.	Record is somewhat standardized but not well kept.	Not standardized and well kept also. Some entries are imperfect.	10
Total Marks						40

CRITERIA		MARKS
Performance	40	40
Viva	10	5
Total	50	45

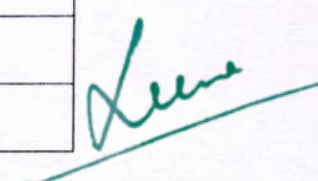
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

Result

O.K.
 V.
 4.
 3

	Total
hm	10
s	10
m	10
ed ept	10
ks	40

Result

Output obtained and verified successfully

[Signature]
3/1/22

[Signature]
HOD/WE

[Signature]

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

PROGRAM & OUTPUT

PROGRAM :-

```
import javax.swing.*;
import java.awt.*;
import java.awt.event.*;

class TrafficLight extends JPanel implements ActionListener{
    private JRadioButton r1;
    private JRadioButton r2;
    private JRadioButton r3;

    private Color red_c;
    private Color green_c;
    private Color orange_c;

    public TrafficLight(){
        setBounds(0,0,640,480);
        r1 = new JRadioButton("Red");
        r2 = new JRadioButton("Green");
        r3 = new JRadioButton("Orange");

        ButtonGroup group = new ButtonGroup();
        r1.setSelected(true);
        group.add(r1);
        group.add(r2);
        group.add(r3);

        add(r1);
        add(r2);
        add(r3);

        red_c = Color.red;
        green_c = getBackground();
        orange_c = getBackground();

        r1.addActionListener(this);
        r2.addActionListener(this);
        r3.addActionListener(this);
    }

    public void actionPerformed(ActionEvent e){
        if(r1.isSelected()){
            red_c = Color.red;
            green_c = getBackground();
            orange_c = getBackground();
        }
        else if(r2.isSelected()){
            green_c = Color.green;
            red_c = getBackground();
            orange_c = getBackground();
        }
        else if(r3.isSelected()){

```

Program

Date: 1/

AIM

Write a
one of the
turned on
starts.

ALGORITHM

Step 1:-

Step 2:-

Step 3:-

Step 4:-

Step 5:-

Step 6:-

Step 7:-

Step 8:-

Step 9:-

Step 10:-

Step 11:-


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Program No: 10

Date: 10/11/22

Java Program that simulates a Traffic Light

AIM

Write a Java program that simulates a traffic light. The program lets the user select one of three lights: red, yellow, or green. When a radio button is selected, the light is turned on, and only one light can be on at a time. No light is on when the program starts.

ALGORITHM / PROCEDURE

- Step 1: Start
- Step 2: import ^{package} String and awt
- Step 3: define a class TrafficLight extends JPanel implements ActionListener
- Step 4: declare parent private object instance of r_1 , r_2 and r_3 color red, green and orange
- Step 5: Define a constructor and call setBounds function with parameter (0,0,600,750)
- Step 6: In it, define object r_1 , r_2 and r_3 as instance of JRadioButton Red Green and orange parameter
- Step 7: Create instance of Button Group and group add r_1 , r_2 and r_3 and add r_1 , r_2 and r_3
- Step 8: set color red, green and getBackground for selected color
- Step 9: Create paint component function sets parameter (Graphics g)
- Step 10: draw oval and set the co-ordinates
- Step 11: Create a class Test3 in that def main method

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

```

        orange_c = Color.orange;
        green_c = getBackground();
        red_c = getBackground();
    }
    repaint();
}

public void paintComponent(Graphics g){
    super.paintComponent(g);

    g.drawOval(50,50,50,50);
    g.drawOval(50,110,50,50);
    g.drawOval(50,170,50,50);

    g.setColor(red_c);
    g.fillOval(50,50,50,50);
    g.setColor(orange_c);
    g.fillOval(50,110,50,50);
    g.setColor(green_c);
    g.fillOval(50,170,50,50);
}

}

class Traffic{
    public static void main(String args[]){
        JFrame f1 = new JFrame();
        f1.setVisible(true);
        f1.setSize(600,480);
        f1.setLayout(null);
        TrafficLight t = new TrafficLight();
        f1.add(t);
    }
}


```

Step

Step

Step

Step

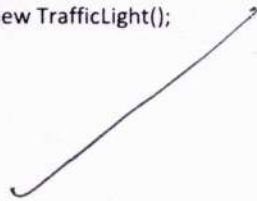

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Step 12: Create an object for JFrame-11 and set
the visibility, size and layout as null
Step 13: Create another object for Traffic Light
Step 14 - Call f1 add(L)
Step 15: Stop


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

SCORING SHEET

No.	Performance criteria	Excellent-10	Good-8	Satisfactory-5	Poor-3	Total
1.	Algorithm / Procedure	The algorithm is precise, logically correct and is computable in minimum time	The algorithm is logically correct. But it is not completely precise and the computation time is not minimum.	The algorithm is logically correct. But not fully precise and takes large amount of time to compute	The algorithm is just logically correct	10
2.	Program	The code is well organized, easy to follow and logically correct.	The code is fairly organized.	The code is readable only by someone who knows its logic.	The code is poorly organized.	10
3.	Output	Accurate results have been achieved for all possible inputs and well formatted.	Accurate results have been achieved for the majority of the inputs.	Program produces accurate results but output is not properly formatted.	The program is free of errors but produces in accurate results.	10
4.	Record	Well kept, strong characterize, standardized and finished within time.	Well kept, attempt is somewhat standardized and finished.	Record is somewhat standardized but not well kept.	Not standardized and well kept also. Some entries are imperfect.	10
Total Marks						40

CRITERIA		MARKS
Performance	40	40
Viva	10	7
Total	50	47

Dr. LEENA A V
PRINCIPAL

**SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR**

Result


04/6/1


[Signature]

or-3	Total
orithm y	10
e is d.	10
ram t in	10
ed ept e	10
ks	40

Result

Output obtained and verified successfully

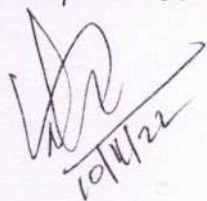
10/11/22

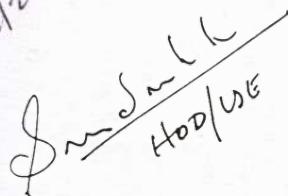
HOD/USE



Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

CYCLE - 3



Dr. LEENA A V
PRINCIPAL
SREE MARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROGRAM & OUTPUT

PROGRAM :-

```
import java.util.Scanner;
class LinkedList{
    private Node head;
    class Node{
        private int data;
        private Node right;
        private Node left;
        public Node(int data){
            this.data = data;
            this.right = right;
            this.left = left;
        }
    }

    public void insert(int data){
        Node temp = new Node(data);
        if(head == null)
            head = temp;
        else{
            Node ptr = head;
            while(ptr.right != null)
                ptr = ptr.right;
            ptr.right = temp;
            temp.left = ptr;
        }
    }

    public void delete(){
        int x = head.data;
        head = head.right;
        head.left = null;
        System.out.println("Element " + x + " deleted.");
    }

    public void display(){
        if(head == null)
            System.out.println("List Empty");
        else{
            Node ptr = head;
            while (ptr != null){
                System.out.print(ptr.data + " ");
                ptr = ptr.right;
            }
            System.out.println();
        }
    }
}

class LinkdLst{
    public static void main(String args[]){
        LinkedList list = new LinkedList();
    }
}
```


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

AL

AL

1

2

2.1

2.1.1

2.2

2.2

2.2

2.2

2.2

2.2.3

2.2

2.3

Program No: 11

Date: 17/11/22

Java Program for Doubly Linked List Operations

AIM

Write a Java program for the following:

1. Create a doubly linked list of elements.
2. Delete a given element from the above list.
3. Display the contents of the list after deletion

ALGORITHM / PROCEDURE

1. Start
2. Define a class LinkedList and declare private instance of Node head
 - 2.1: Define class Node declare private int data and private instance of node left and right
 - 2.1.1: Define constructor receiving data as parameter and assign data i.e., this.data and null as this.left and this.right
 - 2.2: Define function insert taking data as parameter create an instance of node with data as parameter named temp.
 - 2.2.1: If head == null else goto 2.2.2
 - 2.2.1.1: assign temp to head
 - 2.2.2: Define Node instance ptr and assign value as head
 - 2.2.3: With ~~loop~~ indicated using while, check if ptr.right != null. If true goto 2.2.3.1
 - 2.2.3.1: set ptr = ptr.right
 - 2.2.4: Set ptr.right = temp and
 - 2.3: Define function delete define

Leena
DR. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR


```

Scanner sc = new Scanner(System.in);
String ch = "";

System.out.println("1.Insert at end\n2.delete from front\n3.Display\n4.Exit");
while(!ch.equals("4")){
    System.out.print("\n\nEnter choice:");
    ch = sc.nextLine();
    switch(ch){
        case "1":
            System.out.print("Enter a number: ");
            int data = sc.nextInt();
            sc.nextLine();
            list.insert(data);
            System.out.print("Inserted successfully");
            break;
        case "2":
            list.delete();
            break;
        case "3":
            list.display();
            break;
        case "4":break;
        default: System.out.println("Invalid choice");
    }
}
}
}

```

OUTPUT :-

```

1. Insert at end
2. delete from front
3. Display
4. Exit
Enter choice:1
Enter a number: 5
Inserted successfully
Enter choice: 1
Enter a number: 6
Inserted successfully
Enter choice: 1
Enter a number: 7
Inserted successfully
Enter choice:3
5
6
Enter choice:2
Element 5 deleted.
Enter choice:3
6
Enter choice:5
Invalid choice
Enter choice:4

```

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

4.Exit");

int x = head.data, head = head.right and
head.left = null

2.4: Define function display if head == null,
print empty also goto 2.4.1

2.4.1: Define Node ptr = head and with while
loop if ptr != null print ptr.data set
ptr = ptr.right

2.5: Define class Test4 and in main function
create instance of linked list, Scanner
sc and define string choice = ""

2.6: With while loop initiated by condition
!choice.equals(4) goto 2.6.1

2.6.1: Print 1. insert at End 2. Delete from front
3. Display 4. Exit

2.6.2: read input into int choice using scanner

2.6.3: use switch to check value of choice

2.6.3.1: if choice is 1

2.6.3.1.1: Read data to be inserted

2.6.3.1.2: call insert method of list with the data
as parameter and break

2.6.3.2: if choice is 2

2.6.3.2.1: call delete method of list and break

2.6.3.4: if choice is 3
call display method of list and break

2.6.3.5: if choice is 4 : break

2.6.3.6: define default case

2.6.3.6.1: print invalid choice

2.7: close class

3: stop


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

SCORING SHEET

No.	Performance criteria	Excellent-10	Good-8	Satisfactory-5	Poor-3	Total
1.	Algorithm / Procedure	The algorithm is precise, logically correct and is computable in minimum time	The algorithm is logically correct. But it is not completely precise and the computation time is not minimum.	The algorithm is logically correct. But not fully precise and takes large amount of time to compute	The algorithm is just logically correct	10
2.	Program	The code is well organized, easy to follow and logically correct.	The code is fairly organized.	The code is readable only by someone who knows its logic.	The code is poorly organized.	10
3.	Output	Accurate results have been achieved for all possible inputs and well formatted.	Accurate results have been achieved for the majority of the inputs.	Program produces accurate results but output is not properly formatted.	The program is free of errors but produces inaccurate results.	10
4.	Record	Well kept, strong characterize, standardized and finished within time.	Well kept, attempt is somewhat standardized and finished.	Record is somewhat standardized but not well kept.	Not standardized and well kept also. Some entries are imperfect.	10
Total Marks						40

CRITERIA		MARKS
Performance	40	40
Viva	10	6
Total	50	46

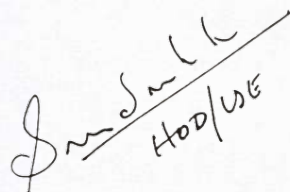

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

	Total
im	10
	10
n	10
i ot	10
is	40

Result

Output obtained and verified successfully


17/11/22


HOD/WE


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROGRAM & OUTPUT

PROGRAM :-

```
import java.io.*;

public class StringQuickSort{
    String names[];
    int length;
    public static void main(String args[]){
        StringQuickSort obj = new StringQuickSort();
        String stringList[] =
{"Raja","Gouthu","Ram","Goutham","Honey","Heyaanch","Hello"};
        obj.sort(stringList);

        for(String i : stringList){
            System.out.print(i);
            System.out.print(" ");
        }
        System.out.println("");
    }

    public void sort(String array[]){
        if(array == null || array.length == 0)
            return;
        this.names = array;
        this.length = array.length;
        quicksort(0,length-1);
    }

    public void quicksort(int lower, int higher){
        int i = lower;
        int j = higher;
        String pivot = this.names[lower + (higher-lower)/2];
        while(i<=j){
            while(this.names[i].compareToIgnoreCase(pivot) < 0)
                i++;
            while(this.names[j].compareToIgnoreCase(pivot)>0)
                j--;
            if(i<=j){
                exchangeNames(i,j);
                i++;
                j--;
            }
            if(lower<j)
                quicksort(lower,j);
            if(i<higher)
                quicksort(i,higher);
        }
    }

    public void exchangeNames(int i, int j){
        String temp = this.names[i];
        this.names[i] = this.names[j];
```


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

Program No: 12

Date: 30/11/22

Java Program That Implements Quick Sort Algorithm

AIM

Write a Java program that implements Quick sort algorithm for sorting a list of names in ascending order.

ALGORITHM / PROCEDURE


- Step 1: start
- Step 2: Define a class Quicksort on String and declare String name[] and int length
- Step 2.1: Define main function and initiate instance of QuicksortOnString obj create String stringList with list of String to sort
- Step 2.2: call sort method of obj with string list as parameter
- Step 2.3: With for loop initiated by string i loop through elements in stringList.
- 2.3.1: print element i
- Step 2.4: define function sort reading a String array as parameter.
- 2.4.1: if array == null as array length = 0 → return
- 2.4.2 set this name as array this length as array length call function quicksort with 0 and length-1 as parameter
- Step 2.5 Define function quicksort with lowerindex and higherindex as parameter
- 2.5.1: int i as lower index, int j as higher index and String pivot as name[lowerindex + (higherindex - lowerindex)/2]

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR



```
        this.names[j] = temp;
    }
}
```

OUTPUT :-

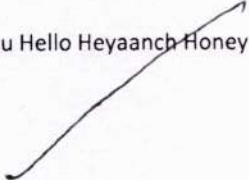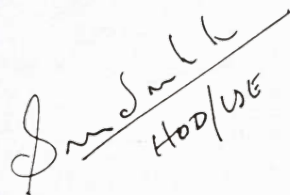Goutham Gouthu Hello Heyaanch Honey Raja Ram



2.5.2: with while loop initiated by $i < j$
 2.5.2.1 with while loop initiated by this.name[i].
 compare case (pivot) < 0
 2.5.2.1.1: increment i by 1
 2.5.2.2: with while loop initiated by this.name[i].
 compare case (pivot) > 0.
 2.5.2.3: decrement j by 1
 2.5.2.3.1 if $i < j$; call exchange name(i, j); i++, j--
 2.5.2.4: if lowerindex < j $\Rightarrow$ quicksort(lowerindex, j)
 2.5.2.5: if $i <$ higherindex $\Rightarrow$ quicksort(i, higherindex)
 2.6: Define function ExchangeName Taking int i
 and int j as parameters
 2.6.1: declare string temp and assign this.name[i]
 2.6.2: assign this.name[i] as this.name[j]
 2.6.3: assign this.name[j] as temp
 2.7: close class Quicksort on string
 3:- Stop


 Hod/USE


Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PATTANUR, KANNUR

VIVA QUESTIONS

1. What is OOPS?
2. What are the main features of OOPs?
3. What are packages?
4. List out any three built in packages.
5. What are data types?
6. List out different types of operators.
7. Syntax for conditional operators.
8. Define control statements.
9. Difference between do-while and while loop statements
10. Flowchart - Nested if else statements.
11. List out the Java Buzzwords.
12. Write basic concepts of OOPs
13. What is a class?
14. Differentiate Super class and Sub class.
15. What is an Object?
16. What is encapsulation?
17. What is abstract class?
18. Difference between abstract class and interface.
19. What is inheritance?
20. What is multi-level inheritance?
21. What is a file?
22. List out the file operations in Java.
23. Differentiate byte stream and character stream.
24. What are object stream.
25. What is a String?
26. Difference between Strings & String Buffer.
27. List some File handling functions.
28. What is String Tokenzier?

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

29
30
31
32
33
34
35
36
37
38
39
40
41
42
43
44
45
46
47
48
49
50
51
52
53
54
55
56
57

29. What are tokens?
30. What are exceptions?
31. What is an error?
32. Types of exceptions in Java
33. What is Exception Handling?
34. Difference between throws and throw keywords.
35. Use of finally keywords.
36. Explain threads in java.
37. What is the process called thread synchronization.
38. Use of synchronized keyword in threads.
39. Life cycle of threads.
40. Example for occurrence of exceptions.
41. What is an Event?
42. Explain Delegation Event Model.
43. How events are handled in Java?
44. List out some source events and its corresponding listeners.
45. Explain the term Listener.
46. What is Swing in Java
47. List out some swing packages.
48. What is an Applet
49. Difference between AWT & Swing.
50. What is JDBC? Explain 5 steps in connecting JDBC.
51. What is a linked list?
52. Briefly explain quick sort?
53. Difference between linked list and doubly linked list.
54. Difference between packages and interface.
55. How multiple inheritance implemented using interface.
56. Differentiate stack, queue, linked list.
57. What is an array?

Sanjith
HOD/ISE

Leena


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

Completed & Certified


8/12/22




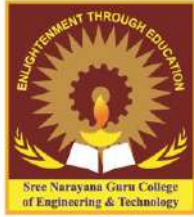Dr. LEENA A. V.
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY, PAYYANUR
KANNUR



Sree Narayana Guru College of Engineering & Technology

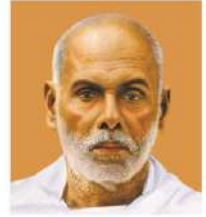CHALAKKODE P.O., KOROM, PAYYANUR, KANNUR-670 307



DEPARTMENT OF ELECTRONICS AND COMMUNICATIONS ENGINEERING

**SREE NARAYANA GURU
COLLEGE OF ENGINEERING & TECHNOLOGY
PAYYANUR - 670 307**



CERTIFICATE

Name.....JISHNU GERISH.....
Semester.....S4..... Branch.....ECE.....
Roll No.....2..... Uni. Reg. No.....SNC21EC002.....

Certified that this is a Bonafide Record of the work done in the ECL 202 ANALOG CIRCUITS AND
SIMULATION LAB of Sree Narayana Guru College of Engineering & Technology, Payyanur by
JISHNU GERISH

Place : PAYYANUR

Date : 10/07/23

[Signature]
17/7/23
Internal Examiner

[Signature]
HOD, ECE

[Signature]
10/07/23
Staff Member Incharge
Department of ECE
SNGCET, Payyanur

[Signature]
17/8/23
External Examiner

[Signature]
Dr. LEENA A. V.
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY, PAYYANUR
KANNUR

INDEX

Sr. No.	Name of the Experiment	Page No.	Date of Experiment	Date of Submission	Remarks
1.	RC INTEGRATOR AND DIFFERENTIATOR	1-9	29/3/23		10/4/23
2.	CLIPPING AND CLAMPING CIRCUIT	10-18	12/4/23		15/6/23
3.	RC COUPLED AMPLIFIER	19-24	17/6/23		21/06/23
4.	RC PHASE SHIFT OSCILLATOR	25-27	16/6/23		21/06/23
5.	CASCADE AMPLIFIER	28-30	15/6/23		21/06/23
6.	SERIES VOLTAGE REGULATOR (LINE AND LOAD)	31-33	21/6/23		10/7/23
	PART B : SIMULATION EXPERIMENTS	34	21/6/23		
	FAMILIARIZATION OF PSPICE SIMULATION SOFTWARE	35-39	21/6/23		10/7/23
1.	RC DIFFERENTIATOR AND INTEGRATING CIRCUITS	40-42	21/6/23		10/7/23
2.	CLIPPING CIRCUITS	43-44			10/7/23
	CLAMPING CIRCUITS	45-46	21/6/23		10/7/23
3.	RC COUPLED AMPLIFIER	47-48	24/6/23		10/7/23
4.	RC PHASE SHIFT OSCILLATOR	49-50	24/6/23		10/7/23
5.	CASCADE AMPLIFIER	51-52	24/6/23		10/7/23
6.	SERIES VOLTAGE REGULATOR	53-56	24/6/23		10/7/23
	Completed all experiments				
	Dr. LEENA A. V. PRINCIPAL				
	SVKM'S DEVA GURU COLLEGE OF ENGINEERING & TECHNOLOGY, PANYAMUR				
	Verify by				
	Thou...				
	Assistant Professor				
	Department of ECE				
	SNGCET, P...				

RC INTEGRATOR AND DIFFERENTIATOR

AIM:

1. To design and set up a RC integrator circuit. RC differentiator circuit and study the response to square wave.
2. To observe the response of the designed circuit for the given square waveform for $RC \ll T$, $RC = T$, $RC \gg T$.


COMPONENTS AND EQUIPMENTS REQUIRED:-

Resistor 50 k Ω	1 No
Capacitor 22 μ F, 0.1 μ F, 0.22 μ F, 1 μ F	1 No
Function generator	1 No
CRO	1 No
Bread Board	1 No
Connecting wires	1 No

THEORY:


An RC integrator is constituted by a resistance in series and a capacitor parallel with the output. This circuit produces an output voltage that is proportional to the integral of the input. When the time constant is very large in comparison with the time required for the input signal to change under this condition the voltage drop across C will be very small in comparison with the drop across R. The current is V_{in}/R almost, all current appears across R.

Integration

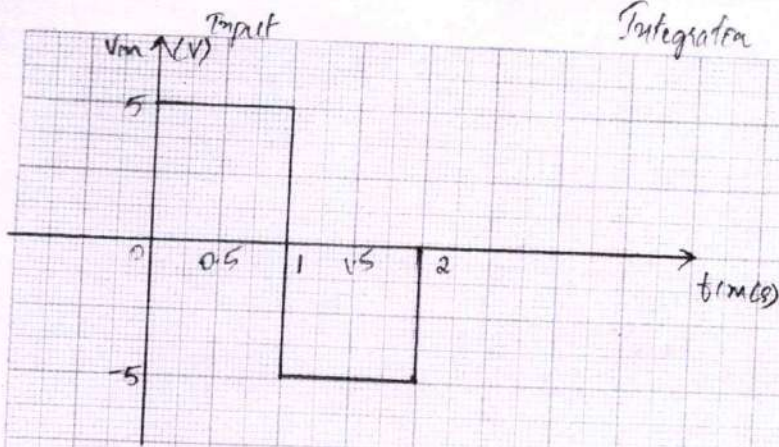


Scale

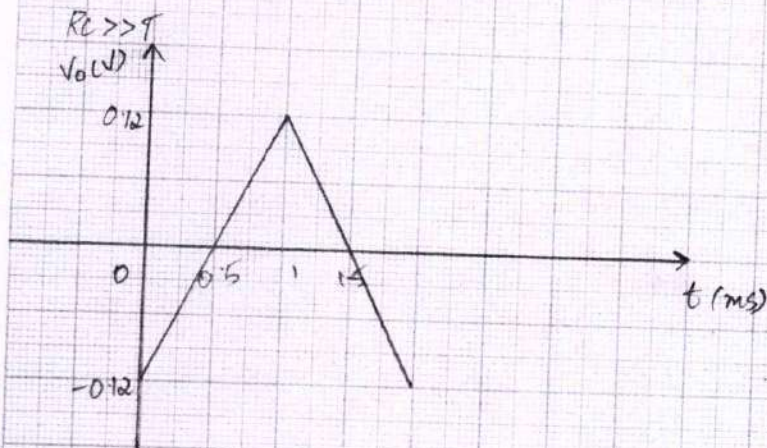on x-axis 1 cm = 0.5 ms
on y-axis 1 cm = 2.5 V




Scale

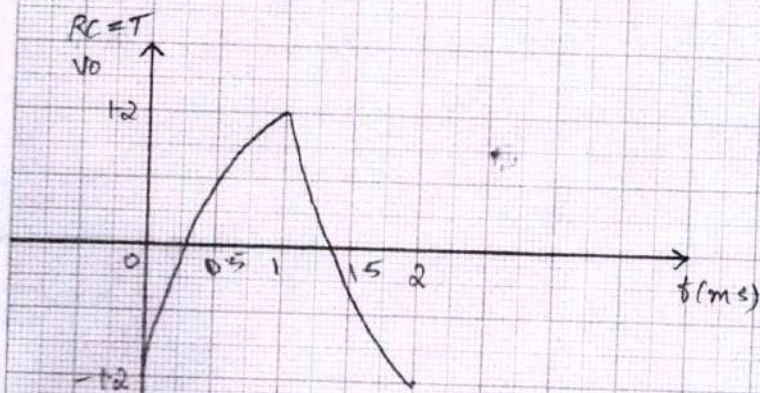on x-axis 1 cm = 0.5 ms
on y-axis 1 cm = 0.6 mV



Scale

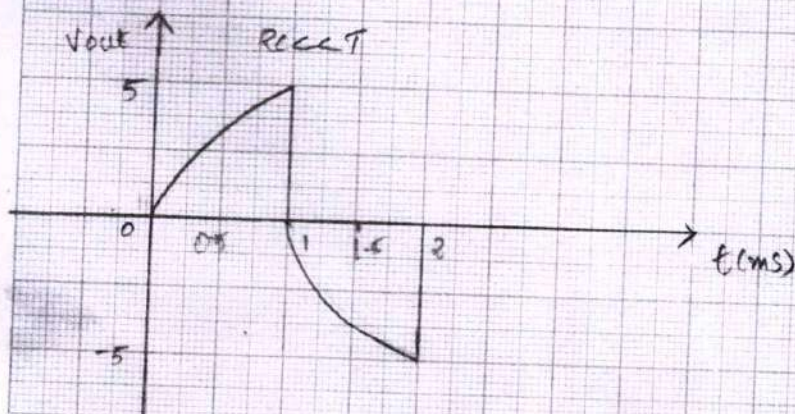on x-axis 1 cm = 0.5 ms
on y-axis 1 cm = 0.6 mV




Scale

on x-axis 1 cm = 0.5 ms
on y-axis 1 cm = 2.5 mV

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

CIRCUIT DIAGRAM

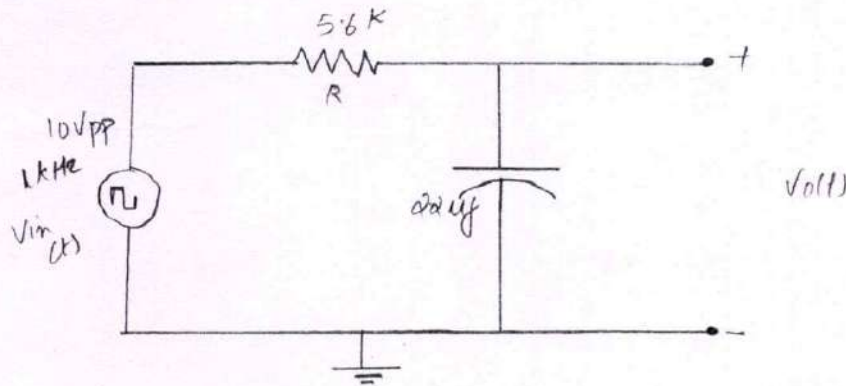

RC Integrator

Design

Case 1: $RC \gg T$

To avoid loading, select $R = 10$ times the o/p impedance of signal generation. If o/p impedance = 600 Ω , select $R = 6000 \Omega$ we $R = 5.6 k\Omega$
 $RC = 10T$ where $R = 5.6 k\Omega$ and $T = 1ms$
 Then $C = 10T/R = 1.78 \mu F$ (2 $\times$ 1 μF std)

Case 2: $RC \approx T$

$RC = T$, where $R = 5.6 k\Omega$ and $T = 1ms$
 Then $C = T/R = 0.178 \mu F$ (0.2 μF std)

Case 3: $RC \ll T$

$RC = 0.1T$

where $R = 5.6 k\Omega$, $T = 1ms$

Then $C = 0.1T/R$
 $= 0.0178 \mu F$ (0.01 μF std)

Leena
Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PATTANUR, KANNUR

output voltage across C for $R \gg T$,

Voltage drop across C increases as time increase a square waveform has positive and negative excursions with respect to its reference zero. In the input is square wave, capacitor charges and discharge from negative voltage to the positive voltage and back. for the input to work as a good integrator $\theta = 90^\circ$. As $\tan \theta = \omega RC$, $\tan 90 = \text{infinity}$ which is practically impossible. Therefore a reasonable criterion for good integration is $\theta = 89.4^\circ$ if $\theta = 89.4^\circ$, $\omega = RC = 95.48^\circ$, so $RC > 167$ will give the integrating practically.



An RC differentiation circuit is constituted with a capacitor connected in series and a resistor connected in parallel to the output. The time constant RC of the circuit is very small in comparison with the time period of all the input signal. The voltage drop across R will be very small in comparison with the drop across C . The current through capacitor is C . Hence the output is proportional to the derivative of the input output voltage across R is
For $RC \ll T$.

Differentiated output is proportional to the rate of change of input. When the input rises to maximum value, differentiated op follows it because the rate of change of voltage is transferred to the output capacitor. by the rate of change of voltage is positive differentiated output also positive. When input remains maximum for a period of time. The rate of change of voltage is zero. so input falls to zero.


Differentiation

Scale

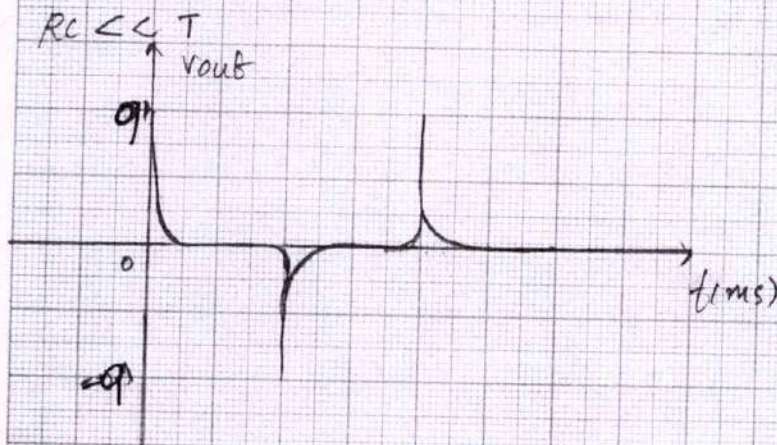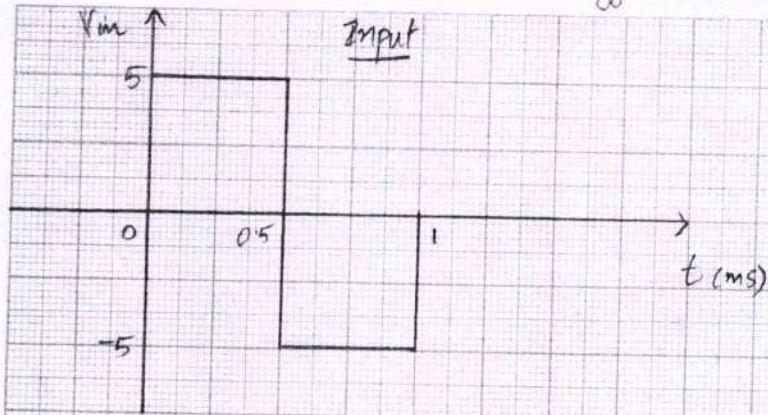
On X axis 10 DIV = 0.25 ms
On Y axis 10 DIV = 2.5 V



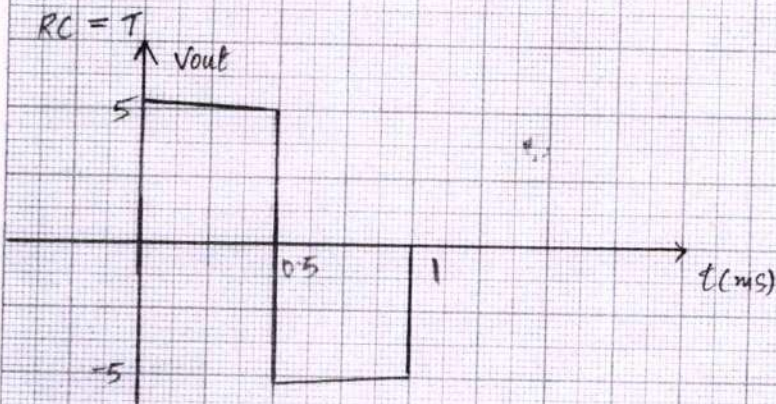On X axis 10 DIV = 0.25 ms
On Y axis 10 DIV = 2.5 V



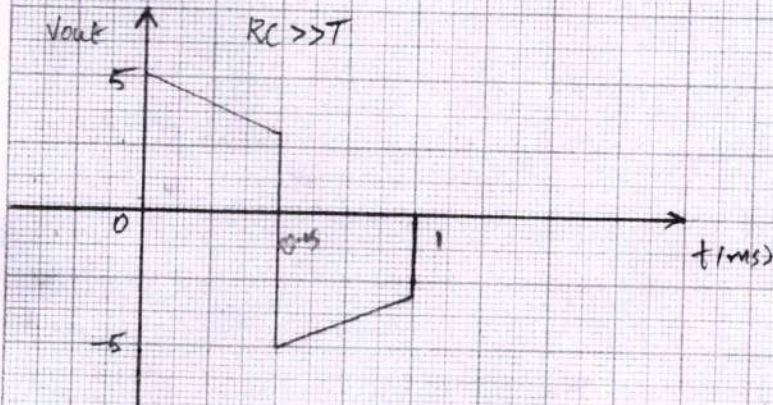On X axis 10 DIV = 0.25 ms
On Y axis 10 DIV = 2.5 V



On X axis 10 DIV = 0.25 ms
On Y axis 10 DIV = 2.5 V


Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

During this time input act like a dc voltage and capacitor offers high impedance to it. So the change in capacitor drains like dc voltage and capacitor offers high impedance to it. So the changes in capacitor drains like a dc voltages and capacitor offers high impedance to it. So the changes in capacitor drains to earth through the resistance. when i/p falls to zero rate of change of input voltage is negative. Then the output also goes to negative.

For the circuit to work as a good to negative differentiator $\theta = 90^\circ$, As for $\theta = 1/\omega R C$, $\tan 90 = \infty$. This result can be obtained only if $RC = 0$ or $C = 0$, which is practically impossible. Therefore a reasonable criterion for good differentiation is $\theta = 89.4^\circ$ if $\omega = 100$ so $RC = 0.00167$ will give the differentiating practically. Assume $R = 1000$ 0.00167 will give good spike waveform. The peak of the output of the differentiator gets doubled when the square wave is fed to the input.

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

RC DIFFERENTIATOR

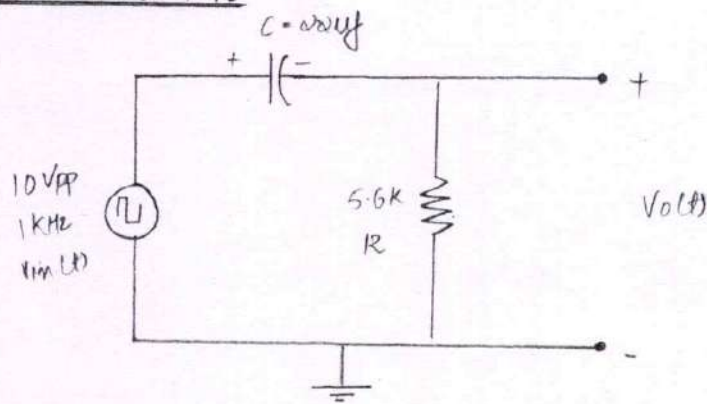

Case 1: $RC \ll T$

To avoid loading, select $R = 10$ times the output impedance of signal generation. If o/p impedance = 600Ω , select $R = 6000 \Omega$ we use $R = 5.6 k\Omega$

$RC = 0.017$, where $R = 5.6 k\Omega$ and $T = 1 \text{ ms}$
then $C = 0.01 T/R = 1.78 \text{ nF}$ (2.2 nF std)

Case 2: $RC = T$

$RC = T$, where $R = 5.6 k\Omega$ and $T = 1 \text{ ms}$
then $C = T/R = 0.22 \mu\text{F}$ (0.22 μF std)

Case 3: $RC \gg T$

$RC = 5T$

where $R = 5.6 k\Omega$ and $T = 1 \text{ ms}$


then $C = 5T/R = 0.89 \mu\text{F}$ (1 μF std)


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Integration

Scale

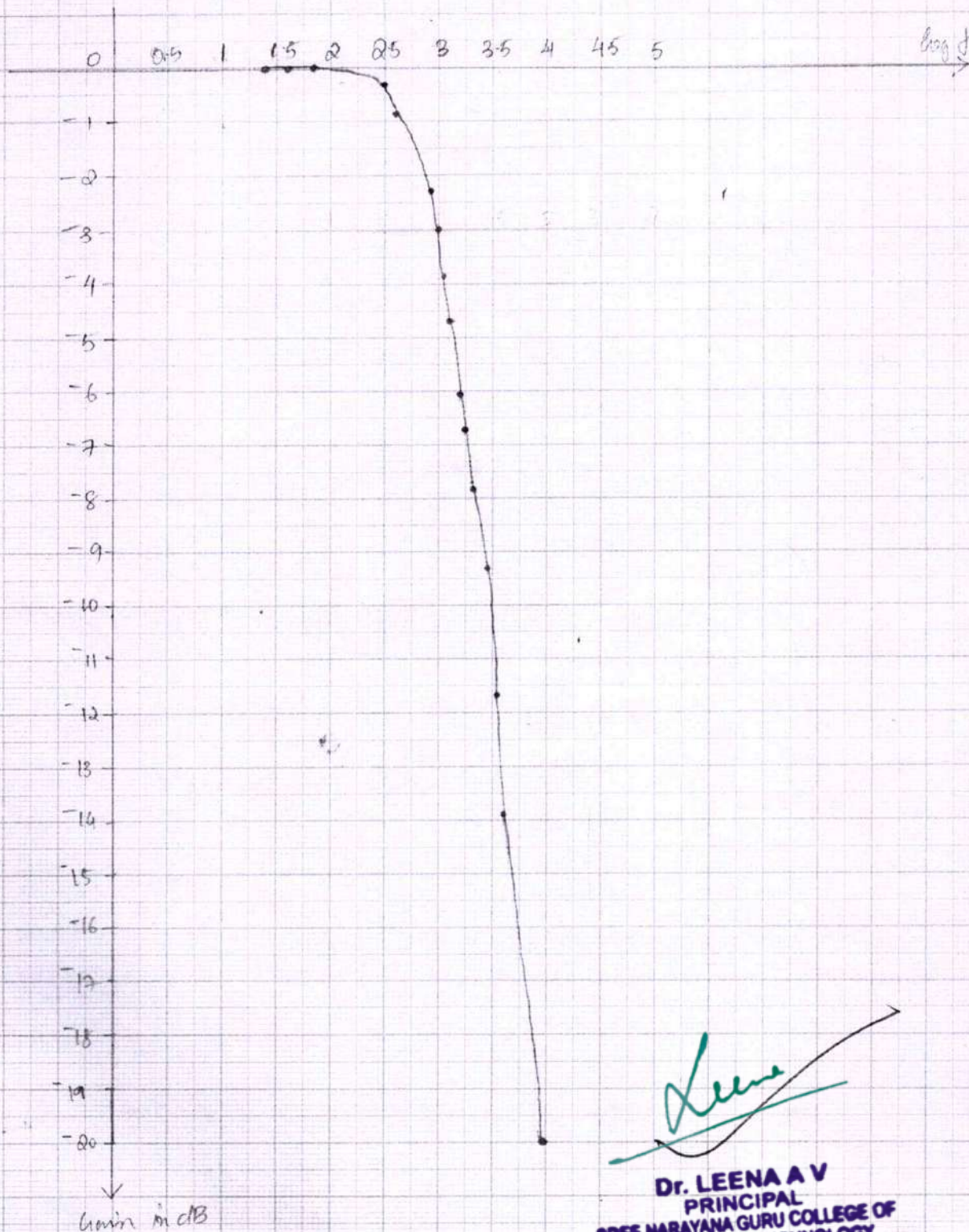On x axis 10 DIV = 0.5
On y axis 10 DIV = 1




Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

OBSERVATION


(DIFF)

P	V_o	$\log P$	Gain = $20 \log \frac{V_o}{V_{in}}$
50 Hz	0.2	1.69	-33.9
100	0.4	2	-27.95
150	1.2	2.17	-18.91
200	1.15	2.3	-18.79
250	2	2.39	-13.97
300	2.35	2.47	-12.57
350	2.8	2.54	-11.05
400	3	2.60	-11.05
450	3.8	2.60	-10.45
500	4.4	2.69	-8.40
600	4.9	2.77	-7.15
700	6.2	2.84	-6.19
1 kHz	6.2	3	-4.15
2 kHz	8.4	3.30	-1.51
3 kHz	9	3	-0.91
4 kHz	9.4	3.60	-0.53
6 kHz	9.6	3.77	-0.35
8 kHz	10	3.90	0
10 kHz	10	4	0
12 kHz	10	4.07	0

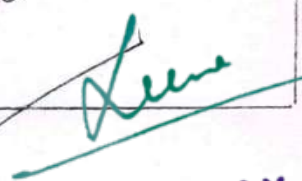
Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PAYYANUR, KANNUR

Differentiation

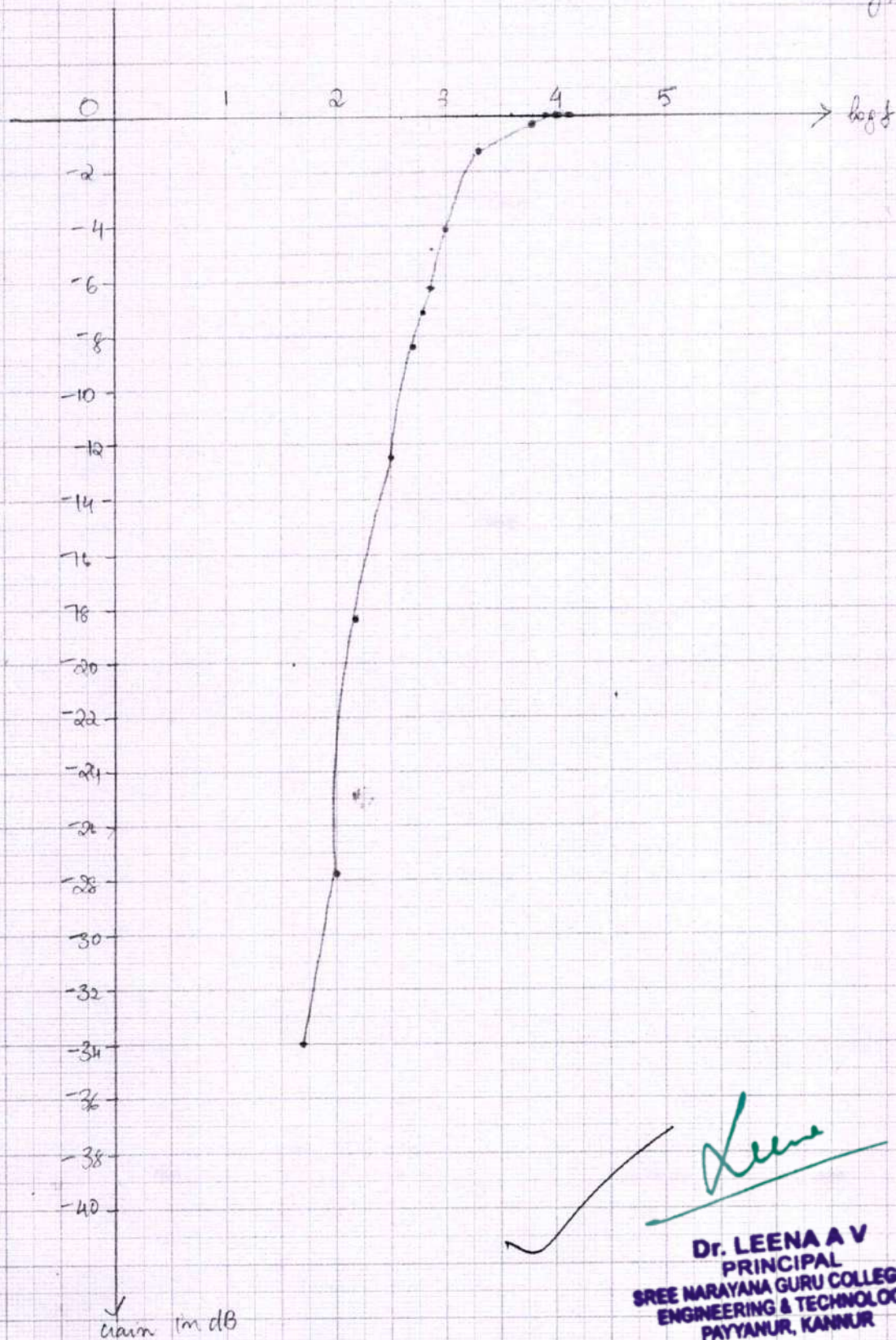Scale
on x axis $1\text{cm} = 0.5$
on y axis $1\text{cm} = 2$



Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROCEDURE :

1. Set up the circuit as per the diagram of integration
2. Switch on the function generator and set a square wave of 20pp, 1kHz
3. Observe the input and output on the x and y channels of CRO respectively
4. Note down the o/p waveform for the following conditions
 - $RC < T$
 - $RC = T$
 - $RC > T$ (Integration)
5. Repeat the same step for differentiation

RESULT:

RC integration and differentiation circuits are designed and observed the waveform for different time constants.

Procedure (5)	5
Conduction (5)	5
Result (5)	4
Viva (10)	8
Record (5)	4


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

Scale


①

ON m-ams 10 DIV = 0.25
ON y-ams 10 DIV = 1(V)

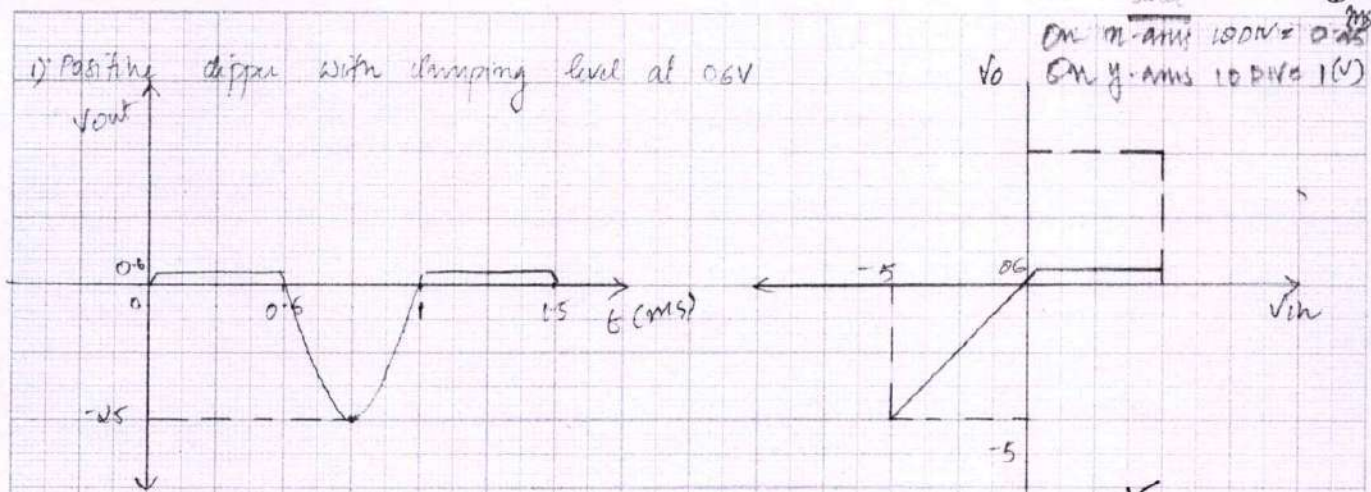
1) Positive dipper with clamping level at 0.6V



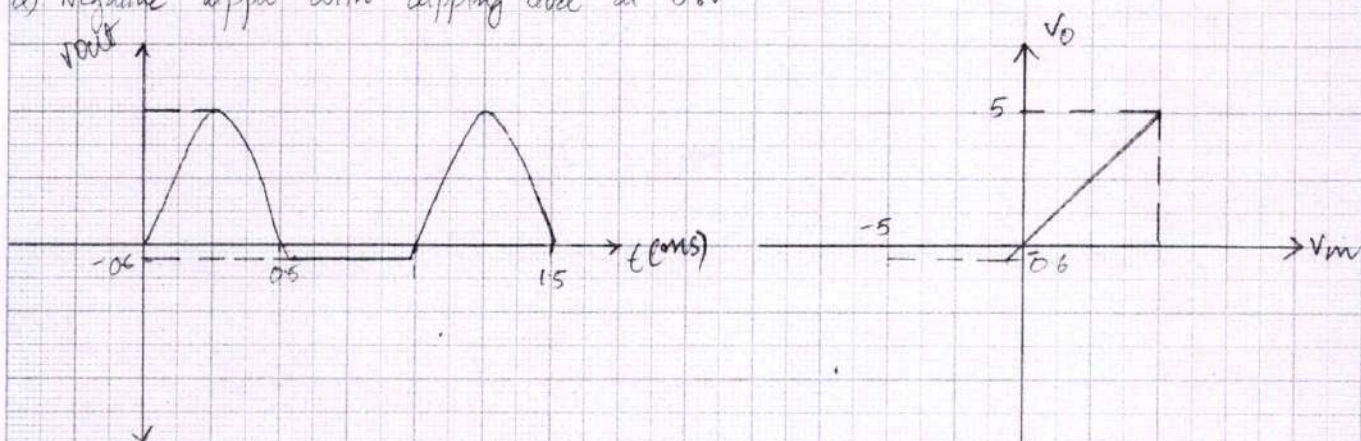2) Negative dipper with clamping level at 0.6V



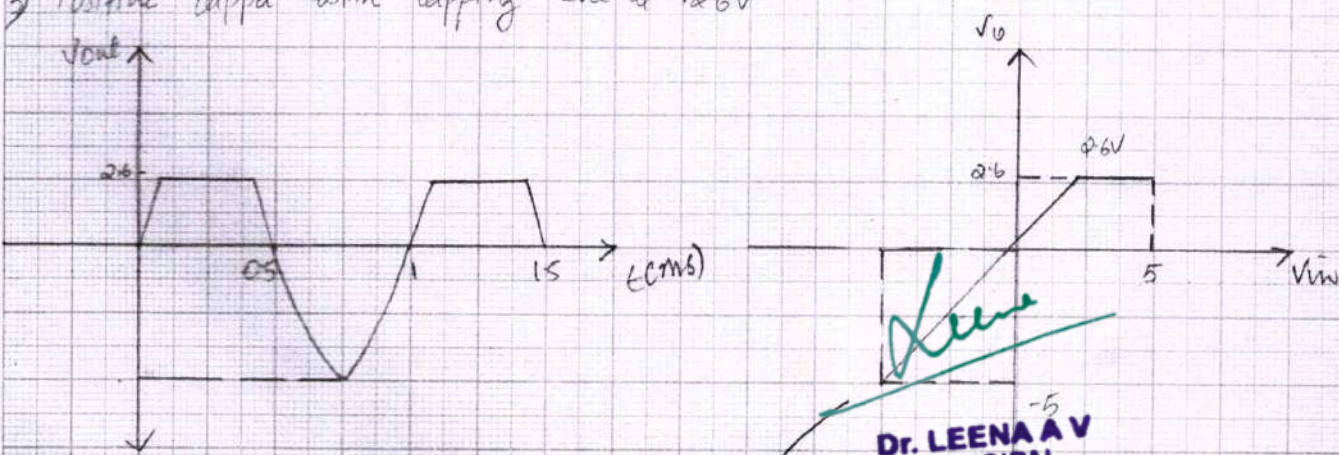3) Positive clipper with clipping level at +2.6V



Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

CLIPPING AND CLAMPING CIRCUITS

AIM:

Design and set up various clipping circuits and clamping circuits using diodes and plot the output waveform and transfer characteristics.

Components and equipments required :-

PN Diode 1N4007 - 1 No

Zener Diode 5.25 V - 1 No

Resistor 33 k Ω - 1 No

Function Generator - 1 No

CRO - 1 No

Regulation power supply - 1 No

Bread Board

Capacitor 1 μ F

Connecting wires.



Theory:

Clipping Circuits:


The property of a diode as a switching device is utilized in clipping circuits. Clipping circuits are linear wave shaping circuits. They are used to clip off the +ve or -ve portions of an input signal waveform. It can also be used to slice off an input waveform between two voltage levels using a positive clipper module. A quality square waveform can be generated using a positive clipper module.

The diode clipper can be classified as series and shunt clipper. If the diode is connected in series with input in a


CIRCUIT DIAGRAM

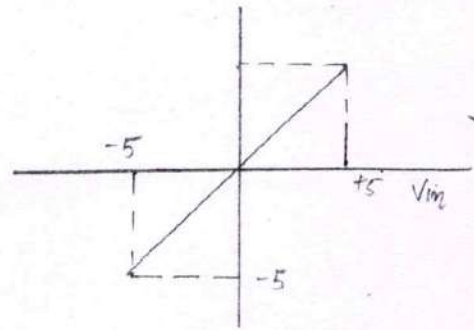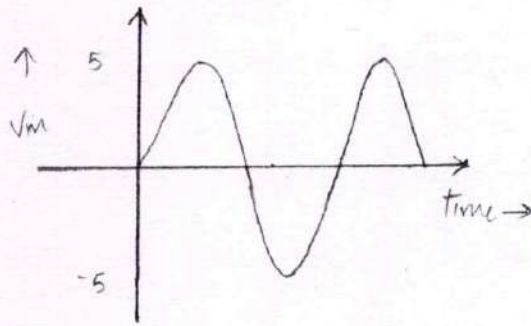

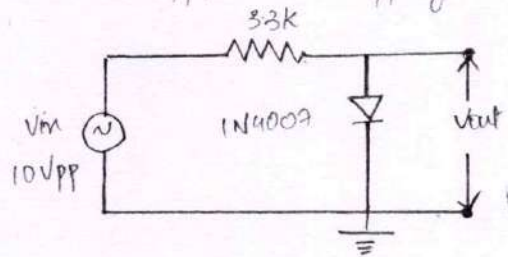
1. Positive clipper with clipping level at 0.6V



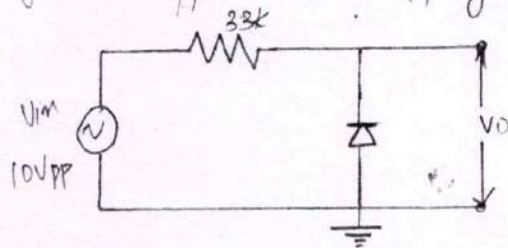2. Negative clipper with clipping level at 0.6V



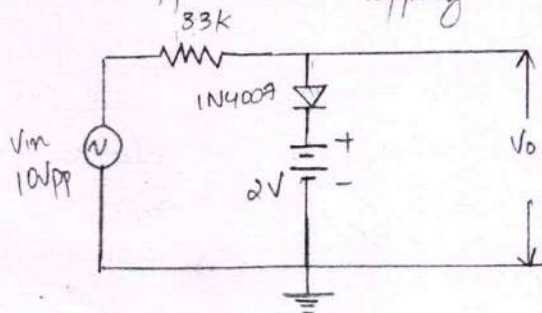3. Positive clipper with clipping level at +2.6V



Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

clippers, such a clipper is called a series clipper. If it is connected in parallel it's called shunt clipper. A resistor is used to limit the current through the diode where R_f = forward resistance of the diode and R_r is reverse resistance of the diode.

1. Positive clipper at clipping level at 0.6V:

This clipper circuit passes only negative going half cycles of the input to the output. The entire positive half cycle is bypassed through the diode since the diode is forward biased. The clipping occurs exactly at 0.6V.

2. Negative clipper with clipping level at 0.6V:

This circuit passes only positive going half cycle of the input to the output. The entire negative half cycle is bypassed through the diode since the diode gets forward biased when the input becomes negative. Due to the voltage drop across the diode the clipping occurs exactly at 0.6V.

3. Positive clipper with clipping level at +2V



For the diode to be forward biased anode voltage must be greater than cathode voltage. Till the input becomes greater than +2V, diode is reverse biased and the input will be at the output. When the input exceeds +2V, diode becomes forward biased and the cell voltage appears at the output. Since the diode is in series with the cell, actual clipping level is +2.6V.

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR



Scale

on x-axis 10 DIV = 0.25 ms
on y-axis 10 DIV = 0.5 V

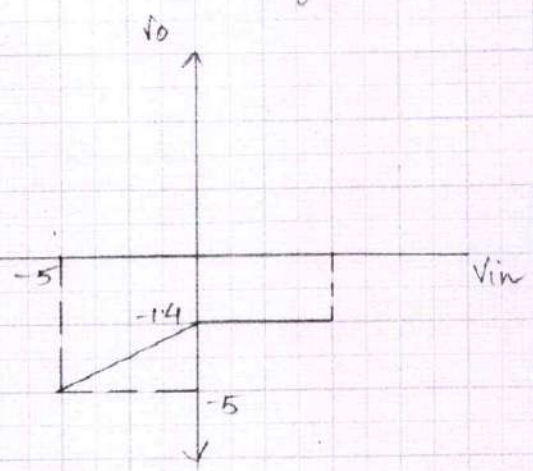
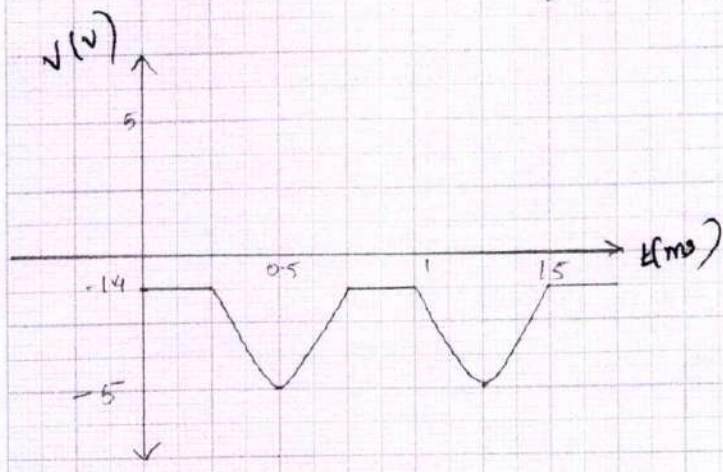
4) Positive clipper with clipping level at -1.4 V



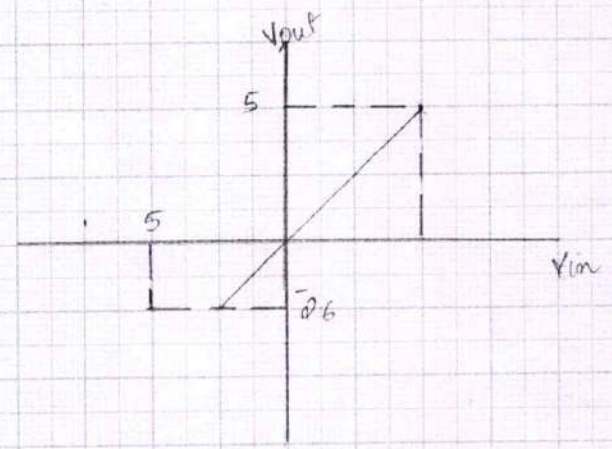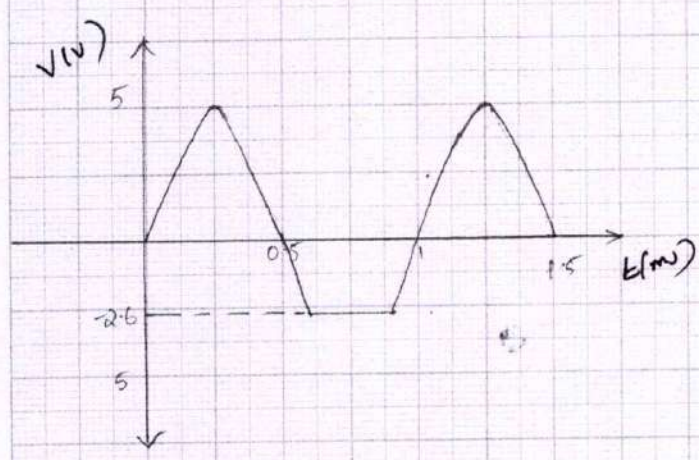5) Negative clipper with clipping level at -2.6 V



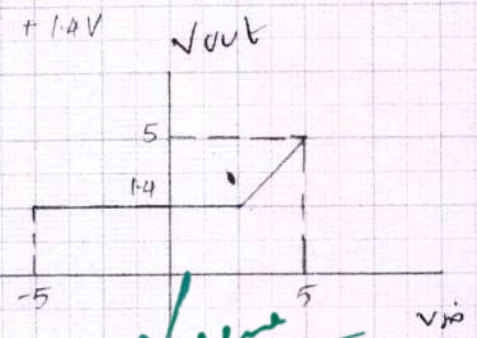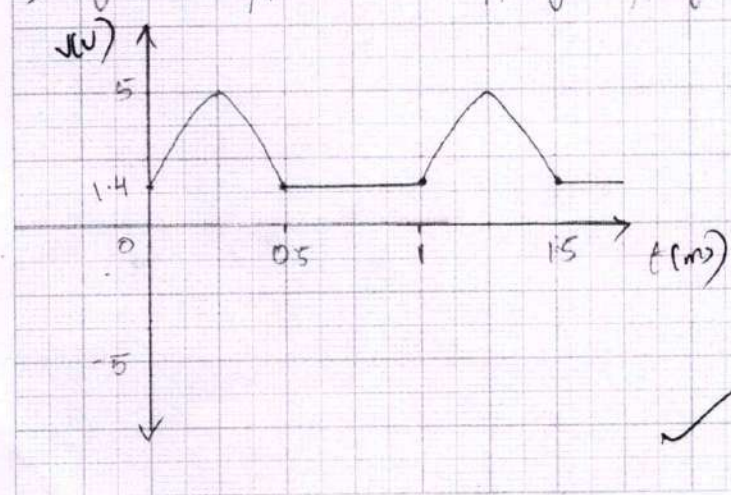6) Negative clipper with clipping level at $+1.4\text{ V}$



Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

4. Negative clipper with clipping level at $-2.6V$

Till the input becomes less than $-2V$, diode is reverse biased and the input will appear at the output. When the input is less than $-2V$, diode becomes forward biased and the cell voltage appears at the output. Since the diode is in series with the cell, actual clipping level is $-2.6V$.

5. Positive clipper with clipping level at $-1.4V$:

The diode is forward biased till the input becomes less than $-1.4V$. Here the cell voltage appears at the output. During the negative cycle when the input is less than $-1.4V$, diode is reverse biased and input appears at the output.

6. Negative clipper with clipping level at $+1.4V$


During the positive cycle when the input is greater than $+1.4V$, diode is reverse biased and input appears at the output. Till the input becomes greater than $+1.4V$ diode is forward biased and the cell voltage appears at the output.

7. Double clipper with clipping level at $+3.6V$ & $-2.6V$


The circuit is the merging positive and negative clippers. During the positive half cycle of the input, one branch will be effectively and the other open and vice versa during negative half cycle. Actual clipping level at $+3.6V$ and $-2.6V$.

Dr. LEENA V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

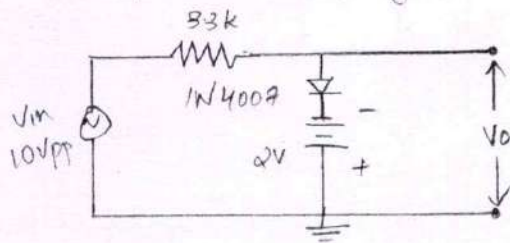
4) Positive clipper with clipping level at $-1.4V$



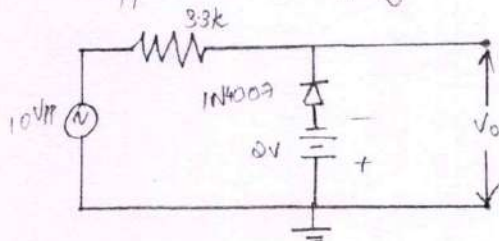
5) Negative clipper with clipping level at $-0.6V$



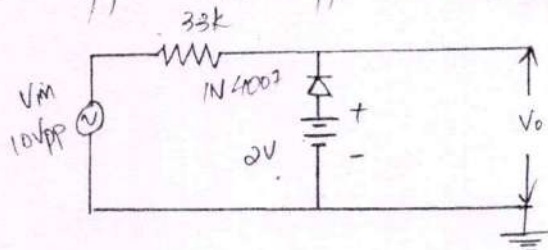
6) Negative clipper with clipper level at $1.4V$



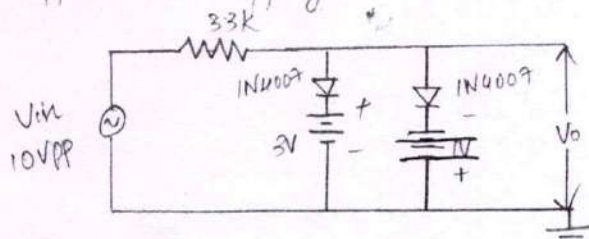
7) Double clipper with clipping level at $+3.6V$ & $-2.6V$



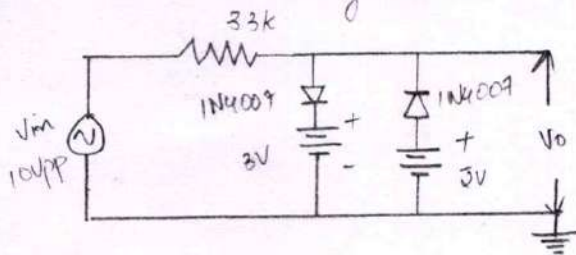8) Positive slicer with slicing level at $1.4V$ & $3.6V$



9) clipper Using Zener diode

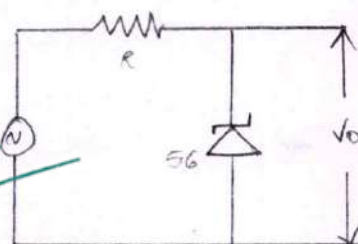


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

8. Positive clipper with clipping level at $+1.4V$ & $+3.6V$

This circuit allows the signal to pass to the output only between $+1.4V$ and $+3.6V$. During the negative half cycle of the input, diode D_1 conducts and diode D_2 gets reverse biased. Thus the output remains at $+2V$. During the positive half cycle of the input, when input exceeds $+2V$, D_1 is reverse biased and D_2 conducts and the output remains at $+2V$. Actual clipping levels at $+1.4V$ and $+3.6V$.

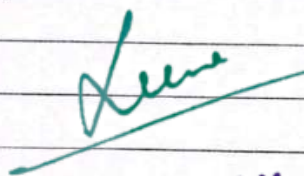9. Clipper using Zener Diode:



During positive cycle till $+5.6V$ Zener diode is reverse biased and all of input will appear at output. The output remains at $+5.6V$. During negative cycle diode is forward biased and the diode drop of $-0.6V$ will appear at the output.





Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

ON 01 AUG 10 DIV = 0.25 CM
ON 10 AUG 10 DIV = 0.5 CM

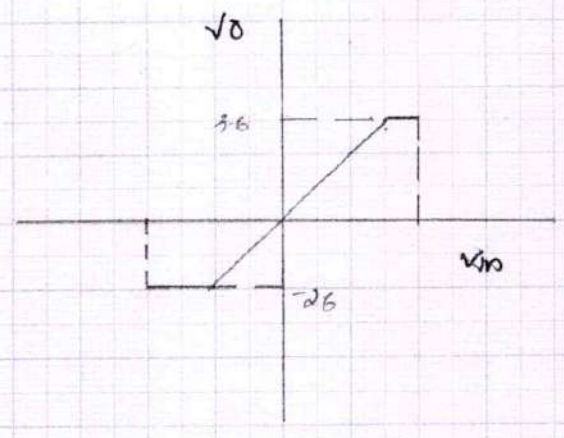
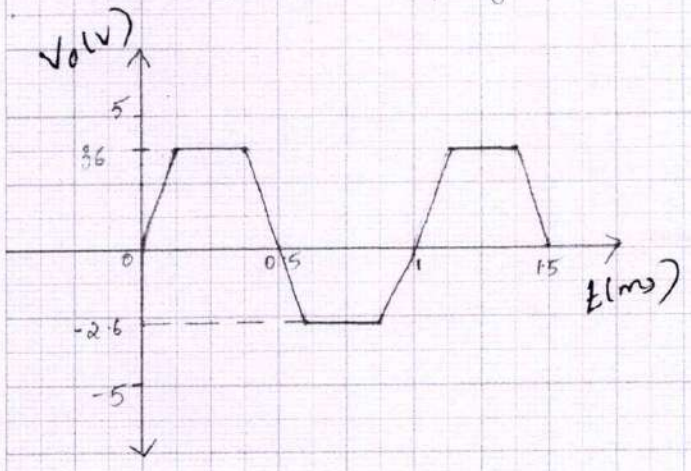
7) Double clipper with clipping level at +3.6V & -2.6V



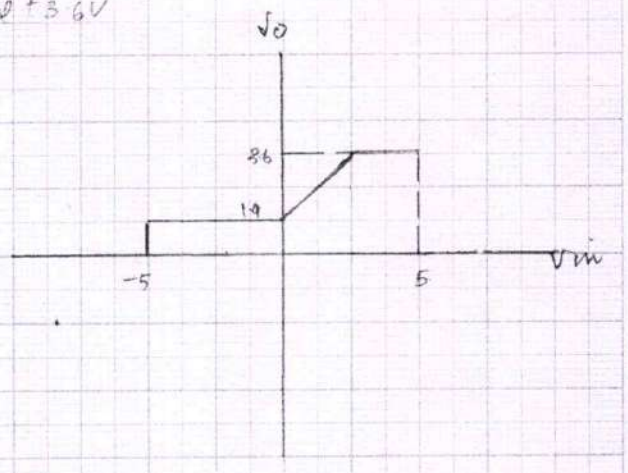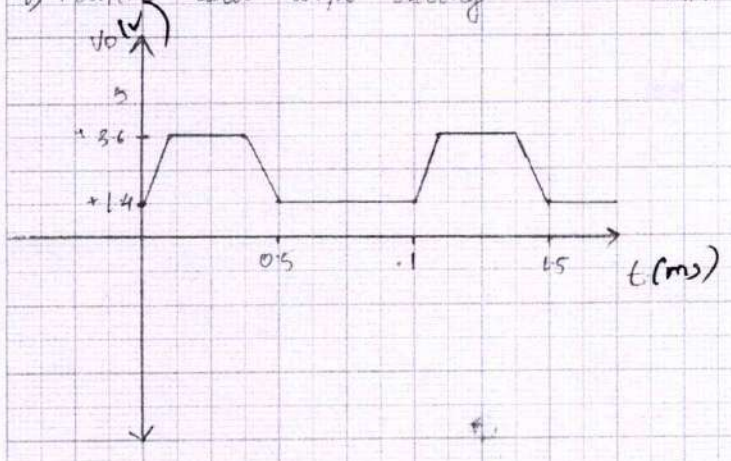8) Positive clipper with clipping level at +1.4V & +3.6V



9) clipper using Zener diode

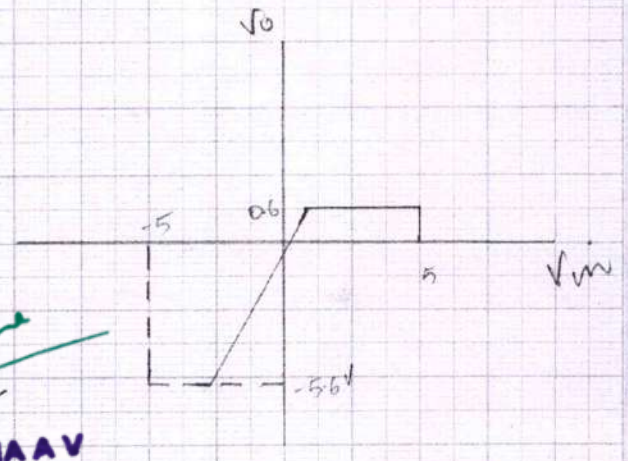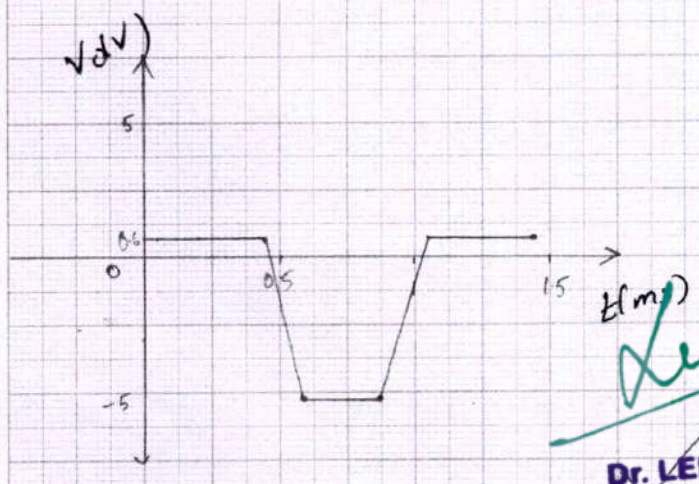

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

CLAMPING CIRCUITS :

Clamping circuits are necessary to add or subtract a dc voltage to a given waveform without changing the shape of the waveform. A capacitor which is charged to a voltage and subsequently prevented from discharging serves as a suitable replacement. This is the principle of clamping circuit. The clamping level can be made upto any level by adjusting the biasing of the diode. Such biasing circuits are called clamping circuits.

1. Positive clamper with clamping level at V_0 :

During one negative half cycle of the input sine wave, the diode conducts and capacitor charges to V_m with positive polarity at right side of the capacitor. During the positive cycle of the input sine wave, the capacitor cannot discharge since the diode not conduct. The capacitor acts as a dc source. The output voltage can be then replaced as $V_0 - V_m + V_m \sin \omega t$.


2. Negative clamper with clamping level at $0V$:

During one positive half cycle of the input sine wave, the diode conducts and capacitor charges to V_m with negative polarity at right side of the capacitor. During negative half cycle of the input sine wave, the capacitor cannot discharge since the diode does not conduct. Thus capacitor acts as a dc source of V_m connected in series with the input signal source. The output voltage then can be expressed as $V_0 - V_m + V_m \sin \omega t$.


DR. LEENA V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

CIRCUIT DIAGRAM

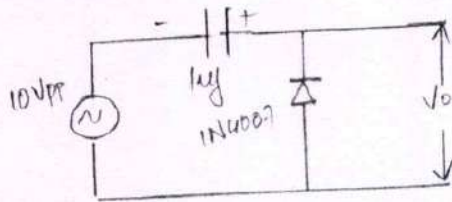
1) Positive clamper with clamping level at 0V



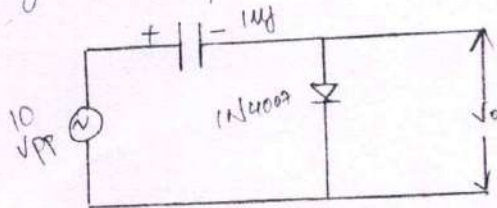
2) Negative clamper with clamping level at 0V



3) Positive clamper level at +3V

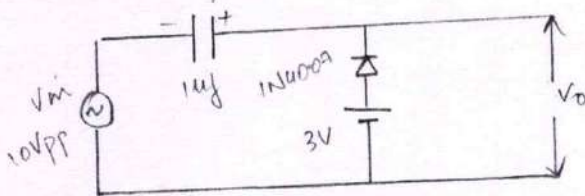

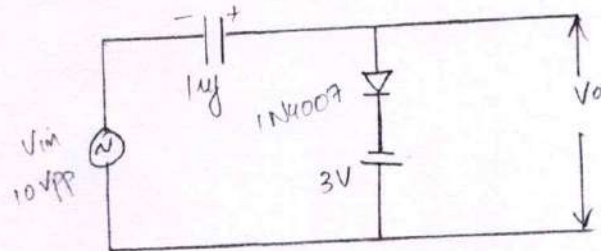4) Negative clamper with clamping level at -3V



Leena
Dr. LEENA A V
PRINCIPAL

SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

3. Positive clamper with clamping level at $+3V$

During one negative half cycle of the input sine wave, capacitor charges through the dc source and diode till $(V_m + 3)$ volts with positive polarity of the capacitor at the right side. The charging of the capacitor is limited to $(V_m + 3)$ volts due to the presence of the dc source. The output is then $V_o = (V_m + 3) + V_m \sin \omega t$.

4. Negative clamper with clamping level at $-3V$:

During one positive half cycle of the input sine wave, capacitor charges through the dc source and diode till $(V_m + 3)$ volts with the negative polarity of the capacitor at the right side. The charging of the capacitor is limited to $(V_m + 3)$ volts due to the presence of the dc source. The output $V_o = -(V_m + 3) + V_m \sin \omega t$.

5. Positive clamper with clamping level at $-3V$:

During one negative half cycle of the input sine wave, capacitor charges through the dc source and diode till $(V_m - 3)$ volts with positive polarity of the capacitor at the right side. The charging of the capacitor is limited to $(V_m - 3)$ volts due to the presence of the dc source. The output is then $V_o = (V_m - 3) + V_m \sin \omega t$.



Dr. LEENA A V

PRINCIPAL



SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR6. Negative clamper with clamping level at $+3V$:

During one positive half cycle of the input sine wave, capacitor charges through the dc source and diode till $(V_m - 3)$ volts with negative polarity of the capacitor at the

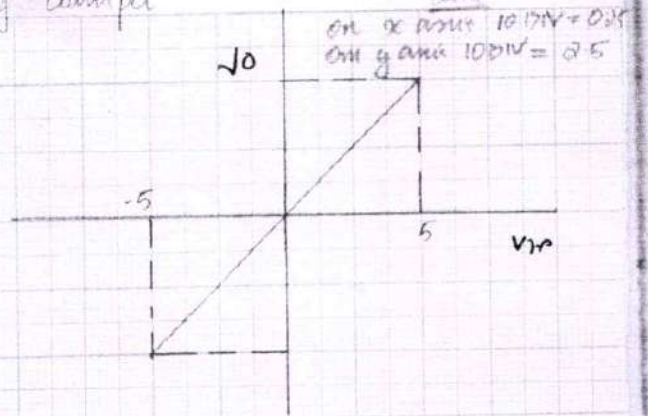
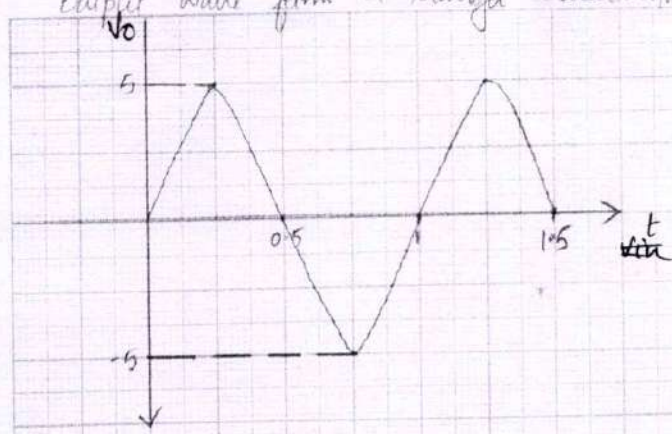
Output wave form & Transfer characteristics of clamping



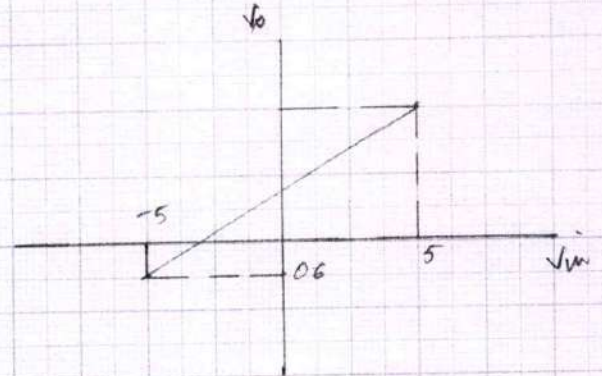
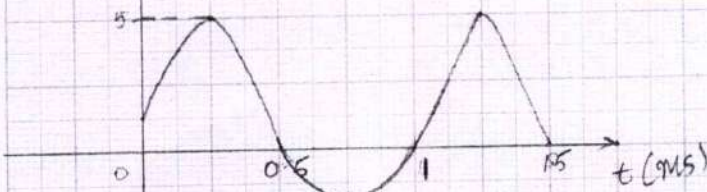
1) Positive clamper with clamping level at 0V



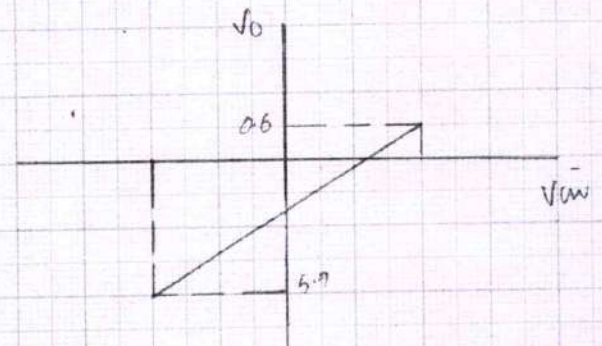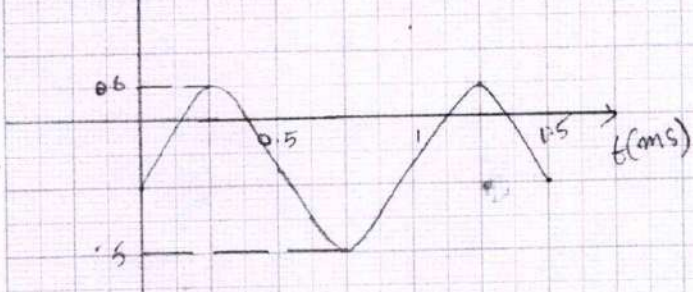2) Negative clamper with clamping level at 0V



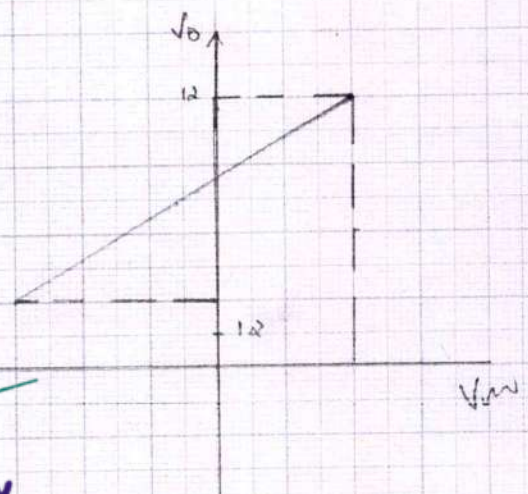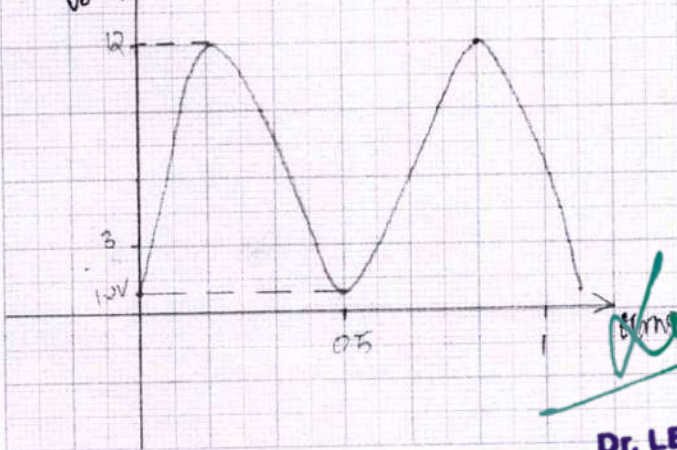3) Positive clamper with clamping level +3V



Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

right side - The charging of the capacitor is limited to $(V_m - 3)$ volts due to the presence of the dc source. The output is then $V_o = (V_m - 3) + V_m$ for w.f.


Design:

Select 1N4007

The series resistance used for current limiting

Typical value of forward resistance $R_f = 30\Omega$ and $R_a = 300k\Omega$
 $R = 3k\Omega$. Use $3.3k\Omega$ standard.

$$R = \sqrt{R_f * R_a}$$

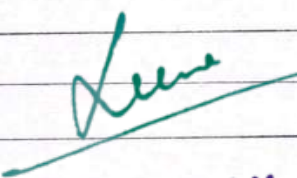
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROCEDURE : CLIPPING


1. Set up the circuit as per the circuit diagram

2. Apply 10 Vpp, 1KHz input sine wave to the circuit from the signal generator.


3. Observe the output wave forms on the IRO. Apply the input to X channel and output to channel Y and observe the waveform simultaneously. Set AC-DC coupling switch to DC mode.

4. To observe the transfer characteristic, keep the X-Y mode switch pressed and view the output.


5. Draw the output concluding the diode drop.

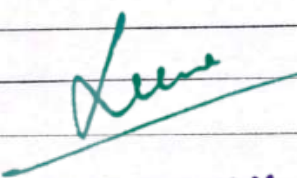
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

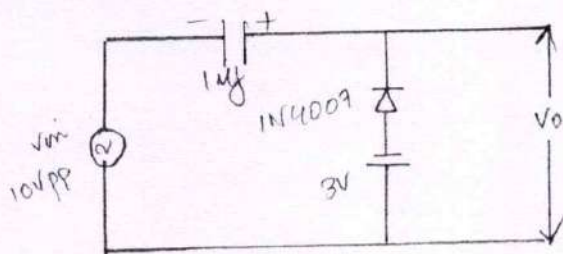5) Positive clamper with clamping level at $-3V$




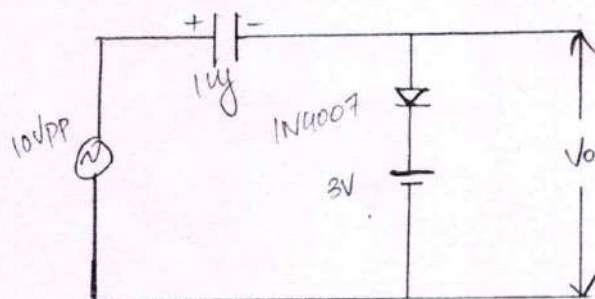6) Negative clamper with clamping level at $+3V$





Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR


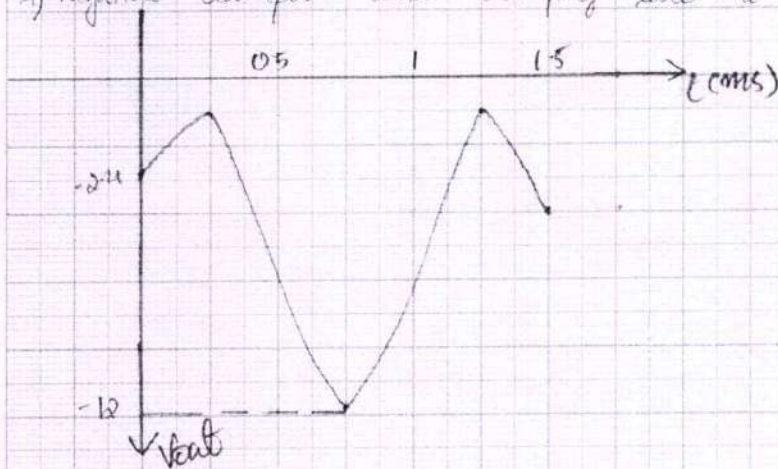
4) Negative clamper with clamping level at $-3V$




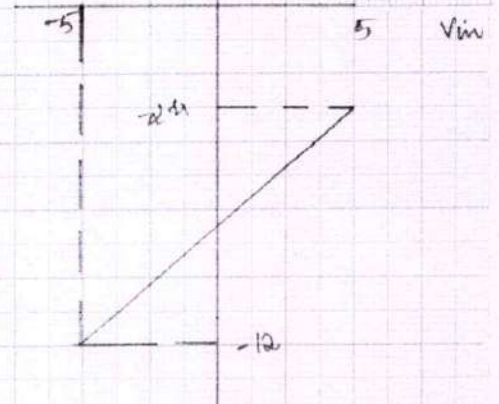
Scale
ON 20ms 10DIV = 0.25
ON 5V 10DIV = 1



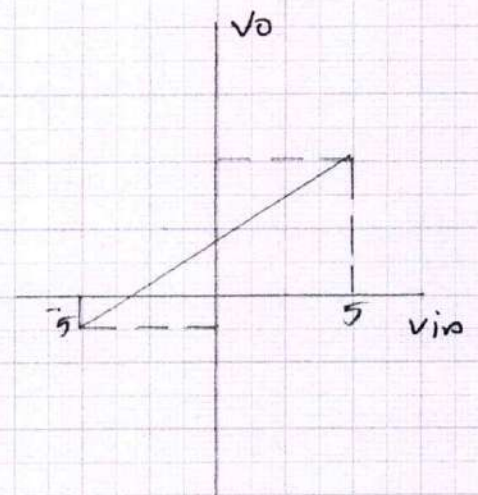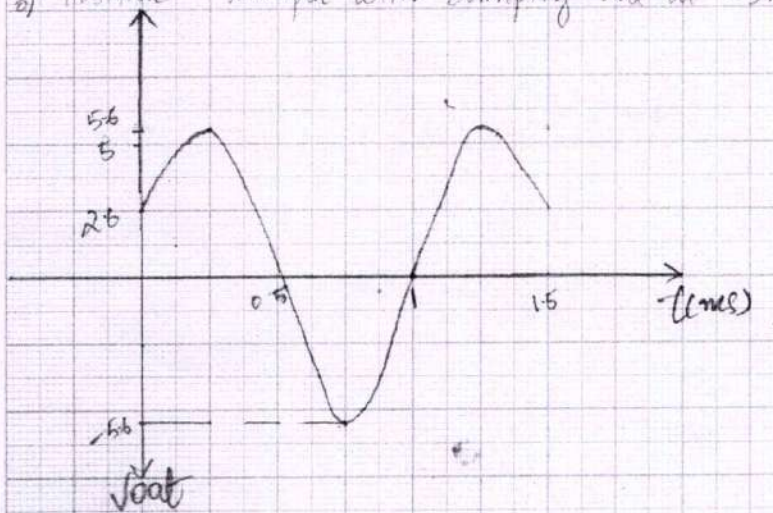5) Positive clamper with clamping level at $-3V$



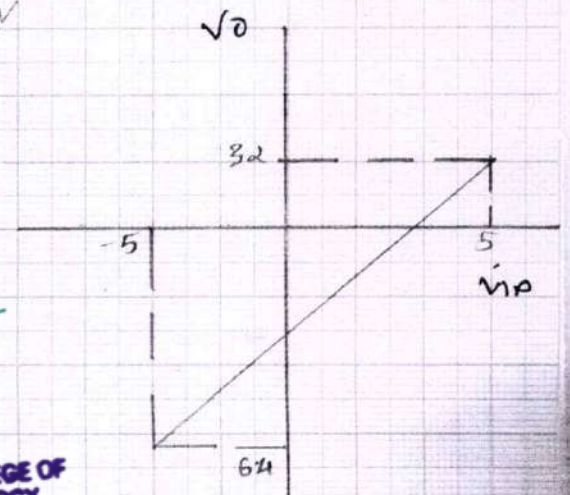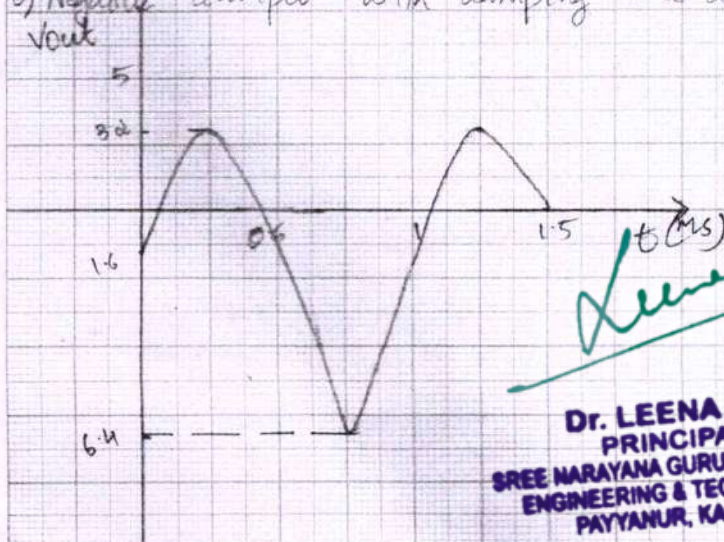6) Negative clamper with clamping level at $+3V$



Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROCEDURE:

CLAMPING:

1. Set up the circuit as the circuit diagram
2. Apply $10V_{pp}$, $1KHz$ input sine wave to the circuit from the signal generator.
3. Observe the output wave form on the CRO, Apply the input x channel and output to channel Y and observe the waveform simultaneously - switch $\alpha-\alpha$ coupling switch to α mode
4. To observe the transfer characteristics, keep the xy mode switch pencil and view the output.
5. Draw the output considering the diode loop.

Procedure (13)	5
Conduction (6)	4
Result (13)	4
Viva (10)	8
Record (12)	5

RESULT:

Various clipping and clamping circuit are studied and plotted the output waveform and transfer characteristics.

15/6/23


Leena

HOD ECE

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Teacher's Signature: _____

CIRCUIT DIAGRAM

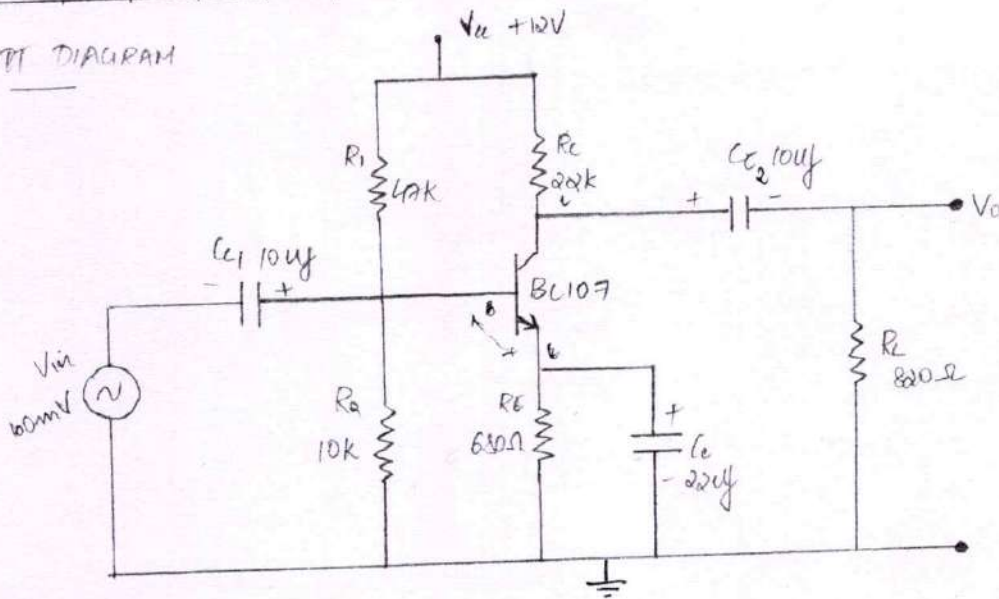

Design:

Output Requirements: Mid band voltage gain of the amplifier ≈ 50 and the required output voltage swing $\approx 10V$.
 selection of Transistor: BC107

Design of RE:

$$V_{RE} = I_E \times R_E = 1.2$$

$$V_{RE} = 1.2 / 2 \text{ mA} = 600 \Omega \quad \therefore \text{Use } 680 \Omega$$

Design of RC:

$$V_{RC} = I_C \times R_C = 4V$$

$$R_{C \text{ (theor)}} = 4V / 2 \text{ mA} = 2K \Omega \quad \text{Use } 2.2K \Omega$$

DC Biasing Condition

$$V_{CE} = 12V, I_C = 2 \text{ mA}$$

$$V_{RC} = 10\% \text{ of } V_{CC} = 4.8V$$

$$V_{RE} = 10\% \text{ of } V_{CC} = 1.2V \text{ and}$$

$$V_{CE} = 50\% \text{ of } V_{CC} = 6V$$

Design of Potential divider R1 and R2:

$$I_B = I_C / \beta_{DC} = 2 \text{ mA} / 100 = 20 \mu A$$

$$V_{R2} = \text{Voltage across } R_2 = V_{BE} + V_{RE} = 0.7 + 1.2 = 1.9V$$

$$V_{R2} = I_B \times R_2$$

$$R_2 = 1.9 / (19 \times 20 \mu A) = 10.6K \Omega \quad \text{Use } 10K \Omega$$

$$V_{R1} = \text{Voltage across } R_1 = V_{CC} - V_{R2} = 12 - 1.9 = 10.1V$$

$$V_{R1} = I_B \times R_1$$

$$R_1 = 10.1 / 10 \times 20 \mu A = 60.5K \Omega \quad \text{Use } 47K \Omega$$

Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PATTANUR, KANNUR

21

RC COUPLED AMPLIFIER

AIM:

To design and setup an RC coupled CE amplifier using bipolar junction transistor and to plot its frequency response.

COMPONENTS AND EQUIPMENTS

SL NO	Components	Specifications	Quantity
1	Resistor	47K, 10K, 22K, 680Ω	1
2	Transistor	BC 107	1
3	Capacitor	10μf, 10μf, 22μf	1
4	IC		1
5	DC Source		1
6	signal generator		1
7	connecting wire		1
8	Bread Board		1

THEORY:

RC coupled CE amplifier is widely used in audio frequency applications in radio and TV receivers. It provides current, voltage and power gains. Base current controls current of a common emitter amplifier. A small increase in base current results in relatively large increase in collector current. Similarly, a small

DR. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

Design of R_L

Gain of the common emitter amplifier is given by the expression

$$A_v = -(\beta r_c / r_e) \text{ where } r_e = R_e \parallel R_L \text{ and } r_e = 25 \text{ mV} / I_E = 25 \text{ mV} / 2 \text{ mA} = 12.5 \Omega$$

Since the required gain = 50, substituting it in the expression $R_L = 845 \Omega$ use 820 Ω std.

Design of coupling capacitor C_1 & C_2

X_{C_1} should be less than the input impedance of the transistor.

R_{in} is series impedance.

$$\text{Then } X_{C_1} \leq R_{in}/10.$$

$$\text{Hence } R_{in} = R_1 \parallel R_2 \parallel (1 + \beta r_e) r_c \text{ we get } R_{in} = 1.1 \text{ k}\Omega$$

$$\text{Then } X_{C_1} \leq 110.$$

$$C_1 \geq 1 / (2\pi f X_{C_1}) = 14 \mu\text{F} \text{ use } 15 \mu\text{F} \text{ std.}$$

$$[R_{out} = R_c]$$

$$\text{Similarly } X_{C_2} \leq R_{out}/10 = 11 \Omega \text{ use } 15 \mu\text{F} \text{ std.}$$

$$X_{C_2} \leq R_{out}/10 = R_c \text{ Then } X_{C_2} \leq 240.$$

$$\text{So } C_2 \geq 1 / (2\pi f X_{C_2}) = 6.6 \mu\text{F} \text{ use } 10 \mu\text{F} \text{ std.}$$

110

240

$f = 100$

66

Design of bypass capacitor C_E :

$$X_{C_E} \leq R_E/10$$

$$\text{then } C_E \geq 1 / (2\pi f X_{C_E}) = 23 \mu\text{F} \text{ use } 22 \mu\text{F}$$

Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

decrease in base current causes large decrease in collector current. Similarly a small decrease in base current causes large decrease in collector current. The emitter-base junction must be forward biased and the collector-base junction must be reverse biased for the proper functioning of an amplifier. In transistor is common emitter ac amplifier R_1 and R_2 are employed for the voltage divider bias of the transistor. Voltage divider bias provides good stabilization. The input signal V_{in} is coupled through C_{in} to the base and output voltage is coupled from collector through the capacitor C_{out} . The input impedance of the amplifier is expressed as $Z_{in} = R_1 || R_2 || (1 + \beta r_e)$ and output impedance as $Z_{out} = R_C || R_L || R_E$ where R_E is the internal emitter resistance. The expression is $25 \text{ mV} / I_E$ where 25 mV is temperature equivalent voltage at room temperature.

Selection of Transistor: Transistor is selected according to the frequency of operation and power required. Low frequency gain of BJT amplifier is given by the expression voltage gain $A_v = -\beta R_C / R_i$ in the circuit case with $R_i = R_1$, $A_v = -\beta R_C$. β of any transistor will vary in large ranges. For β 10^3 varies from 100 - 500. Therefore a transistor must be selected such that its minimum guaranteed β is greater than or equal to A_v required.


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

Selection of V_{CC} and V_{CE} :-
m oscillator from an audio amplifier, the

V_{CE} for a distortion less output from


51 Coupled Amplifier

$V_{in}(V)$

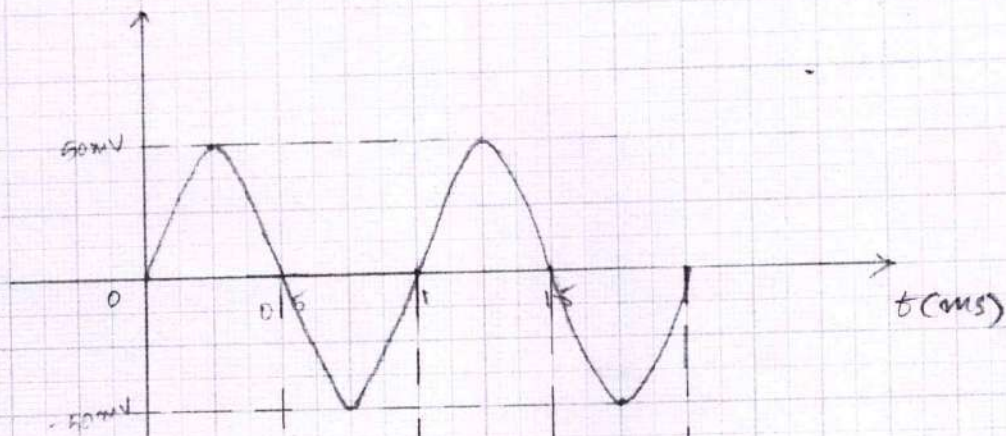

Scale
On x axis 1 cm = 0.5 ms
On y axis 1 cm = 50 mV

$V_{out}(V)$

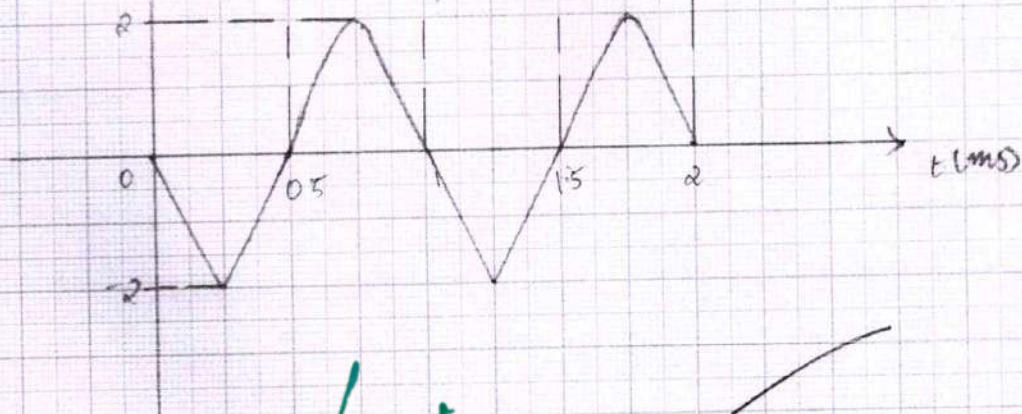

Scale
On x axis 1 cm = 0.5 ms
On y axis 1 cm = 2 V

Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

Experiment Name / No.:

Operating point must be kept at the middle of the load line selecting $V_{CE} = 50\% V_{CC}$. This means that the output voltage swing in either positive or negative direction is half of V_{CC} . However V_{CC} is 20% more than required voltage swing.

Selection of collector current I_C :

The nominal value of I_C can be selected from data sheet. Usually it will be given corresponding to h_{FE} sat. It is the bias current at which h_{FE} is measured. For BC107 it is 2mA and for power amplifier 2N3055 it is 4A.

Design of emitter resistance R_E :

Current series feedback is used in this circuit using R_E . It stabilizes the operating point against temperature variation. Voltage across R_E must be as high as possible.


Design of R_E : Value of R_E can be obtained from the relation $R_E = 0.4 V_{CC} / I_C$

Since remaining 40% V_{CC} is dropped across R_E .

Design of potential divider R_1 & R_2 : Value of V_B is obtained by using the relation $V_B = V_{CC} / h_{FEmin}$. At least $10V_B$ should be allowed through R_1 and $9V_B$ through R_2 for the better stability of bias voltage. If the current through R_1 and R_2 is near to I_B , slight variation in I_B will affect the voltage across R_1 and R_2 . For the other

gain in dB

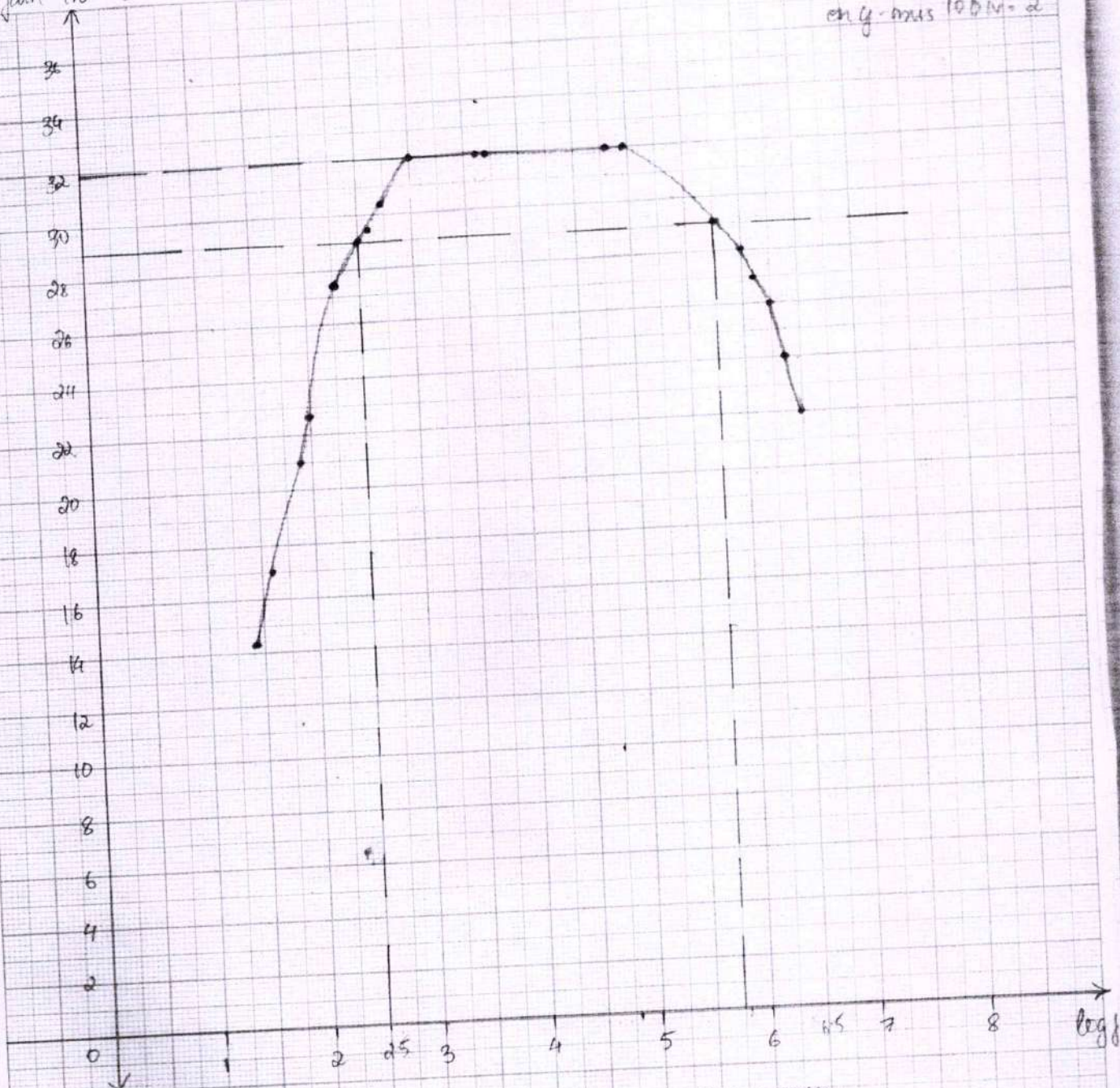Scale
on x-axis 10 DIV = 0.5
on y-axis 10 DIV = 2



$\log F_H = 6$
 $F_H = \text{antilog}(6) = 10^6$
 $= 1,000,000 \text{ Hz}$

$\log F_L = 2.5$

$F_L = \text{antilog}(2.5) = 10^{2.5}$

Dr. LEENA V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

Bandwidth

$= 999874.11 \text{ Hz}$

$= 999.87411 \text{ kHz}$

The same capacitor will load the voltage divider.

Design of Bypass Capacitor C_b :-

The purpose of the bypass capacitor is to bypass signal current to ground. To bypass the frequency of interest, X_{C_b} compared at the frequency should match less than the emitter resistance.

Design of Coupling Capacitor C_c :- The purpose of the coupling capacitor is to couple the ac signal to the input of the amplifier and block dc. It also determines the lowest frequency that to be amplified. Value of the coupling capacitor C_c is obtained such that is its resistance X_{C_c} at the lowest frequency.

PROCEDURE :-

1. Test all the components using a multimeter. Set up the circuit and verify the bias conditions. To check the bias condition, measure input signal of capacitor on the circuit.
2. Connect the capacitor in the circuit. Apply a 100 mV peak to peak sinusoidal signal from the function generator to the circuit input. Observe the input and output waveform.
3. Keep the input signal constant at 100 mV, vary the frequency of the signal from 0 to 1 MHz or highest frequency available. Measure the output amplitude.

DR. LEENA K. S.
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR KANNUR

Experiment Name / No.: _____

Camlin Page No. 24

Date / /

RESULT :-

Designed and setup an RC coupled amplifier and studied its frequency response


with CB :-

Used bias gain of the amplifier = 32 dB

Bandwidth of the amplifier = 999.6 KHz

HL
21/06/23


Procedure (5)	5
Conduction (5)	4
Result (5)	5
Viva (10)	8
Record (5)	5

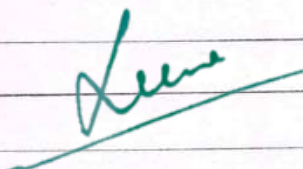
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR


HOD ECE

Teacher's Signature: _____

CIRCUIT DIAGRAM :

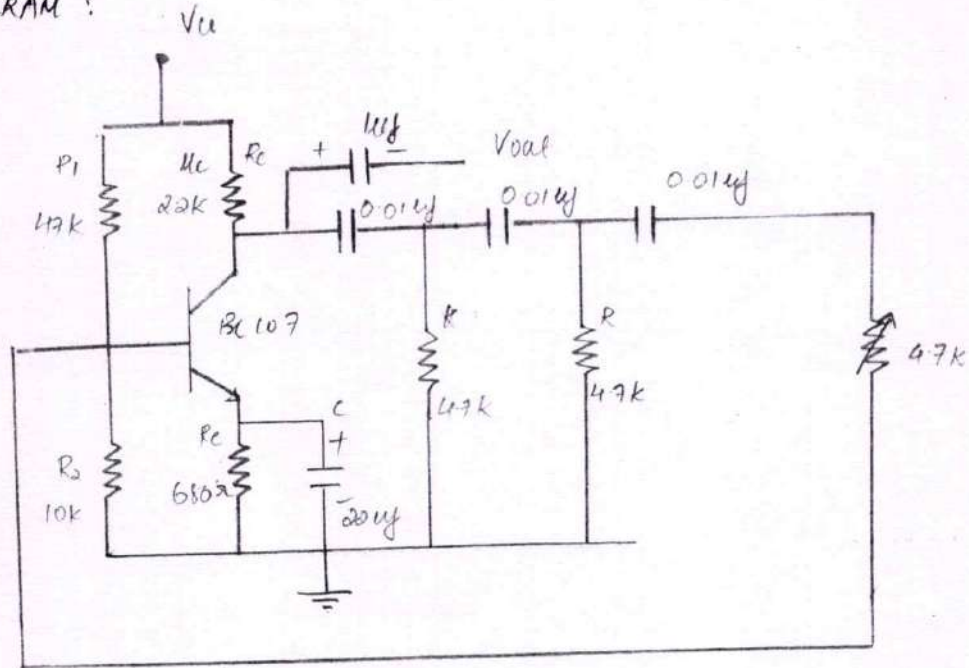

DESIGN :

Output Requirements : Sine wave with amplitude 10Vpp and frequency 1kHz

Design of the amplifier : Select transistor BC107. It can provide a gain more than 29 because its minimum β is 100

Dc Biasing Condition:

$$V_{CE} = 12V, I_C = 2mA,$$

$$V_{CE} = 40\% \text{ of } V_{CC} = 4.8V$$

$$V_{CE} = 10\% \text{ of } V_{CC} = 1.2V \text{ and}$$

$$V_{CE} = 50\% \text{ of } V_{CC} = 6V$$

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

RC PHASE SHIFT OSCILLATOR

AIM:

To design and setup an RC phase shift oscillator using BJT and to observe the sinusoidal output waveform.

COMPONENTS AND EQUIPMENTS REQUIRED:

COMPONENTS	SPECIFICATIONS	QUANTITY
1. Transistor	BC 107	3
2. Capacitor	0.01 μ f, 1 μ f, 10 μ f	3, 1, 1
3. Resistor	4.7K, 10K, 4.7K, 680, 22K	1, 1, 2, 3, 3
4. Potentiometer	4.7 K (pot)	1
5. Bread Board		
6. CRO		
7. DC Source		

THEORY:

An oscillator is an electronic circuit for generating an ac signal voltage with a dc supply as the only input requirement. The frequency of the generated signal is decided by the circuit element. An oscillator requires an amplifying frequency selective network and a positive feedback. The output is fed back to the input. The feedback network is for the feedback factor. The unity gain means signal is in phase.

Design of R_L

$$V_{R_L} = I_C \times R_L = 4.8$$

$$V_{R_L} = 4.8 / 2 \text{ mA} = 2.4 \text{ k}\Omega, \text{ we } 2.4 \text{ k}\Omega$$

Design of R_E :

$$V_{R_E} = I_E \times R_E = 1.2$$

$$V_{R_E} = 1.2 / 2 \text{ mA} = 600 \Omega \text{ we } 680 \Omega$$

Design of R_1 & R_2

$$I_B = I_C / \beta = 2 \text{ mA} / 100 = 20 \mu\text{A}$$

Assume the current through $R_1 = 10 I_B$ and that through divider by the base current.

$$V_{R_2} = I_B \times R_2, R_2 = 1.9 / 9 \times 20 \mu\text{A} = 10.6 \text{ k}\Omega \text{ we } 10 \text{ k}\Omega$$

$$V_{R_1} = \text{Voltage across } R_1 = V_{CC} - V_{R_2} = 12 - 1.9 = 10.1 \text{ V}$$

$$V_{R_1} = I_{R_1} \times R_1, R_1 = 10.1 / 10 \times 20 \mu\text{A} = 50 \text{ k}\Omega \text{ we } 47 \text{ k}\Omega$$

Design of Bypass Capacitor C_E

$$X_{C_E} \leq R_E / 10 \quad \text{Then } C_E \geq 1 / (2\pi \times 100 \times 68) = 2.3 \mu\text{F} \text{ we } 47 \mu\text{F}$$

Design of frequency selective network

$$f = 1 / (2\pi R_E \sqrt{C_E + 4R_E / R}) = 1 \text{ kHz}$$

The frequency determined by R & R_E must be shifted in such a way to avoid loading of amplifier so R is taken as $2R_E$

$$R = 2R_E = 2 \times 2.4 \text{ k}\Omega = 4.8 \text{ k}\Omega \text{ we } 4.7 \text{ k}\Omega \quad \text{Then}$$

$$C = 1 / (2\pi \times 4.8 \times 10^3 \times 1 \times 10^3 \sqrt{8}) = 0.14 \mu\text{F} \text{ we } 0.1 \mu\text{F}$$

Tabular Column:

DC condition:

DC condition	V_{CC}	V_{R_1}	V_{R_2}	V_{R_L}	V_{R_E}	V_{CE}
Theoretical	12V	10.1V	1.9V	4.8V	1.2V	6V
Practical	12V	10V	2V	4.6V	1.4V	

DR. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

4. Connect the feedback network and observe the sine wave measure its amplitude and frequency.

Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR


Procedure (3)	5
Conduction (4)	4
Result (5)	5
Viva (10)	8
Record (4)	5

RESULT:

Designed and setup the Re phase shift oscillator and obtained the output.

La...
HOD ECE

CASCADE AMPLIFIER CIRCUIT DIAGRAM

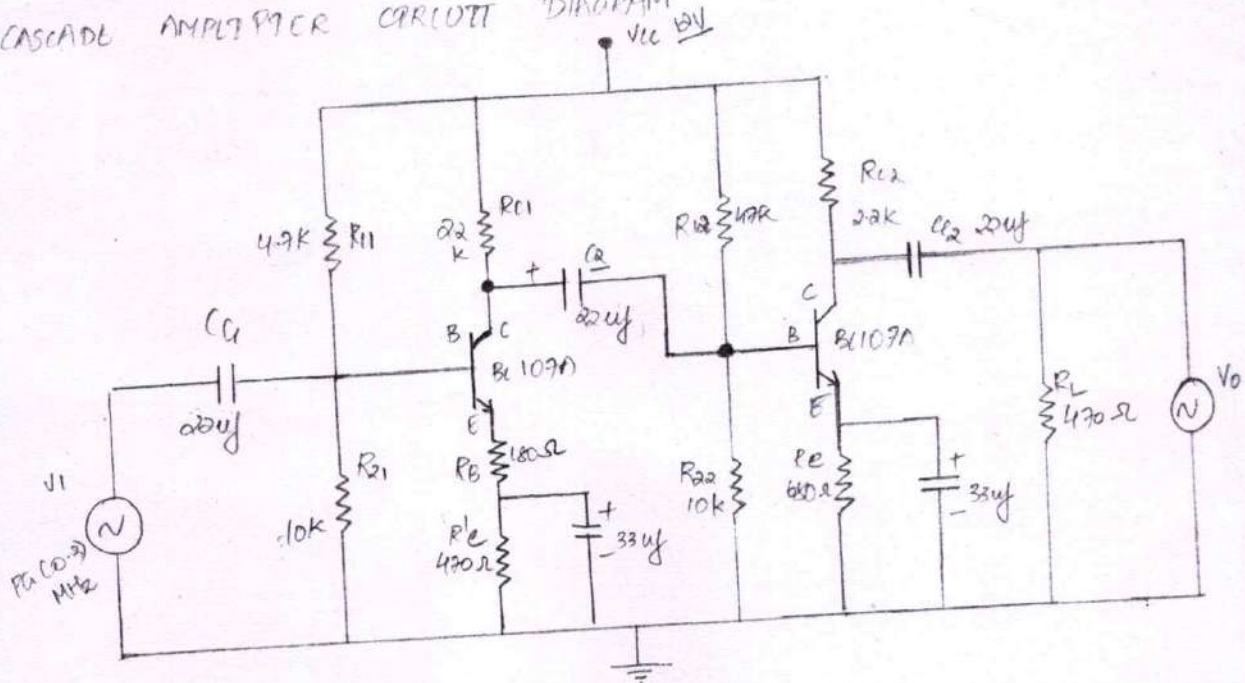

P (Hz)	V ₀ (V)	log 6	gain
30 Hz	0.6	1.47	29.54
100 Hz	1.2	2	35.56
300 Hz	2	2.47	40
1 kHz	2.4	3	41.58
2 kHz	2.5	3.3	41.9
5 kHz	2.5	3.69	41.9
10 kHz	2.5	4	41.9
50 kHz	2.5	4.69	41.9
100 kHz	2.4	5	41.58
200 kHz	2.3	5.30	41.21
300 kHz	2.2	5.47	40.8
350 kHz	2	5.54	40
700 kHz	1.9	5.84	38.58
1 MHz	1.6	6	38.06
1.5 MHz	1.2	6.19	35.56
2 MHz	1	6.30	33.99
3 MHz	0.7	6.47	30.88

$$\left[20 \log \frac{V_o}{V_{in}} \right]$$

$$20 \log \frac{V_o}{(20 \times 10^{-3})} = 20 \log \frac{V_o}{0.02}$$

Design:

Design: amplifier
 output requirement: Mid band voltage gain of the
 selection of transistor: select transistor BC107
 Assume gain $A_1 = 4$ & $A_2 = 25$. Since $A = A_1 A_2$
 A_1 should be lower value to avoid high input
 voltage to second stage high input

DC Biasing Condition

$V_{CE} = 12V$, $I_C = 2mA$, $V_{CE} = 40\%$ of $V_{CC} = 48V$

$V_{RE} = 10\% \text{ of } V_{CC}$ and $V_{CE} = 50\% \text{ of } V_{CC}$

Design of R_{E1} & R_{E2} : take $R_{E1} = R_{C2} = R_E$ $V_{RE} = 2V_E$

$V_{RE} = 4.3V$, $R_E = 2.4k$ Use 2.2k std

Design of RE1 & RE of fault stage is split into A + B. link use 225k

$V_{RE} = I_E \times R_E = 4 \text{ V} \Rightarrow R_E = 24 \text{ k}\Omega$ MC 22.5k

$V_{RE} = I_C \times R_C = 48V$
 $V_{RE} = I_E \times R_E$ Because $I_E \approx I_C$
 $= 12V \Rightarrow R_E = \frac{12V}{I_E}$

Dr. LEENA A Y
 PRINCIPAL
 SHREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 HANUR, HANUR

$= 1.2V$. $\Rightarrow$ RE

Dr. LEENA A V
PRINCIPAL

PRINCIPAL

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Experiment Name / No.: 5

Camlin / Page No. 28

Date 15/06/2023

CASCAD AMPLIFIER

AIM:

To design, set up and study a two stage RC couple
CE amplifier using BJT

COMPONENTS REQUIRED

SL NO.	APPARATUS	RANGE	QUANTITY
1	function generator	0-3 MHz	1
2	TRD	0-3 MHz	1
3	Bread Board	10 k Ω (2)	1
4	Resistor	47k Ω , 22k, 680 Ω 470 Ω	
5	Capacitors	0.01 μ F, 10 μ F	
6	Transistor	BC107	2
7	Connecting wire	Single strand	As required
8	Power Supply	(0-30 V)	1

THEORY:

Multistage amplifier are used in cascade to improve parameters such as voltage gain, current gain, input impedance and output impedance etc. Common emitter stage provide an overall voltage gain $A_1 A_2$ where A_1 & A_2 are the gains of first and

Teacher's Signature: _____

CASCADE FMP

$V_{in}(V)$

10
mV

0

0.5

1

1.5

$t \rightarrow$
(ms)

10

0

$V_o(V)$

0.9

0

0.5

1

1.5

$t \rightarrow$
(ms)

0.9

Scale

On X axis 2cm = 0.5 units
On Y axis 1cm = 0.5 units

Scale

on X axis 2cm = 0.5 units
on Y axis 1cm = 0.5 units



Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

second stage respectively - Since each stage provide a phase inversion. The final output signal is in phase with the input signal.

The input impedance of the signal stage is in parallel with R_{E1} of the first stage. The ac voltage gain of the first stage is $A_1 = R_{E1} \parallel R_{in2} / (R_{E1} + R_{E1})$ where R_{in2} is the input resistance of the second stage $R_{in2} = R_{B1} \parallel R_{B2} \parallel (1 + \beta R_{E2})$.

The ac voltage gain of the second stage is $A_2 = (R_{C2} \parallel R_L) / R_{E2}$.

A three type of amplifier circuits are employed in designing microphone and loudspeaker.

PROCEDURE:

1. Connect the circuit as per the circuit diagram.


2. Determine the Q point of the amplifier using DC analysis.

3. Determine Maximum input voltage that can be applied to amplifier using AC analysis.

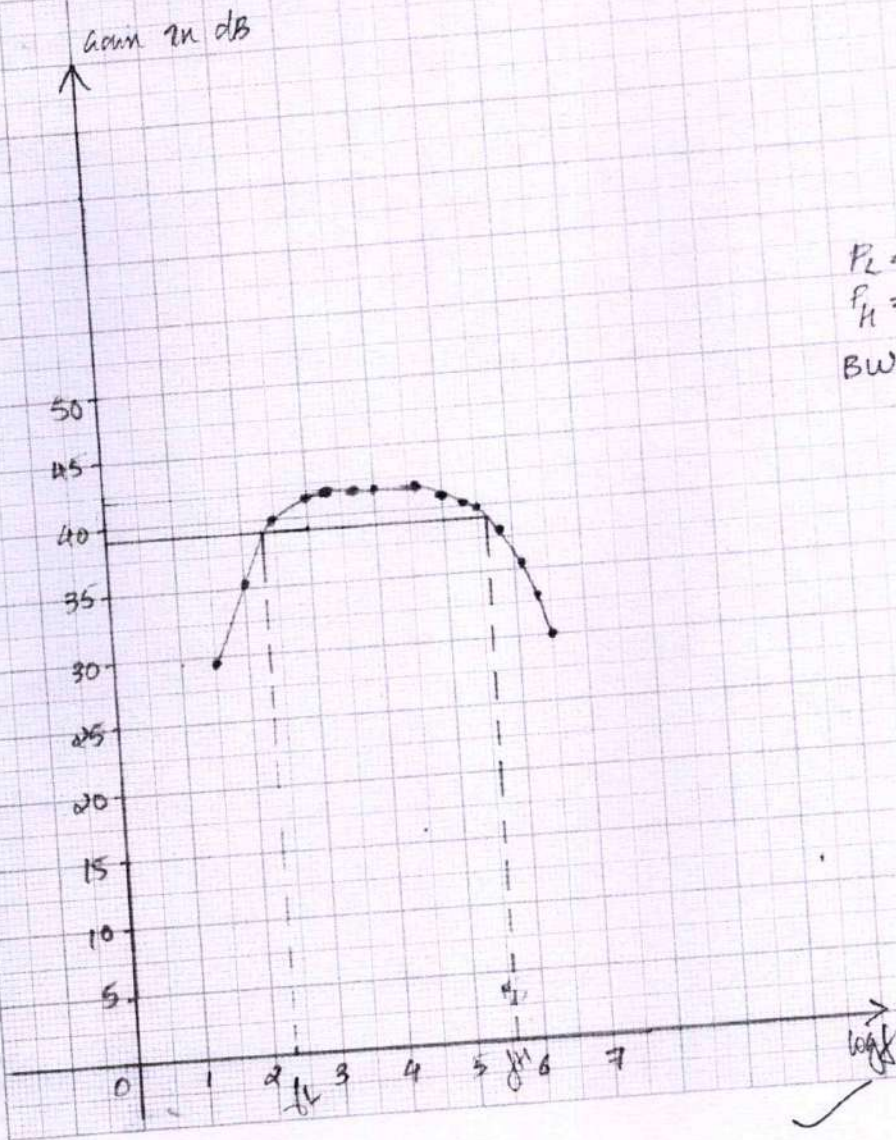4. Set the input voltage $V_{in} = 1 \text{ mV}$ and vary the input signal frequency from 0 Hz to 1 MHz in incremental steps and observe the corresponding output voltage V_o for at least 20 different values for the considered range.

DR. LEENA A V
PRINCIPAL
SREEHARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

on x axis 1cm = 100 Hz
on y axis 1cm = 5 dB



$$P_L = 10^{-2.3}$$

$$P_H = 10^{-5.6}$$

$$BW = 10^{-2.3} - 10^{-5.6}$$

$$= 399 \text{ KHz}$$

To bypass the lowest frequency (100 Hz) X_{CE} should be less than or from a equal to the resistance R_E .

$$\text{if } X_{CE} \leq R_E / 10$$

Then

$$C_E \geq \frac{1}{2\pi \times 100 \times 68}$$

$$= 23 \mu\text{F}$$

$$\text{Use } 33 \mu\text{F} //$$

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

min is 100.

$I_B = I_C / \beta_{FE} = 2mA / 100 = 20\mu A$. Assume $R_1 = 10^5 \Omega$ and that $R_2 = 47k \Omega$ for the

stability of the potential divider bias current.

V_{R2} - voltage across $R_2 = V_{CC} + V_{RE}$

$V_{R2} = V_{BE} + V_{RE} = 0.6V + 12V = 12.6V$ also $V_{R2} = 47k R_2 = 18V$

Then $R_2 = 12.6 / 0.7 \times 10^{-3} \times 10^{-6} = 10k$

V_{R1} - Voltage across $R_1 = V_{CC} - V_{R2} = 12V - 12.6V = 10.2V$ / $V_{R1} = 10^5 R_1 = 10.2V$

Then $R_1 = \frac{10.2}{10 \times 10^{-3} \times 10^{-3}} = 51k$

Design for R_E and R_E'

$$A_1 = \frac{R_{E1} R_{in2}}{(R_{E1} + R_E)} \quad R_E = R_E - R_E' \quad \text{and} \quad R_{in2} = R_1 \parallel R_2 \parallel (1 + \beta_{FE} r_{e1}) = 1.1k \Omega \quad | \quad r_{e1} = 25mV / I_E$$

$$R_E = 173\Omega \quad \text{use } 180\Omega \quad | \quad R_E = R_E - R_E' = 680\Omega - 180\Omega = 500\Omega \quad \text{use } 470\Omega$$

Design of R_C

Gain of the second stage is given by the expression $A_2 = (R_C \parallel R_L) / r_{e2} = 25$
 $R_C = 863\Omega$. Use 470Ω

Design of coupling capacitor (C_1 , C_2 and C_3) to permit the lowest frequency f_c (say 100Hz). X_{C1} should be less than or equal to the i/p resistance R_{in1} .

$X_{C1} \leq R_{in1} / 10$. Then $R_{in1} = R_1 \parallel R_2 \parallel (1 + \beta_{FE}) R_E = 1.1k \Omega$ as of std.

Then take $C_2 = C_3 = C_4 = 22\mu F$ because of i/p impedance of second stage

Design of Bypass capacitor C_E

To bypass the lowest frequency (100Hz). X_{C_E} should be less than or than or equal to the resistance R_E .

$$\text{i.e. } X_{C_E} \leq R_E / 10$$

Then

$$C_E \geq \frac{1}{2\pi f \times 100 \times R_E}$$

$$= 23\mu F$$

Use $33\mu F$


Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PATTANUR, KANNUR

5. The voltage gain calculated as

$$A_v = 20 \log (V_o/V_i) \text{ dB}$$

6. Find the Bandwidth and gain-Bandwidth product from
 semi-log graph taking frequency on x-axis and
 gain in dB on y-axis.

RESULT: Obtained And Verified the output of Cascade Amplifier.
 BW = 397 kHz

10/7/23


Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PAYANUR, KANNUR

Procedure	5
Conduction	4
Result	4
Viva	8
Record	4


La...
 HOD ELE

Circuit Diagram

1) Line Regulation

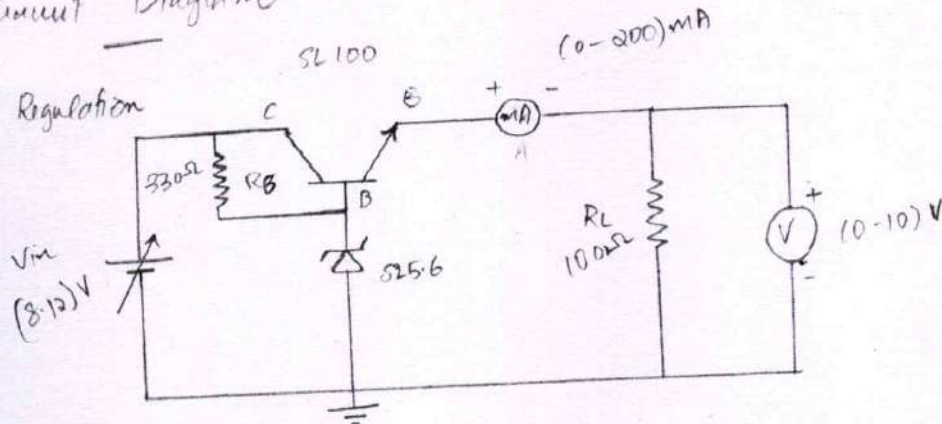

2) Load Regulation

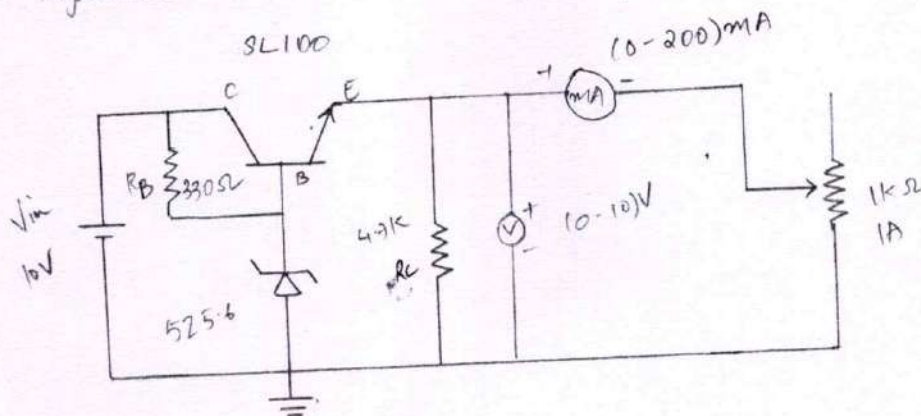

Design:

Since $I_C = 50\text{mA}$ SL100 is used. Nominal voltage of SL100 is $V_{CE} = 5\text{V}$,

$I_1 = 150\text{mA}$ $R_{FC} = 40-300$

Requirements: $V_{out} = 5\text{V}$, $I_L = 50\text{mA}$ $V_{in} = (8-12)\text{V}$

Solution of Zener diode: $I_{Z\min} = 10\text{mA}$ $I_{Z\max} = 30\text{mA}$

Solution of R_B :

$$R_{B\max} = \frac{V_{in\max} - V_Z}{(I_{Z\min}) + I_B} = \frac{12 - 5.6}{(10 + 0.7)\text{mA}} = 597.6\Omega$$

$$R_{B\min} = \frac{V_{in\min} - V_Z}{(I_{Z\max}) + I_B} = \frac{8 - 5.6}{(30 + 0.7)\text{mA}} = 76.6\Omega$$

$$R_B = (R_{B\max} + R_{B\min})/2 = 338\Omega \text{ (Use } 330\Omega)$$

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

SERIES VOLTAGE REGULATOR (TWO TRANSISTORS)

LINE AND LOAD CHARACTERISTICS

AIM:

To design and set up a series voltage regulator - line & load characteristics.

COMPONENTS AND EQUIPMENTS REQUIRED:

Transistor 2N3055, BC107	- 1, 1 No.
Resistor 470 Ω , 680 Ω , 390 Ω	- 1, 2, 1 No.
Rheostat 1k Ω	- 1 No.
Capacitor 0.1 μ F (2)	- 1 No.
Regulated Power supply 0-15V	- 1 No.
Ammeter (0-1A)	- 1 No.
Voltmeter (0-30)V	- 1 No.
Diode SZ5.6	- 1 No.
Bread Board	- 1 No.
CRO	
Connecting wires	

THEORY:

The circuit is quite similar to that of a simple transistor series voltage regulator except that transistor Q₂ is connected to the negative supply through a Zener diode. The base of transistor Q₁ is connected to the variable tap of a potentiometer.

Selection of R_L Load Regulation: $I_L = 1mA$

$$R_L = V_{out} / I_L = 5 / 1mA = 5k\Omega \quad \text{use } 4.7k\Omega$$

Selection of R_L (line regulation):

$$R_L = V_{out} / I_L = 5 / 1mA = 5k\Omega \quad \text{use } 4.7k\Omega$$

$$= 5 / 50mA = 100\Omega$$

Power rating of $R_L = I_L^2 R_L = (50mA)^2 \times 100 = 0.25W$ use $100\Omega, 0.25W$ resistor

1. Line Regulation

$V_{in} (V)$	$V_o (V)$
8V	4.70
9V	4.75
10V	4.77
11V	4.8
12V	4.83

2. Load Regulation

$I_L (mA)$	$V_o (V)$
5	5.36
10	5.34
20	5.33
30	5.33
40	5.33
50	5.31
60	5.31
70	5.29
80	5.29
90	5.29
100	5.28

Calculation:

Percentage line regulation:

$$= (\Delta V_{out} / \Delta V_{in}) \times 100$$

$$= \frac{4.83 - 4.7}{12 - 8} \times 100$$

$$= 0.0325 \times 100$$

$$= 3.25\%$$

Calculation:

Percentage load Regulation

$$= \frac{V_{NL} - V_{PL}}{V_{PL}} \times 100$$

$$= \frac{5.37 - 5.28}{5.28} \times 100$$

$$= 0.0174 \times 100$$

$$= 1.74\%$$

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR


This voltage regulator employs the principle of negative feedback to hold the output voltage almost constant despite variations in supply voltage and/or load current. The BJT transistor is the control element, is called the pass transistor. The voltage divider consisting of resistors R_1 and R_2 sample the output voltage and deliver a negative feedback.

Operation:


Suppose the output voltage increases, the voltage across R_2 is also increased as it is part of the output circuit. This causes an increase in voltage ($V_{BE2} + V_d$). As a result I_{B2} and I_{E2} increase. Assuming β relatively constant, I_B decreases. Decrease in base current of transistor Q_1 causes the increase in collector-emitter resistance of transistor Q_1 . This causes an increase in V_{CE1} thereby offsetting the increasing in output voltage. Therefore output voltage remains constant. Reverse happens should the output voltage decrease. The voltage V_d provided by $R_1 - R_2$ must be equal to the sum of the base-emitter voltage of transistor Q_2 and the Zener diode. Thus the regulated output voltage is equal to the closed-loop gain multiplied by the sum of Zener diode voltage and base-emitter voltage of transistor Q_2 . Like emitter follower regulator, this regulator also has the drawback of excessive power dissipation. This high-power dissipation output of limited to 30-40 W, as safe value of V_{CE} is 50V. Another drawback of this regulator is that it has no overload.

Observation

Line Regulation

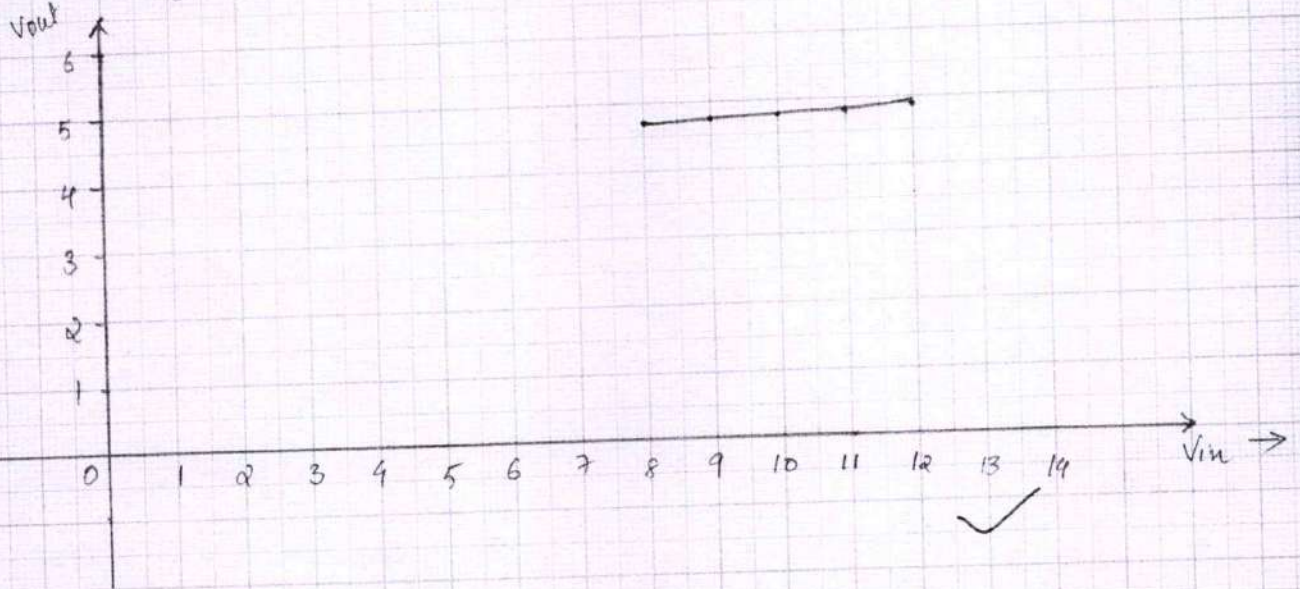

Load Regulation

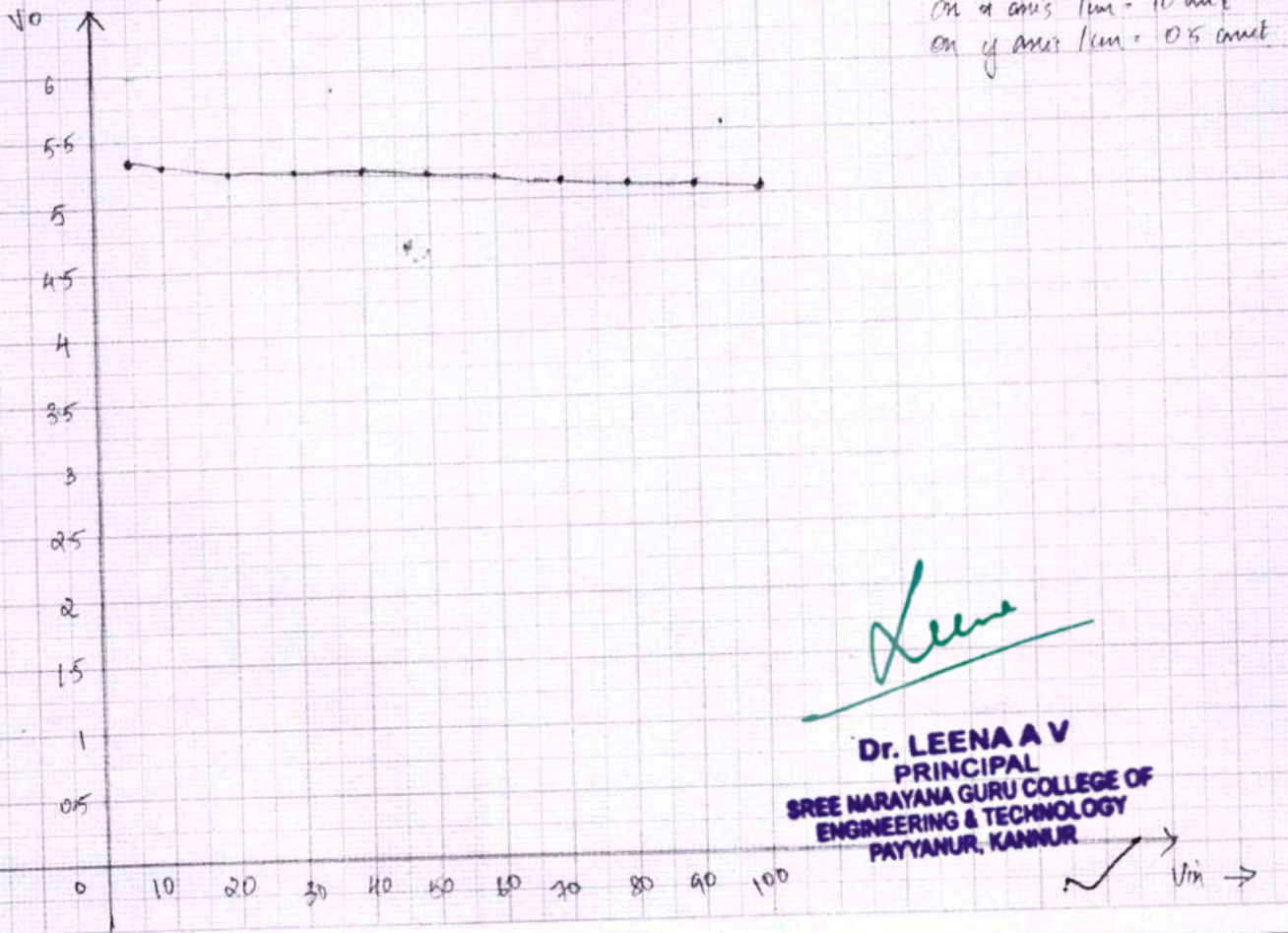

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Short circuit protection

PROCEDURE:

Line regulation:

1. Set up the circuit. Vary the input voltage and measure the corresponding output voltage.
2. Plot the V_o vs V_{in} which gives line regulation curve. From this, calculate the percentage line regulation factor using the expression.

Load Regulation:

1. Vary the load resistance and measure the load current and corresponding load voltage. Plot the load regulation graph.
2. Mark the no-load output voltage V_{NL} and full load output voltage V_{FL} on the graph. V_{NL} corresponds to voltage without load and full load means voltage at rated current.
3. Calculate the load regulation factor using the expression.
4. Calculate the output impedance using the expression.

RESULT:

Series voltage regulator circuit is set and stretched studied. plotted load & line regulation characteristics.

% line regulation = 8.25%
% load regulation = 1.704%

Dr. LEENA A V
PRINCIPAL

SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

HOD ECE

Procedure	5
Conduction	4
Result	4
Viva	7
Record	5

Teacher's Signature

FAMILIARISATION OF PSPICE SIMULATION SOFTWARE

AIM: To familiarize with PSPICE simulation software environment

THEORY:

ORCAD is a popular software tool suite used primarily for electronic design automation (EDA). The software is used mainly by electronic design engineers to create electronic schematic and electronic parts for manufacturing printed circuit board. The name ORCAD is a portmanteau, reflecting the company and its software design.

ORCAD is a suite of products for EDA and includes a schematic editor, a circuit simulator and a PCB designer. ORCAD capture.

ORCAD is a schematic capture application, and part of the ORCAD circuit design suite. Capture is a design entry program you need to prepare your circuit for simulation.

When the simulation process begins, capture first generate files describing the parts and connections in the circuit. These files are the netlist file and the circuit file. Capture imports netlist data to the simulator. ORCAD EE capture can also export a hardware description of the circuit. ORCAD EE PSpice.

The simulation program with integrated circuit Emphasis (PSpice) became an industry standard for circuit simulation. The PC-compatibility standard for

DR. JEEENA A V
PRINCIPAL
BREEHARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY (PCE)
PAYANUR, KANNUR

hac. Pspice is an acronym for personal simulation program with Integrated Circuit Emphasis. Pspice was a modified version of the academically developed SPICE, and was commercialized by Microsim in 1989.

ACAD EE Pspice is a SPICE circuit simulation application for simulation and verification of analog and mixed signal circuit. Pspice can be together thought of as a software based breadboard of your circuit that you can use to test and refine your design before ever touching a piece of hardware. A circuit is to be analysed using Pspice is described by a circuit description file, which is processed by Pspice and executed as a simulation. Pspice create an output file to store the simulation results, and such results are also graphically displayed within the ACAD EE interface. Pspice uses high-resolution graphics so you can view the result of a simulation both on the screen and in printed form.

Analyses:

This type of simulation performed by Pspice depends on the source specification and control statements.

- DC Analysis :- It is used for circuits with time invariant source. It calculate all nodal voltage and branch current over a range of values. Supported types include linear sweep, logarithmic sweep and sweep over list of values.

- Transient Analysis :- It is used for circuit with time variant source.

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

- **AC Analysis:** It is used for small signal analysis of circuit with source of varying frequencies. It calculates the magnitude and phase angle of all nodal voltages and branch current over a range of frequencies.

Minimum requirement to run a DC sweep analysis:

- Voltage source with a DC specification
- Current source with a DC specification

Minimum requirement to run a transient analysis:

- An independent source with a transient specification
- An initial condition on a reactive element
- A controlled source that is a function of time

Pspice Output file:

The Pspice output file is an ASCII text file that contains:

- The netlist representation of the circuit
- The Pspice command syntax for simulation command and options
- simulation results and
- warning and error message for problems encountered during
- read in or simulation.
- the type of analysis you run
- the option you select for running Pspice

Pspice circuit file:

A Pspice circuit description file contains the configuration data for circuit simulation.

ORCAD EE Pspice simulator. The circuit file contains the component netlist, simulation option, analysis statement, and the output control statement - The component netlist comprises a list of all circuit elements, along with the node names connected to their terminals.

Circuit files:

The file contains 5 types of statements:-

- The Title
- Device Statements
- Control statements
- Comment lines
- The End statement

Steps for circuit analysis:

There are 4 main steps involved in circuit simulation using Pspice.

Step 1: Creating New Project and Schematic Diagram.

Step 2: Selecting circuit components connecting them together and setting components.

Step 3: Creating a new simulation Profile and setting up the simulation.

Step 4: Simulating the circuit and observing the simulation results.

To create a New Pspice Project:

1) From the window start menu choose the ORCAD 16.0 program folder and there the ORCAD PRINCIPAL to start capture.

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Teacher's Signature

- 2) Make a project [File] → [New] → [Project] Name the project and choose Analogue as kind of location
- 3) Select [Place] → [Part] Place necessary circuit components.
- 4) Find the part you want to add and press Ok.
- 5) Click where you want to place the part on your schematic.
- 6) When you are finished with the part, right click and select End Node to return to the pointer.
- 7) Select Parts ⇒ Wire. The pointer changes to non-hack.
- 8) Drag mouse from one connection point to another clicking on any valid connection wire end the wire.
- 9) When you are finished, right click the mouse and select End Wire to return to the pointer.
- 10) 10) PSpice uses node-voltage method for circuit simulation and therefore, need a reference node with (Zero Voltage)
- 11) To change a part's value double click the value of the part.
- 12) Abuses can be used to take the input and output modes.
- 13) Set up the required analysis [PSpice] → [New Simulation Profile] Name the new profile
- 14) After the parameters are set you can start simulation from capture in either following ways:-
 - From the PSpice menu select Run
 - Click the simulate button on the PSpice toolbar.
- 15) A new window will pop up that can display what PSpice calls traces. If the desired trace is not displayed then click [Trace] → [Add Trace].

RESULT: PSpice simulation software environment is familiarized.


Dr. LEENA V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR.

Teacher's Signature


HOD ECE

RC DIFFERENTIATING AND INTEGRATING CIRCUITS

CIRCUIT DIAGRAM:

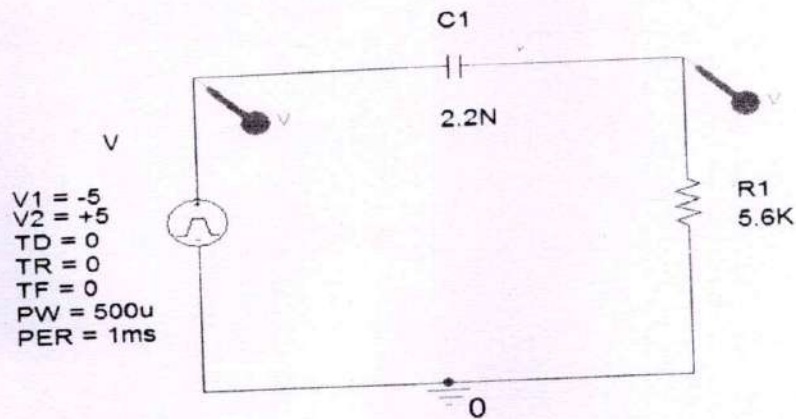

Profile Settings:

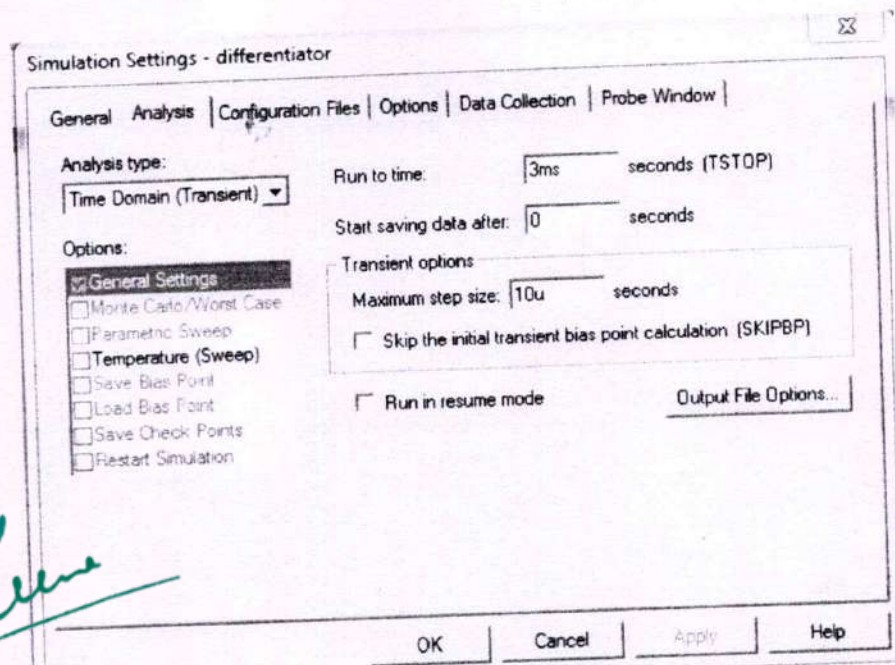

Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

RC DIFFERENTIATOR AND INTEGRATING CIRCUITS.


AIM: To verify and simulate input and output waveform of RC differentiator and Integrating circuits.

EQUIPMENTS REQUIRED:

PC installed with ORCAD simulation software.


PROCEDURE 1:-

1. Create a new project and a new schematic page.
2. Place the necessary circuit components and source select the circuit ground.
3. Set up the required analysis in the simulation setting window.
4. Under the Analysis type, select time domain sweep select general setting option. Set the run to time and maximum step size values. Then save the simulation profile.
5. After the parameter are set you can start simulation by selecting Run option.
6. The input and output waveform of circuit will be shown in the graph. Observe the graph.

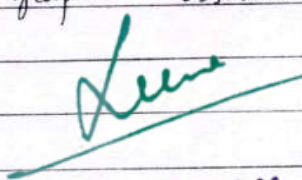

Dr. LEENA A V
PRINCIPAL

SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Observation:

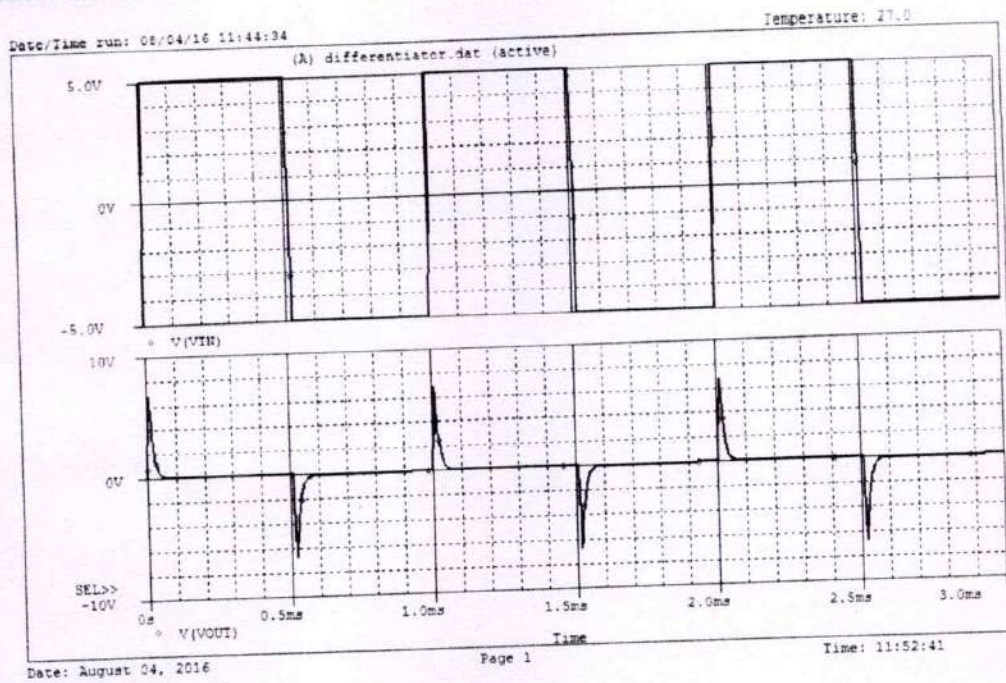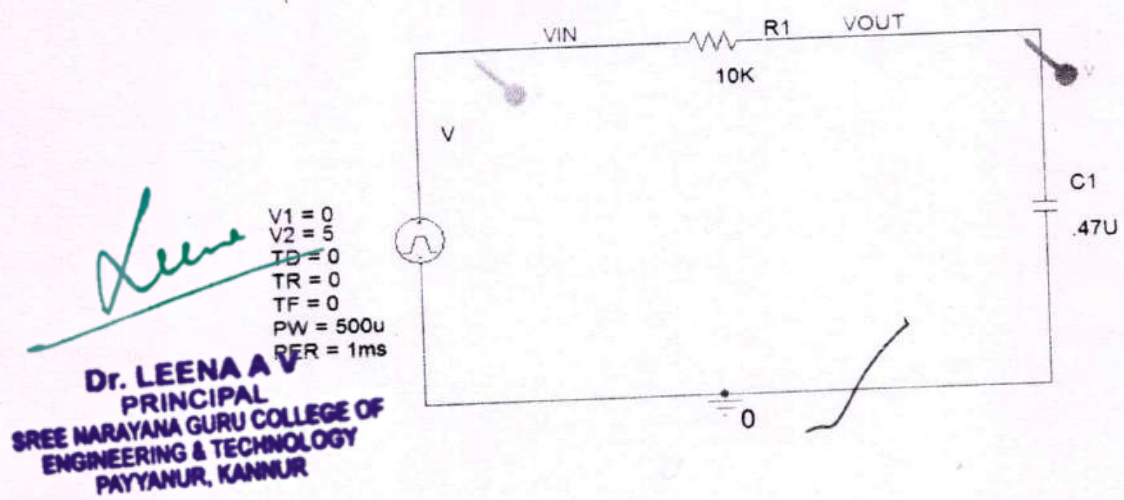


CIRCUIT DIAGRAM:



PROCEDURE 2:

1. Create a new project and a new schematic page
2. Place the necessary circuit components and source. Select the circuit ground. Interconnect the components using wires.
3. Set up the required analysis in the simulation setting window.
4. Under the analysis type - select time domain (transient) sweep. Select General setting option. Set the run to time and maximum step size values. Then save the simulation profile.
5. After the parameters are set you can start simulation by Run option.
6. The input and output waveform of circuit will be shown in the graph. Observe the graph.

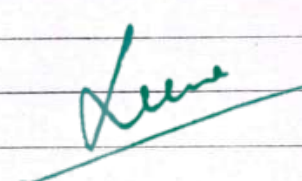
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

Profile Settings:

Simulation Settings - INTERGRATOR2

General Analysis Configuration Files Options Data Collection Probe Window

Analysis type:
 Time Domain (Transient) ▼

Run to time: 100m seconds (TSTOP)
 Start saving data after: 95m seconds

Options:

- ☒ General Settings
- ☐ Monte Carlo/Worst Case
- ☐ Parametric Sweep
- ☐ Temperature (Sweep)
- ☐ Save Bias Point
- ☐ Load Bias Point
- ☐ Save Check Points
- ☐ Restart Simulation

Transient options

Maximum step size: 10u seconds


☐ Skip the initial transient bias point calculation (SKIPBP)

☐ Run in resume mode

Output File Options...

OK Cancel Apply Help

Observation:

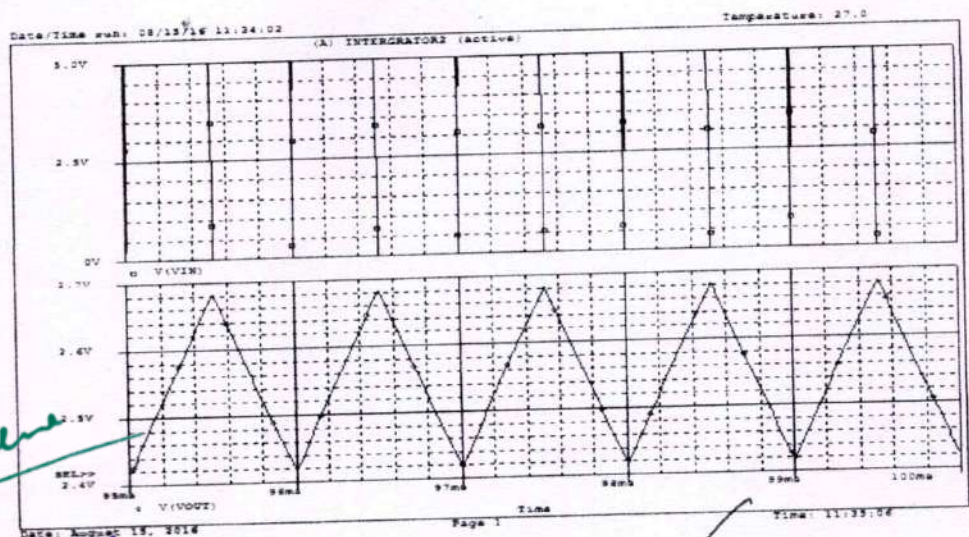


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Experiment Name / No.: _____

Camlin Page No. 42


Date / /

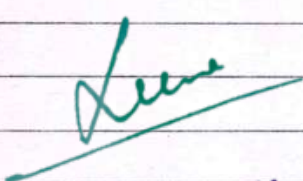
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR


25 RESULT : Verified and obtained the output waveform of RC differentiator and Integrator circuit using PSPICE software.

Procedure	5
Conduction	5
Result	5
Viva	9
Teacher's Signature	5


HOD ECE

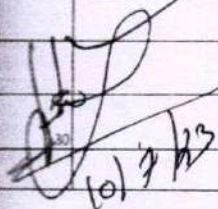
10/7/23

positive clipper

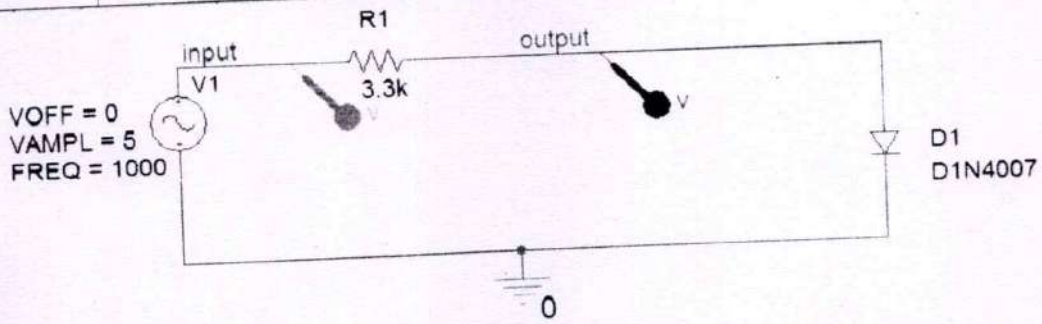

Simulation Settings - positive clipper

General Analysis Configuration Files Options Data Collection Probe Window

Analysis type: Time Domain (Transient)

Run to time: 3m seconds (TSTOP)

Start saving data after: 0 seconds

Options:

☒ General Settings

☐ Monte Carlo/Worst Case

☐ Parametric Sweep

☐ Temperature (Sweep)

☐ Save Bias Point

☐ Load Bias Point

☐ Save Check Points

☐ Restart Simulation


Transient options

Maximum step size: 10u seconds

☐ Skip the initial transient bias point calculation (SKIPBP)

☐ Run in resume mode

Output File Options...

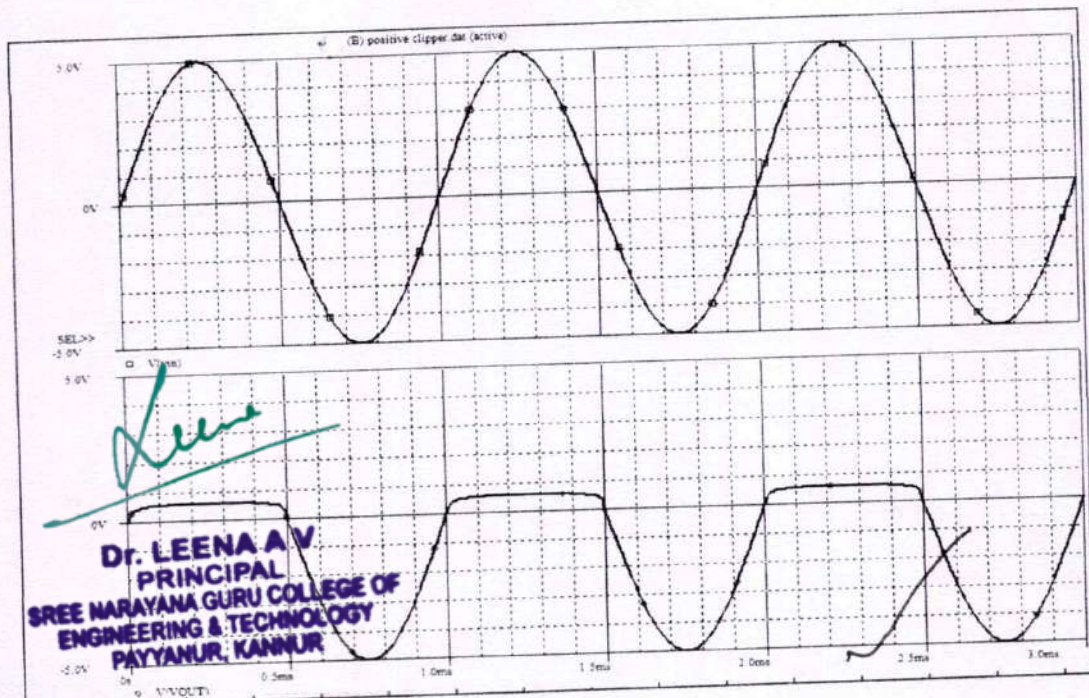

CLIPPING CIRCUITS

AIM:

To verify and simulate the input and output waveform of clipper circuit.


EQUIPMENTS REQUIRED:

PC installed with CREAD simulation software.


PROCEDURE:

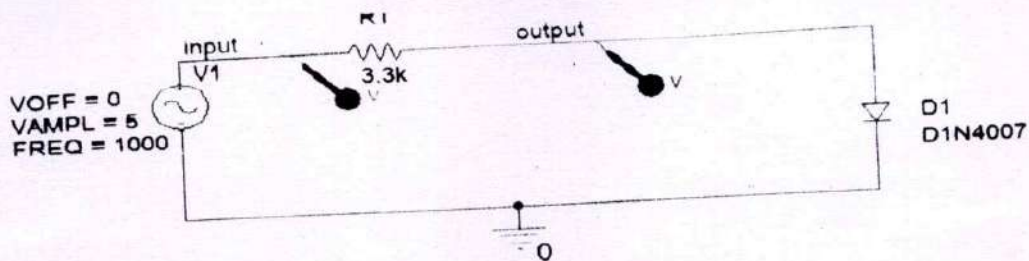1. Create a new project and a new schematic page
2. Place necessary circuit components and some selected the circuit ground interconnect the component using wire tool. After that place current probe at the resistor
3. Set up the required analysis in the simulation setting window
4. Under Analysis the time delay step select general setting option. Set the run to time and maximum step size values. Then click "Apply" and OK to save the simulator profile
5. After the parameter are set you can start simulation by selecting run option

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR



Negative clipper

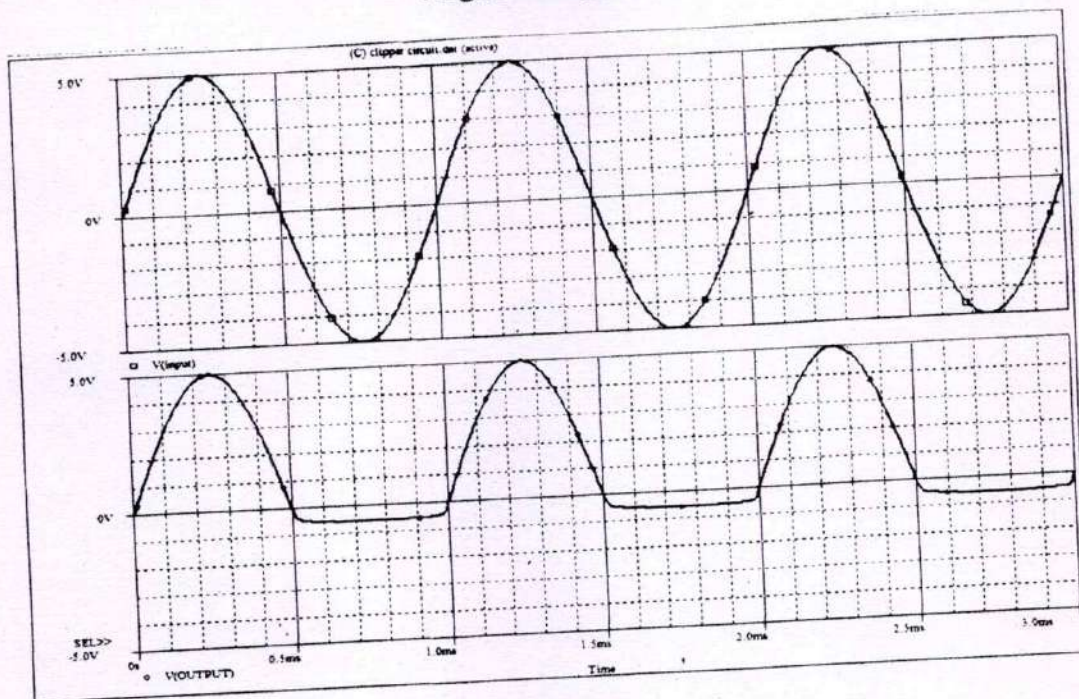

Simulation Settings

General Analysis Configuration Files Options Data Collection Probe Window

Analysis type:
Time Domain (Transient)

Run to time: 3m seconds (TSTOP)

Start saving data after: 0 seconds

Options:

General Settings

☐ Monte Carlo/Worst Case

☐ Parametric Sweep

☐ Temperature (Sweep)

☐ Save Bias Point

☐ Load Bias Point

☐ Save Check Points

☐ Restart Simulation

Transient options

Maximum step size: 10u seconds

☐ Skip the initial transient bias point calculation (SKIPBP)

☐ Run in resume mode

Output File Options...

OK Cancel Apply Help

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

6. Input and output waveform will be shown in the graph - Observe the graph.


10 RESULT: Verified and obtained the output waveform of diode circuit using PSPICE software.

10/11/23

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Procedure	5
Conduction	5
Result	5
Viva	8
Record	5

HOD EEE

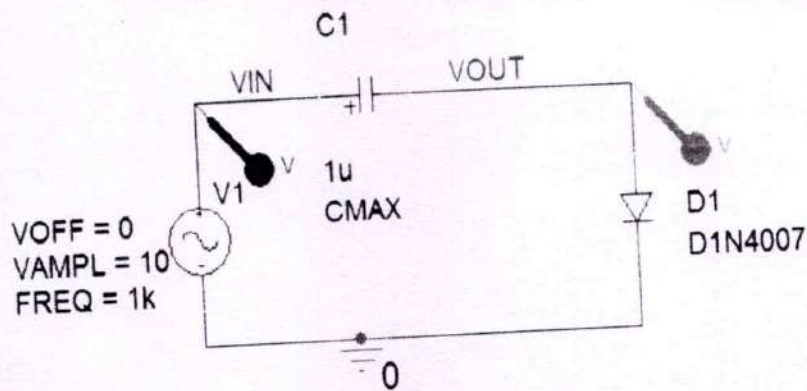

Simulation Settings - NEGATIVE CLAMPER

General Analysis Configuration Files Options Data Collection Probe Window

Analysis type: Time Domain (Transient)

Run to time: 3ms seconds (TSTOP)

Start saving data after: 5m seconds

Options:

☒ General Settings

☐ Monte Carlo/Worst Case

☐ Parametric Sweep

☐ Temperature (Sweep)

☐ Save Bias Point

☐ Load Bias Point

☐ Save Check Points

☐ Restart Simulation

Transient options

Maximum step size: 10u seconds


☐ Skip the initial transient bias point calculation (SKIPBP)

☐ Run in resume mode

Output File Options...


OK Cancel Apply Help

Temperature: 27.0

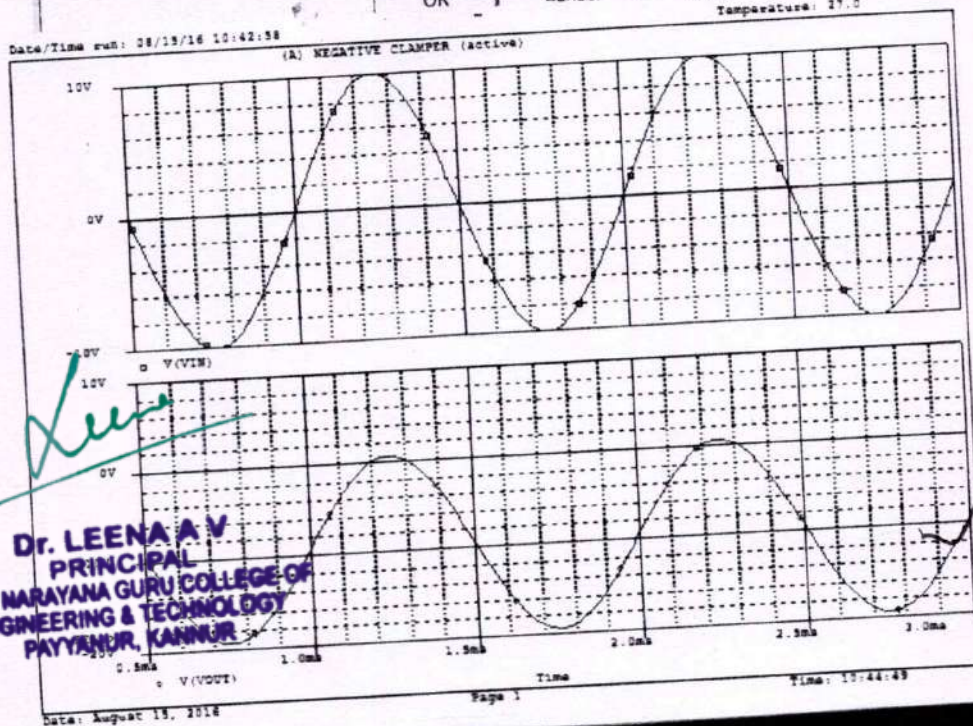

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

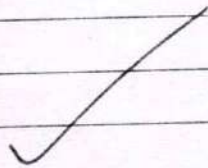6) Input and output waveform will be shown in the graph. Observe the graph.



15 RESULT: Verified the input and output waveform of both positive and negative clamper using PSPICE software.

20
10/7/23

25
Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

Procedure	5
Conduction	5
Result	5
Viva	8
Record	5

Leena
HOD ECE

Simulation Settings - rc freq

General Analysis Configuration Files Options Data Collection Probe Window

Analysis type:

AC Sweep/Noise

Options:

- ☒ General Settings
- ☐ Monte Carlo/Worst Case
- ☐ Parametric Sweep
- ☐ Temperature (Sweep)
- ☐ Save Bias Point
- ☐ Load Bias Point

AC Sweep Type

☐ Linear

☒ Logarithmic

Decade

Start Frequency: 10

End Frequency: 4e9

Points/Decade: 10

Noise Analysis

☐ Enabled

Output Voltage

I/V Source

Interval

Output File Options

☐ Include detailed bias point information for nonlinear controlled sources and semiconductors (.OP)

OK

Cancel

Help


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Experiment Name / No.:

Camlin

Page No.

48

Date

/

/

5

10

15

20

25

RESULT:

Simulated

DI. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Frequency response of RC coupled amplifier was
simulation software


Procedure	5
Conduction	5
Result	5
viva	8
Teacher's Signature:	5

10/7/23


Signature

HOD ECE

CIRCUIT DIAGRAM

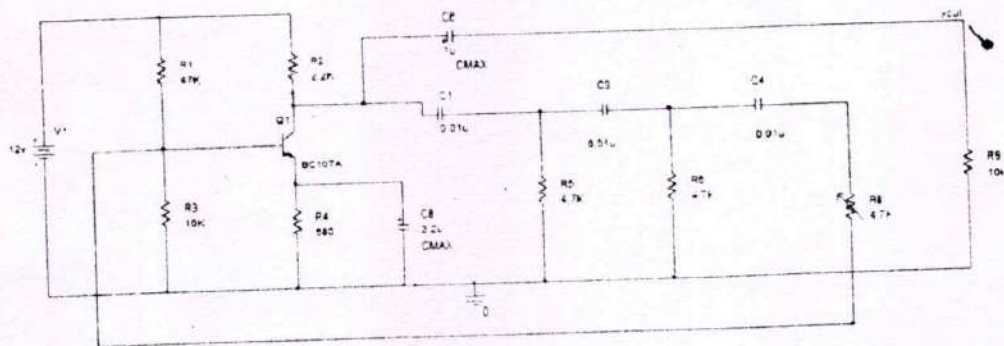

SIMULATION PROFILE

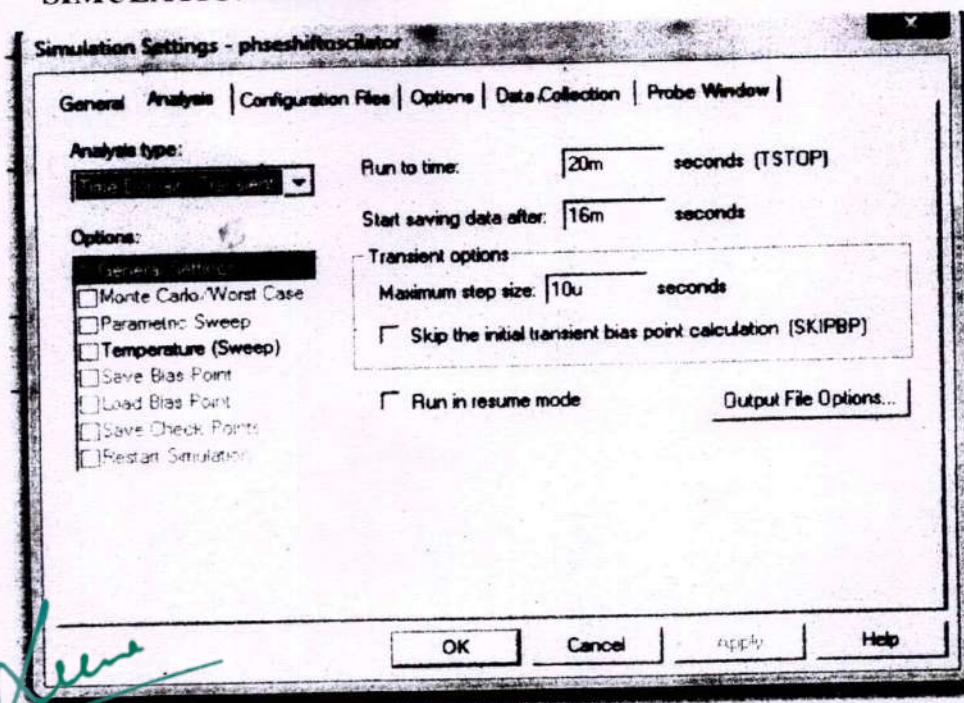

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

RC PHASE SHIFT OSCILLATOR

AIM:

To verify and simulate the RC phase shift oscillator.

EQUIPMENT REQUIRED:


PC installed with ORCAD simulation software

PROCEDURE:

1. Create a new project and a new schematic page for both units.
2. Place the circuit components and source select the circuit ground. Interconnect using wire tool.
3. Setup the required analysis in the simulation setting window.
4. Under Analysis type, Time domain sweep - select general setting option.
5. Set the run to time and maximum steps size values. Then save the simulation profile.
6. After the parameter are set you can run simulation by selecting Run option.

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

OUTPUT

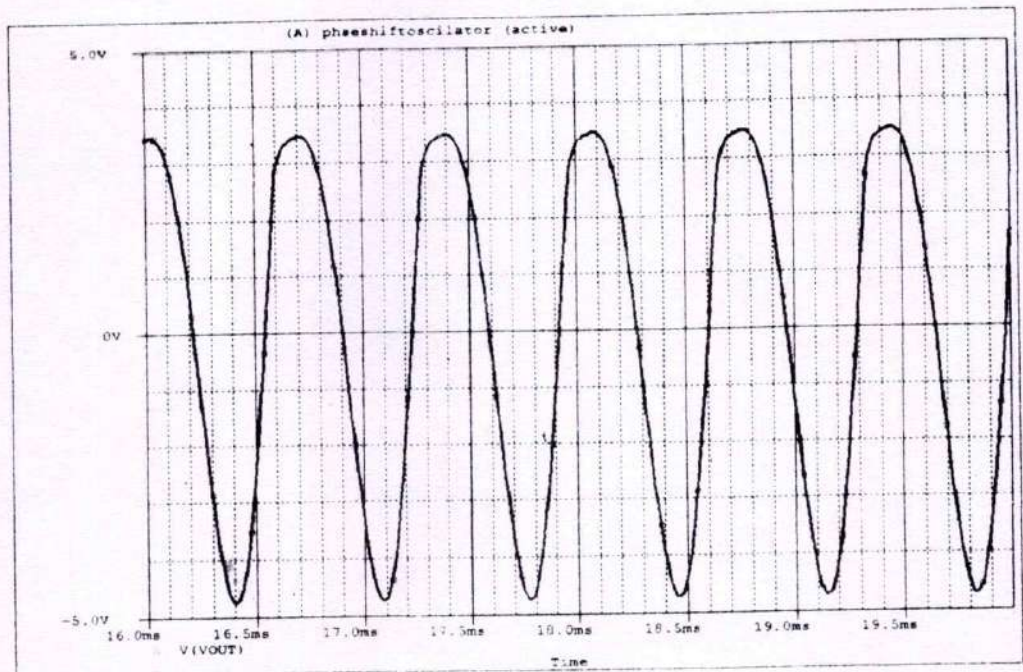


RESULT: RC Phase Shift Oscillator was simulated using PSPICE simulation software.

Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Experiment Name / No.:

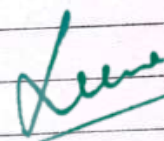7. Output waveform will be shown in the graph observe the graph.




Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

25. RESULT: RC phase shift oscillator was simulated using
Prote simulation software


Procedure	5
Conduction	5
Result	5
Viva	9
Teacher's Signature	5
Record	



HOD ECE

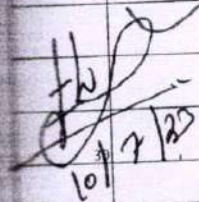

CIRCUIT DIAGRAM

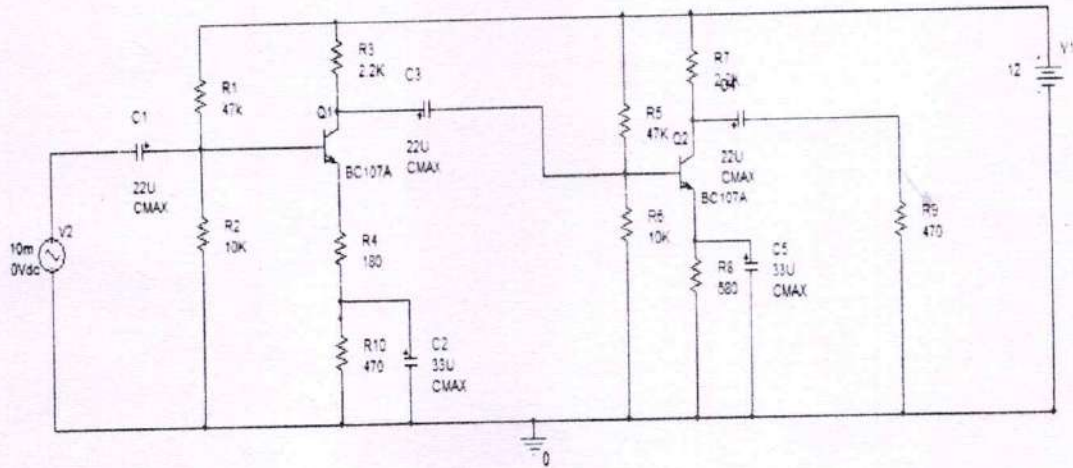

SIMULATION RESULTS

Simulation Settings - CASCADE

General Analysis Configuration Files Options Data Collection Probe Window

Analysis type:
☒ AC Sweep/Noise

Options:
☒ General Settings
☐ Monte Carlo/Worst Case
☐ Parametric Sweep
☐ Temperature (Sweep)
☐ Save Bias Point
☐ Load Bias Point

AC Sweep Type
☐ Linear
☒ Logarithmic
 Decade

Start Frequency: 10
 End Frequency: 1e9
 Points/Decade: 10

Noise Analysis
☐ Enabled
 Output Voltage:
 I/V Source:
 Interval:
☐ Include detailed bias point information for nonlinear controlled sources and semiconductors (.OP)

Output File Options
☐ Include detailed bias point information for nonlinear controlled sources and semiconductors (.OP)

OK Cancel Apply Help

Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

CASCAD AMPLEPER

AIM:

To vary and simulate the input and output waveform of positive and negative clamper circuits.


EQUIPMENT REQUIRED:

PC installed with ORCAD Simulation software.

PROCEDURE:

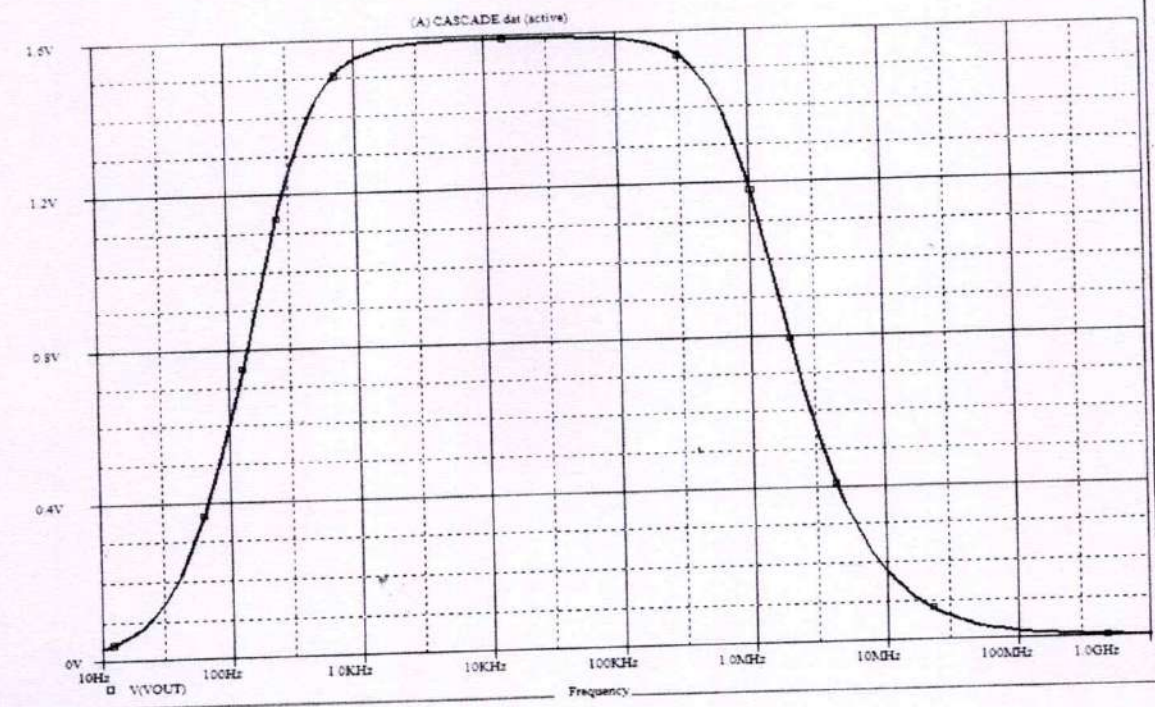1. Create a new project and a new schematic page.
2. Place necessary circuit components and source select the circuit ground. Interconnect the components using wire tool.
3. Set up required analysis in the simulation setting window.
4. Under Analysis type. Select a sweep. enter message parameter value for logarithmic sweep. Then click "Apply" to save the simulation profile.
5. After the parameter are set you can run the simulation by selecting Run option.

Dr. LEENA A V
PRINCIPAL Simulation
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR



Leena


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Experiment Name / No.:

Camlin Page No. 52

Date / /


6. Input and Output waveform will be shown on the graph. Observe the graph.

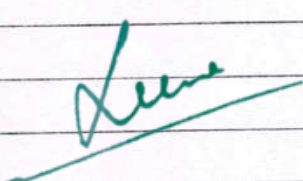
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Procedure	5
Conduction	5
Result	5
Viva	9
Recd.	5

25 RESULT:

Frequency response of Cascade Amplifier was simulated using Pspice software.

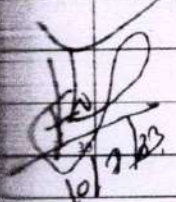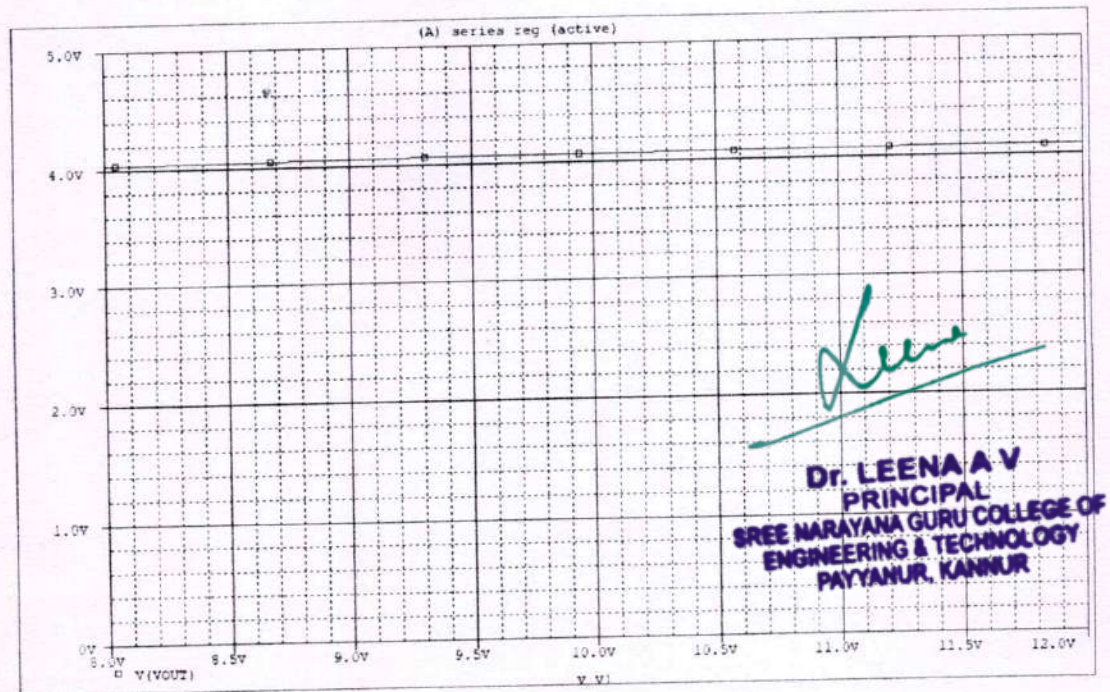
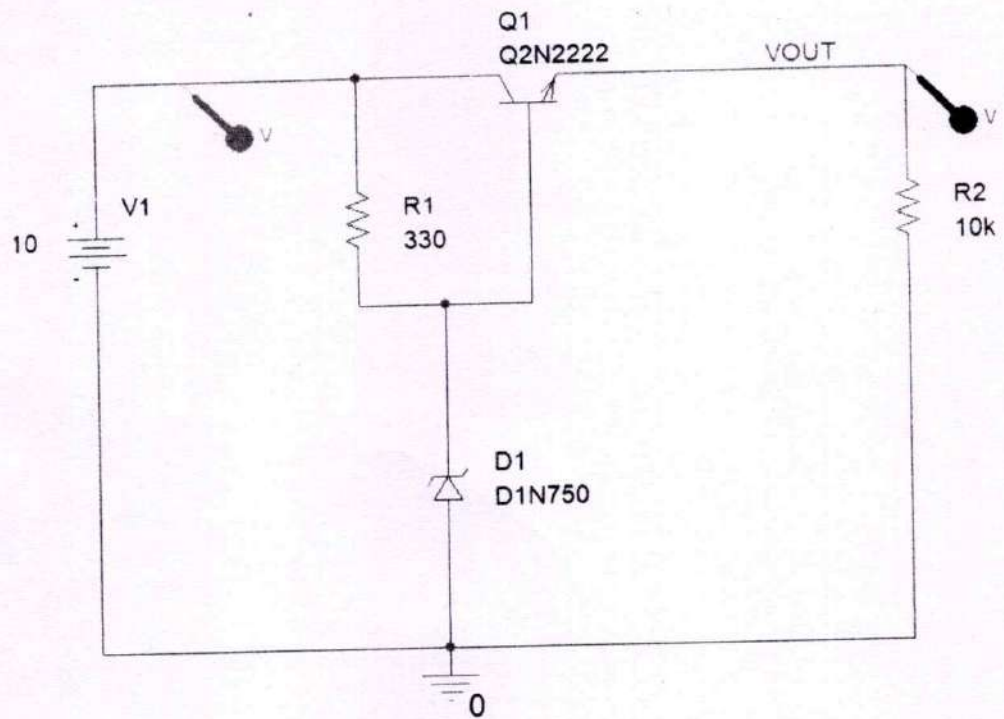

10/12/23



HOD ECE

Teacher's Signature

LINE REGULATION



SERIES VOLTAGE REGULATOR

AIM:

To verify and simulate a series voltage regulator - line and load characteristics.

EQUIPMENT REQUIRED:-


PC installed ORCAD simulation software.

PROCEDURE:

1. Create a new project and a new schematic page.
2. Place necessary circuit components and source. Select the circuit ground. Interconnect the components using wires.
3. Set up the required analysis in the simulation setting window.
4. Under Analysis type, select DC sweep. Enter necessary parameter values (start, end and increment values for linear sweep type). Then click "Apply" to save the simulation profile.
5. After the parameter are set go to simulation by clicking Run option.

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

VOLTAGE LOAD REGULATOR

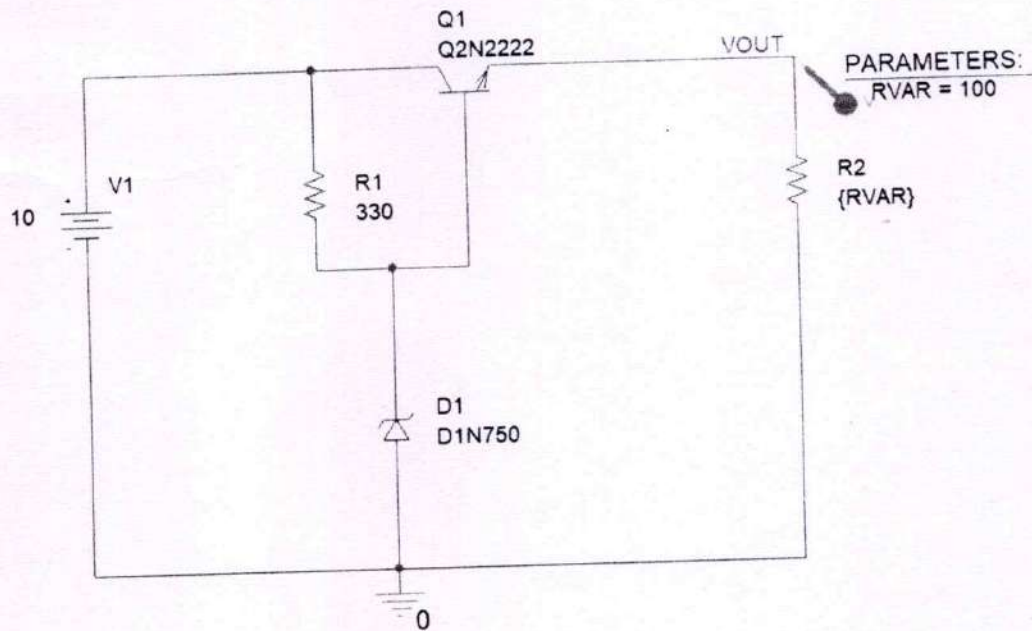

Simulation Settings - series reg

General Analysis Configuration Files Options Data Collection Probe Window

Analysis type:

DC Sweep

Options:

- ☒ Primary Sweep
- ☐ Secondary Sweep
- ☐ Monte Carlo/Worst Case
- ☐ Parametric Sweep
- ☐ Temperature (Sweep)
- ☐ Save Bias Point
- ☐ Load Bias Point

Sweep variable

- ☐ Voltage source
- ☐ Current source
- ☒ Global parameter
- ☐ Model parameter
- ☐ Temperature

Name: V1

Model type:

Model name:

Parameter name: RVAR

Sweep type

- ☒ Linear
- ☐ Logarithmic
- ☐ Value list

Decade

Start value: 10

End value: 1000

Increment: 5

OK

Cancel

Apply

Help

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Experiment Name / No.:

5. Enter necessary parameter values. Then click "Apply" to save the simulation profile.

6. After the parameters are set, you can start a simulation by selecting Run option.

7. Waveform will be shown in the graph observe the graph.

8. On the output waveform click the option plot → Axis setting → Y axis → user defined (select the data range 0 to 5V).

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

Axis Settings

X Axis Y Axis X Grid Y Grid

Data Range

- ☐ Auto Range
☒ User Defined

0 to 5V

Scale

- ☒ Linear
☐ Log

Y Axis Number

1

Axis Position

- ☒ Left
☐ Right

Axis Title

1


OK

Cancel

Save As Default

Reset Defaults

Help

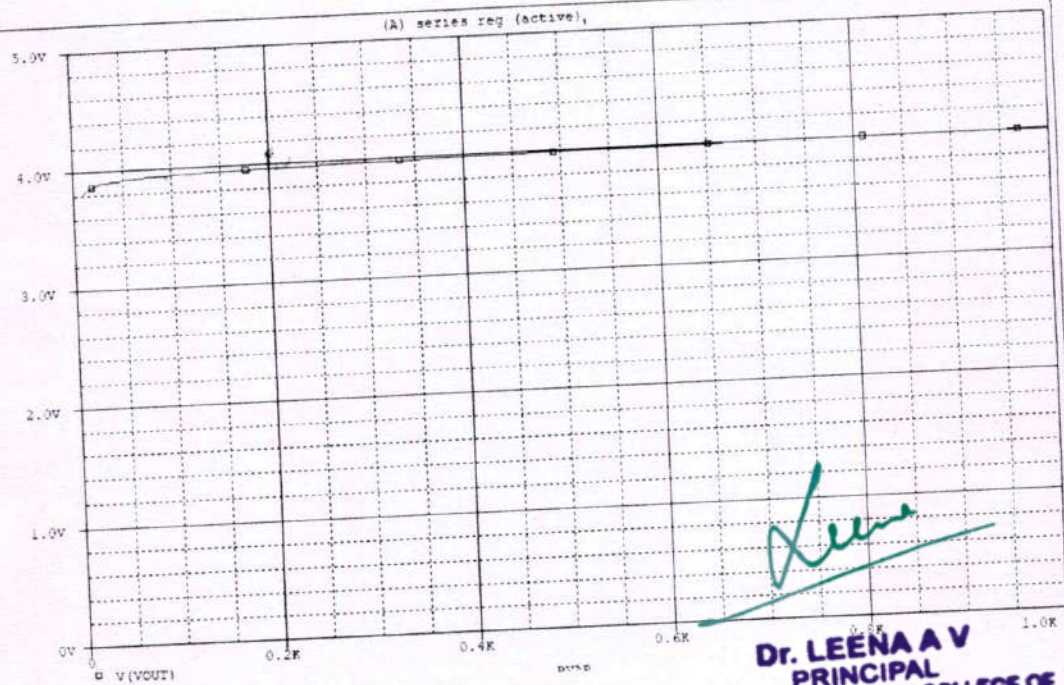


Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Experiment Name / No.:

Camlin Page No. 56


Date / /

RESULT: Verified And simulated series voltage regulator using
PSICE software.

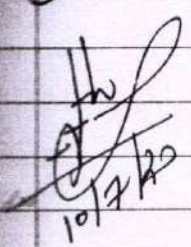
10/7/22

Procedure	5
Conduction	5
Result	5
Viva	9
Record	5


HOD ECE

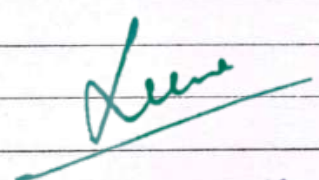
DR. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Teacher's Signature:

2

Completed

all

experiments

certify and

Verify By


10/7/23


Thrishna. S
Assistant Professor
ECE
Sree Narayana Guru College of Engineering & Technology, Payyanur




Dr. LEENA A. V.
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY, PAYYANUR
KANNUR



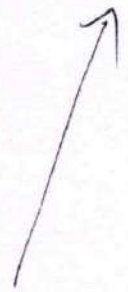
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR



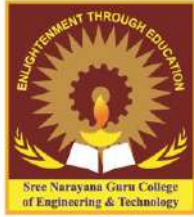


Sree Narayana Guru College of Engineering & Technology

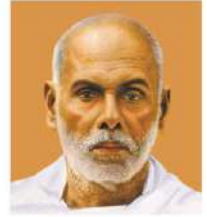CHALAKKODE P.O., KOROM, PAYYANUR, KANNUR-670 307



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

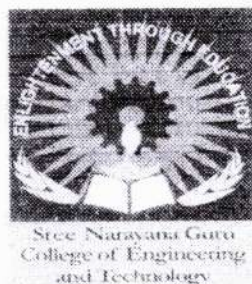**SREE NARAYANA GURU
COLLEGE OF ENGINEERING & TECHNOLOGY
PAYYANUR – 670 307**



CERTIFICATE

Name.....HRUDHUL RAGH.....
Semester.....55..... Branch.....EEE.....
Roll No.....3..... Uni. Reg. No.....

Certified that this is a Bonafide Record of the work done in the **EEL 331 MICROPROCESSORS**

MICRO CONTROLLERS LAB of Sree Narayana Guru College of Engineering & Technology, Payyanur by

Mr. / Miss. **HRUDHUL RAGH**

Place : **Payannur**

Date : **03/02/2023**

Internal Examiner

Vasbakh. M. Nigam
AP, EEE SNGCET
16/02/23


Dr. Leena A. V.
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY, PAYYANUR


Staff Member in charge

External Examiner


SUTHI D.K
AP, EE, CETKR
16/02/23

INDEX

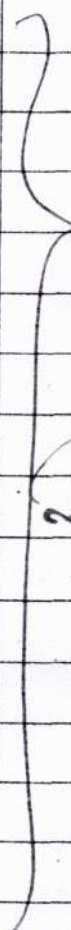Sl. No.	Name of Experiment	Date	Page No.	Initial of Teacher
1	ARITHMETICS OPERATIONS USING 8085 MICRO PROCESSOR [8 BIT]	19/09/22	1 - 5	
2	ARITHMETIC OPERATIONS USING 8085 MICROPROCESSOR [16-BIT]	20/09/22	6 - 8	
3	SEARCH FOR SMALLEST AND LARGEST DATA IN AN ARRAY	10/10/22	9 - 10	
4	SORTING AN ARRAY IN ASCENDING ORDER	17/10/22	11 - 12	
5	BCD TO BINARY CONVERSION	01/11/22	13 - 14	
6	ADDITION OF AN ARRAY OF DATA	14/11/22	15 - 16	
7	FAMILIARIZATION OF ARDUINO IDE	21/11/22	17 - 20	
8	LED CONTROL USING ARDUINO	28/11/22	21 - 22	
9	DC MOTOR SPEED CONTROL USING ARDUINO	05/12/22	23 - 24	
10	VOLTAGE MEASUREMENT USING ARDUINO	12/12/22	25 - 26	
11	ARITHMETIC OPERATIONS USING 8051	19/12/22	27 - 29	
12	SEARCH FOR LARGEST DATA IN AN ARRAY	03/01/23	30 - 31	
13	HEXADECIMAL TO DECIMAL CONVERSION	09/01/23	32 - 33	

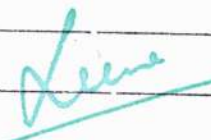

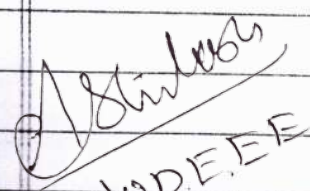Dr. LEENA A. V.
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY, PATTANUR
KANNUR



HADEE

PROGRAM :
(ADDITION)

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENTS
4100	8A 00 42		LDA 4200 H	Get 1st data in A and save in B
4103	47		MOV B, A	
4104	3A 01 42		LDA 4201 H	Get 2nd data in A register.
4107	0E 00		MVI C, 00H	Clear C register to account for carry
4109	80		ADD B	Get the sum in A register.
410A	D2 0E 41		JNC AHEAD	if CF=0, go to AHEAD
410D	0C		INR C	if CF=1, increment C- register.
410E	82 02 42	AHEAD	STA 4202 H	Store the sum in memory.
4111	79		MOV A, C	
4112	32 03 42		STA 4203 H	Store the carry in memory
4115	76		HLT	Halt program Execution


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

EXPERIMENT - 01

19/09/22

ARITHMETICS OPERATIONS USING 8085 MICROPROCESSOR [8-BIT]

01

AIM :

- i) Write an assembly language program to add two numbers of 8 bit data stored in memory locations 4200H and 4201H and store the result in 4202H and 4203H
- ii) Write an assembly language program to subtract two numbers of 8-bit data stored in memory 4200H and 4201H. Store the magnitude of results in 4202H. If the result is positive store 00 in 4203H or if the result is negative store 01 in 4203H
- iii) Write an assembly language program to multiply two numbers of 8-bit data stored in memory 4200H and 4201H and store the product in 4202H and 4203H
- iv) Write an assembly language program to divide two numbers of 8 bit data stored in memory locations 4200H and 4201H. Store the quotient in 4202H and the remainder in 4203H

Algorithm (Addition)

1. Load the first data from memory to accumulator and move it to B register.
2. Load the second data from memory to accumulator.
3. Clear C register.
4. Add the content of B register to accumulator.
5. Check the carry. If carry = 1, go to step 6 or if carry = 0, go to step 7
6. Increment the C-register.

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

PROGRAM

SUBTRACTION

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENTS
4100	3A 01 42		LDA 4201 H	
4103	47		MOV B,A	Get the subtracted in B-register.
4104	3A 00 42		LDA 4200H	Get the minuend in A register.
4107	0E 00		MVI C, 00H	Clear the Cregister to account for sign
4109	90		SUB B	Get the difference in A register.
410A	02 11 41		JNC AHEAD	IF CF=0, then go to AHEAD.
410D	0C		INR C	IF CF=1 then increment Cregister
410E	2F		CMA	Get 2's complement of difference
410F	C6 01		ADI 01H	(result) in A register
4111	32 02 42	AHEAD	STA 4202 H	Store the result in memory
4114	79		MOVA,C	
4115	32 03 42		STA 4203 H	Store the sign bit in memory
4118	76		HLT	Halt program execution

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

7. Store the sum in memory
8. Move the carry to accumulator and store in memory.
9. Stop.

Algorithm (Subtraction)

1. Load the subtrahend (data to be subtracted) from memory to accumulator and move it to B-register.
2. Load the minuend from memory to accumulator.
3. Clear C register to account for sign of the result.
4. Subtract the content of B register (subtrahend) from the content of accumulator (minuend).
5. Checks for carry. If carry=1, go to step 6 or if carry=0, go to step 7.
6. Increment C register. Complement the accumulator and add 1.
7. Store the difference (accumulator) in memory.
8. Move the content of C-register (signbit) to accumulator and store in memory.
9. Stop.

Algorithm (Multiplication)

1. Load the address of the first data in HL pair (pointer)
2. Clear C-register for overflow (carry).
3. Clear the accumulator.
4. Move the first data to B register [Count].
5. Increment the pointer.
6. Move the second data to D-register (multiplier).
7. Add the content of D-register to accumulator.

Leena
Dr. LEENA A V
 PRINCIPAL
 SHREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PAYANUR, KANNUR

PROGRAM

MULTIPLICATION

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENTS
4100	21 00 42		LXI H, 4200H	Specify program starting address
4103	0E 00		MVI C, 00H	Clear C to account for overflow (carry)
4105	AF		XRA A	Clear Accumulator
4106	46		MOV B, M	Get 1st data in B register
4107	23		INX H	
4108	56		MOV, D, M	Get second data in D register
4109	82	REPT:	ADD D	ADD D register to accumulator
410A	D2 0E 41		JNC AHEAD	
410D	0C		INR C	IF CF=1, increment C register
410E	05	AHEAD:	DCR B	
410F	C2 09 41		JNZ REPT	Repeat addition until ZF=1
4112	23		INX H	
4113	77		MOV M, A	Store low byte of product in memory.
4114	23		INX H	
4115	77		MOV M, A	Store high byte of product in memory.
4116	76		HLT	Execution

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

8. Check the carry. If $\text{carry} = 1$, go to step 9 or if $\text{carry} = 0$, go to step 10
9. Increment C register
10. Decrement B-register (count).
11. Check whether count has reached zero. If $ZF = 0$ repeat steps 7 through 11, or if $ZF = 1$ go to next step.
12. Increment the pointer and store low byte of the product in memory.
13. Increment the pointer and store high byte of the product in memory.
14. Stop.

Algorithm (Division)

1. Load the divisor in accumulator and move it to B register
2. Load the Divident in accumulator.
3. Clear C-register to account for quotient.
4. Check whether divisor is less than dividend. If divisor is less than dividend, go to step 8, otherwise go to next step.
5. Subtract the content of B register from accumulator.
6. Increment the content of C register (quotient)
7. Go to step 4.
8. Store the content of accumulator (remainder) in memory.
9. Move the content of C register (quotient) to accumulator and store in memory
10. Stop.

Leena
Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PATTANUR, KANNUR

PROGRAM

DIVISION

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENTS
4100	3A 01 42		LDA 4201H	
4103	47		MOV B,A	Get the divisor in B register
4104	3A 00 42		LDA 4200H	Get the dividend in A register
4107	0E 00		MVI C,00H	Clear C register for quotient
4109	B8	AGAIN	CMP B	
410A	DA 12 41		JC STORE	If divisor is less than dividend go to store
410D	90		SUB B	Subtract divisor from dividend.
410E	0C		INR C	Increment quotient by one for each subtraction
410F	C3 09 41		JMP AGAIN	
4112	32 03 42	STORE	STA 4203H	Store the remainder in memory
4115	79		MOV A,C	
4116	32 02 42		STA 4202H	Store the quotient in memory.
4119	76		HLT	Halt program execution

Dr. LEENA A V
PRINCIPAL
SREE HARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

	<u>Memory Address</u>	<u>Content</u>
For Addition ;	4200	E2
	4201	45
	4202	27
	4203	01
For Subtraction ;	4200	5E
	4201	34
	4202	2A
	4203	00
For Multiplication ;	4200	C7
	4201	4A
	4202	86
	4203	39
For Division ;	4200	C9
	4201	0A
	4202	14
	4203	01


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

RESULT :

Performed arithmetic operations in 8085 μ p and output is verified.

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

HODEEE

PROGRAM

ADDITION

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENTS
4100	2A 00 42		LHLD 4200H	Get the 1 st data in HL pair
4103	EB		XCHG	Save 1 st data in DE pair
4104	2A 02 42		LHLD 4202H	Get 2nd data in HL pair
4107	AF		XRA A	Clear A register to carry
4108	19		DAD D	Get the sum in HL pair
4109	02 0D 41		JNC AHEAD	IF CF=0 go to AHEAD
410C	3C		INR A	IF CF=1 increment A-register
410D	22 04 42	AHEAD	SHLD 4202H	Store the sum in memory
4110	32 06 42		STA 4206H	Store the carry in memory
4113	76		HLT	Halt program execution

Memory address.	Content
4200	54
4201	C2
4201	92
4203	8A

Memory address	Content
4204	EG
4205	4C
4206	01

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

EXPERIMENT - 2

26/09/22

ARITHMETIC OPERATIONS USING 8085 MICROPROCESSOR [16-BIT]

06

AIM :

To write a assembly language programme (ALP) for performing arithmetic operations such as

(i) Addition


(ii) Subtraction

(iii) Division

using 8085 microprocessor

Algorithm

- 1) Start the program
- 2) Load the two inputs into the memory
- 3) Perform Addition, Subtraction and Multiplication
- 4) Stop the Program

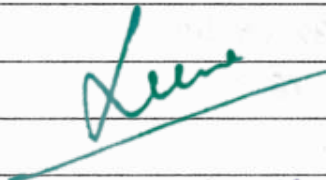
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROGRAM SUBTRACTION

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENTS
4100	3A 02 42		LDA 4202H	
4103	47		MOV B,A	Get low byte submitted in B register
4104	3A 00 42		LDA 4200H	Get low byte of minuvend in A register
4107	90		SUB B	Get difference of low byte in A register
410B	32 04 42		STA 4204H	Store the result in memory
410B	3A 03 42		LDA 4203H	
410E	47		MOV B,A	Get high byte of subtrahend in B register
410F	3A 01 42		LDA 4201H	Get high byte of minuvend in A register
4112	98		SBB B	Get difference of high bytes in A - register
4113	32 05 42		STA 4205	Store the result
4116	76		HLT	Halt program execution

Memory Address	Content
4200	A8
4201	B2
4202	2C
4203	92
4204	7F
205	20

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

PROGRAM

MULTIPLICATION

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENTS
4100			LHLD 4200H	Get 1 st data in HL pair
4103			SPHL	Save the 1 st data in SP
4104			LHLD 4202	Get 2 nd data in HL pair
4107			XCHG	Save 2 nd data in DE pair
4108			LXI H, 0000H	Clear HL pair
410B			LXI B, 000H	Clear BC pair account overflow
410 E		NEXT	DAD SP	Add the content of SP to sum.
410F			JNC AHEAD	
410F			INX B	IF CF = 1, increment BC pair
4102				
4113		AHEAD	DCX D	
4114			MOV A, E	Check for zero in DE pair This is done by logically
4115			ORA D	ORing D and E
4116			JNZ NEXT	Repeat ADDITION until count is zero.
4119			SHLD 4204H	Store lower 16 bit of product in memory
411C			MOV L, C	
411D			MOV H, B	
411E			SHLD 4206	Store the 16 bit of product in memory
4121			HLT	Halt program execution

Leena
Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PAYYANUR, KANNUR

Memory Address	Content
4200	24
4201	5A
4201	C2
4203	47

Memory Address	Content
4204	48
4205	4B
4206	44
4207	19

RESULT :

Obtained assembly language programs to perform the addition, subtraction and multiplication of 16 Bit data

HODEEE

Leena
Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PAYANUR, KANNUR

PROGRAM [search for smallest data in a array]

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENTS
4100	21 00 42		LXI H, 4200H	Set pointer for array
4103	46		MOV B, M	Set count for no. elements in array
4104	23		INX H	
4105	7E		MOV A, M	Set list element of array as smallest data
4106	05		DCR B	Decrement the count.
4107	23	LOOP	JNX H	
4108	BE		CMP M	Compare an element of array with current smallest data
4109	DA 0D41		JC AHEAD	IF CF=1 go to AHEAD
410C	7E		MOV A, M	IF CF=0 then content of memory is smaller than A. Hence if CF=0, make memory as smallest by moving to A
410D	05	AHEAD	DCR B	
410E	C2 07 41		JNZ LOOP	Repeat Comparison until count is zero
4111	32 00 43		STA 4300H	Store the smallest data in memory.
4114	76		HLT	Halt program execution

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

EXPERIMENT - 3

10/10/22

SEARCH FOR SMALLEST AND LARGEST DATA IN A ARRAY


09

AIM :

Write an assembly language program to search the smallest/Largest data in an array of N data stored in memory from 4200H to (4200H + N). The first element of the array gives the number of data in the array. Store the smallest / largest data in 4300H.

Algorithm

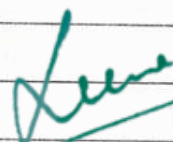- 1) Start the program
- 2) Load the two inputs into the memory
- 3) Perform the search.



Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROGRAM [Search for Largest data in a array]

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENT
4100	21 00 42		LXI H, 4200H	Set pointer for array
4103	46		MOV B, M	Set count for number of elements in array
4104	23		INX H	
4105	7E		MOV A, M	Set 1 st element of array as largest data
4106	05		DCR B	Decrement the count
4107	23	LOOP	INX H	
4108	BE		CMP M	Compare an element of array with current largest data.
4109	D2 0D 41		JNC AHEAD	IF CF=0, go to AHEAD
410C	7E		MOV A, M	IF CF=1 then count of memory is larger than accumulator. Hence if CF=1 make memory content as current largest by moving it to A register
410D	05	AHEAD	DCR B	
410E	C2 07 41		JNZ LOOP	Repeat comparison until count is zero
4111	32 00 43		STA 4300H	Store the largest data in memory.
4114	76		HLT	

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

OBSERVATIONS

	Memory address		
	4200	07	
	4201	42	
	4202	3A	
Array	4203	1C	
	4204	24	
	4205	B4	
	4206	25	
	4207	4F	
Smallest data	4300	1C	
Count	4200	07	
	4201	62	
Array	4202	7D	
	4203	FC	
	4204	24	
	4205	C2	
	4206	0F	
	4207	92	
Largest data	4300	FC	

RESULT:

Obtained the ALP to search the smallest / Largest data in array.

Leena
Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PAYYANUR, KANNUR

PROGRAM [To sort an array of data in Ascending Order]

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENT
4100	3A 00 42		LDA 4200H	Load the count value in A-register
4103	47		MOV B, A	Set count for N-1 repetitions
4104	05		DCR B	of N-1 comparisons
4105	21 00 42	LOOP 2	LXI H, 4200H	Set pointer for array
4108	4E		MOV C, M	Set count for N-1 comparisons.
4109	0D		DCR C	
410A	23		INX H	Increment pointer
410B	7E	LOOP 1	MOV A, M	Get one data of array in A
410C	23		INX H	
410D	BE		CMP M	Compare next data with A register.
410E	DA 16 41		JC AHEAD	If content of A is greater than coming go to AHEAD.
411	56		MOV D, M	If the content of A is greater than
			MOV M, A	The content of memory then exchange the content of memory pointed by HL and pre-location
			DCX M, A	
			MOV M, D	
			INX H	
			DCR C	
			JNZ LOOP 1	Repeat CMP until count is zero
			DCR B	
			JNZ LOOP 2	Rep CMP(N-1) until B count is zero


Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PAYYANUR, KANNUR

EXPERIMENT - 4

17/10/22 SORTING AN ARRAY IN ASCENDING ORDER

11

AIM:

Write an assembly language program to sort an array of data in the ascending order. The array is stored in the memory starting from 4200H. The first element of the array gives the count value for the number of elements in the array.

Algorithm

1. Load the count value from memory to A register and save it in B register.
2. Decrement B-register (B is counter for N-1 repetitions)
3. Set HL pair as data array address pointer.
4. Set C register as counter for N-1 comparisons.
5. Load a data of the array in accumulator using the data address pointer.
6. Increment the HL pair (data address pointer)
7. Compare the data pointed by HL with accumulator
8. If carry flag is set (if the content of accumulator is smaller than memory) then go to step 10, otherwise go to next step.
9. Exchange the content of memory pointed by HL and the accumulator.
10. Decrement C register. If zero flag is reset go to step 6 otherwise go to next step
11. Decrement B register. If zero flag is ~~reset~~ go to the step 3 otherwise go to next step.
12. Stop.

Dr. Leena A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

411E

76

HLT

Halt program execution

OBSERVATION

	INPUT	OUTPUT
Memory Address	Content	Content
4200	07	07
4201	AB	34
4202	92	4F
4203	84	69
4204	4F	84
4205	69	92
4206	F2	AB
4207	34	F2


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

RESULT

Obtained the assembly language program to sort an array of data in ascending order

Asst. Prof.
HODEEE

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROGRAM

Program to Convert 2 digit BCD to Binary Numbers

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENT
4100	3A 00 42		LDA 4200H	Get the data in A register
4103	5F		MOV E, A	and save in E - register
4104	E6 F0		ANI F0H	Mask the lower nibble
4106	07		RLC	Rotate the upper nibble
4107	07		RLC	to lower nibble position
4108	07		RLC	and save in B.
4109	07		RLC	
410A	47		MOV B, A	
410B	AF		XRA A	Clear accumulator
410C	0E 0A		MVI C, 0AH	Multiply tens digit by 0AH &
410E	80	REPT	ADD B	get the product in A-registers
410F	0D		DCR C	
4110	C2 0E 41		JNZ REP	
4113	47		MOV B, A	Save the product in B register
4114	7B		MOV A, E	Get the BCD data in A register
4115	E6 0F		ANI 0FH	Mask the upper nibble
4117	80		ADD B	Get the binary data in A register.
4118	32 01 42		STA 4201H	Save the binary data in memory
411B	76	HLT		Halt program execution

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

EXPERIMENT - 5

BCD TO BINARY CONVERSION

01/11/22


13

AIM:

Write an assembly language program to convert a two digit BCD (8-bit) data to binary data. The BCD data is stored in the 4200H and store the binary data in 4201H.

Algorithm

1. Get the BCD data in A register and save in E-register
2. Mask the lower nibble (units) of the BCD data in A register
3. Rotate the upper nibble to lower nibble position and save in B-register.
4. Clear the accumulator.
5. Move 0AH to C-register
6. Add B-register to A-register
7. Decrement C-register. If $ZF=0$ go to step 6. If $ZF=1$, go to next step.
8. Save the product in B-register
9. Get the BCD data in A register from E-register and mask the upper nibble.
10. Add the units to product
11. Store the binary value
12. Stop

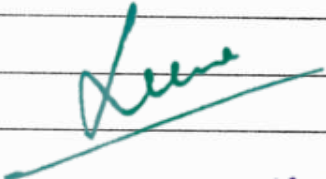
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

**RESULT :**

Obtained the ALP to convert an 8 bit, two digit BCD data to binary data

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROGRAM (TO ADD AN ARRAY OF DATA)

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENTS
4100	21 00 42		LXI H, 4200	Set pointer for data
4103	46		MOV B, M	Set or no. of data
4104	0E 00		MVI C, 00H	Clear c register to
				account for carry
4106	AF		XRA A	clear accumulator,
				initial sum = 0
4107	23	REPT	INX H	
4108	86		ADD M	Add an element of
				the array to sum
4109	D2 0D 41		JNC AHEAD	If No carry then jump
				to A head
410C	DC		INRC	If CF=1, increment
				C-register
410D	05	AHEAD	DCR B	
410E	C2 07 41		JNZ REPT	Repeat addition until
				count is zero.
4111	32 00 43		STA 4300	Store low byte of sum
				in memory.
4114	79		MOV A, C	Move contents of
				C to A
4115	32 01 43		STA 4301	Store high byte of
				sum in memory
4118	76		HLT	Halt the program
				execution

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

EXPERIMENT - 6

14/11/22

ADDITION OF AN ARRAY OF DATA

15

AIM:

To write an assembly language program to add an array of data stored in memory from 4200H to 420FH. The first element of the array gives the number of elements in the array. Store the result at 4300H and 4301H. Assume the sum does not exceed 16-bit.

ALGORITHM:

1. Load the address of the first element of the array in HL pair (pointer).
2. Move the count to B-register.
3. Clear C-register for carry.
4. Clear accumulator for sum.
5. Increment the pointer (HL pair).
6. Add the content of memory addressed by HL to accumulator.
7. Check for carry. If carry = 1, go to step 8, or if carry = 0, goto step 5.
8. Increment C-register.
9. Decrement the count.
10. Check for zero of the count. If ZF = 0, go to step 5 or if ZF = 1, go to next step.
11. Store the content of accumulator (low byte of sum).
12. Move the content of C-register (high byte of sum) to accumulator. Store the content of accumulator in memory.
13. Stop.

Leena A V
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

	Memory Address	Content
Count :	4200	07
	4204	C2
	4202	45
	4203	B3
Array	4204	F4
	4205	7C
	4206	ED
	4207	16
Sum {	4300	2D
	4301	04

Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR




Obtained the ALP to add an array of DATA and verify the result.

[Handwritten signature]

[Handwritten signature]
HODEEE

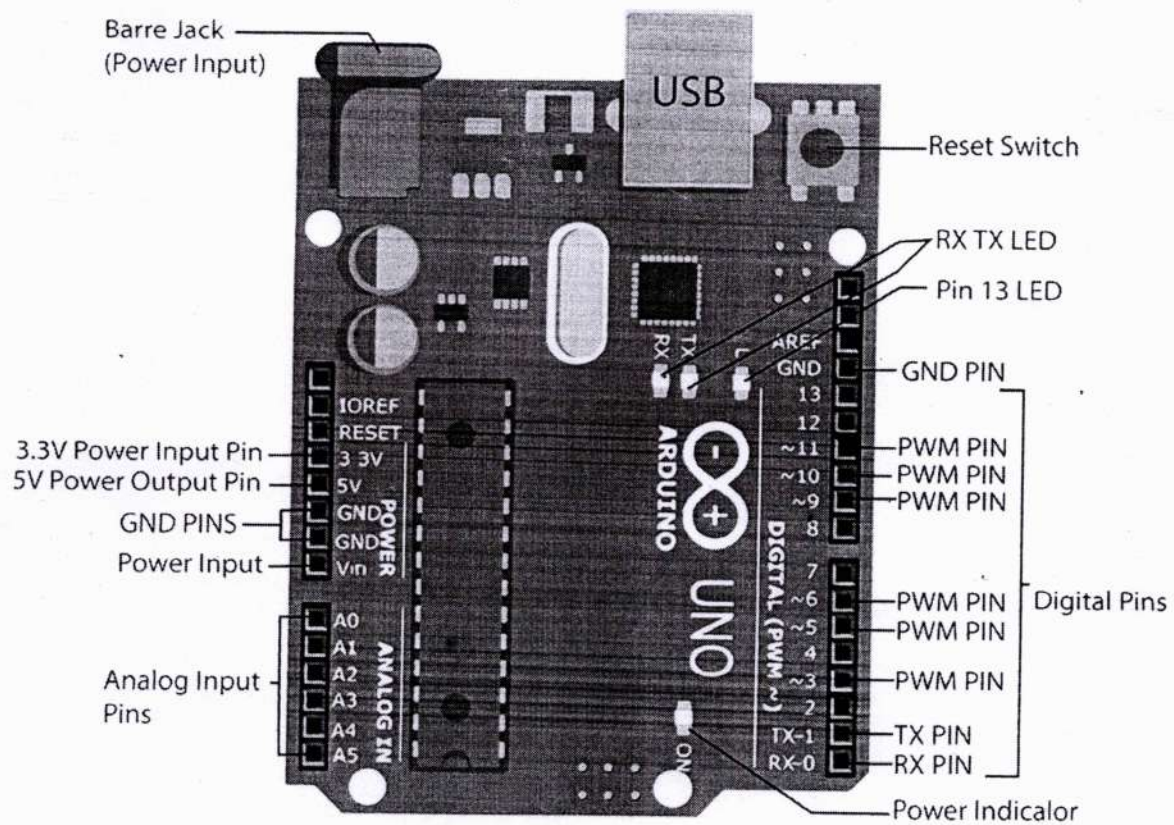[Handwritten signature]
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR



Arduino Uno

Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

EXPERIMENT 7

21/11/22 FAMILIARIZATION OF ARDUINO IDE

17

AIM :


Familiarization of Arduino IDE

THEORY :

Arduino is an open-source prototyping platform based on easy-to-use hardware and software. Arduino boards are able to read inputs - light on a sensor, a finger on a button, or a Twitter message - and turn it into an output - activating a motor, turning on a LED, publishing something online. You can tell your board what to do by sending a set of instructions to the microcontroller on the board. To do so you use the Arduino programming language (based on Wiring), and the Arduino Software (IDE), based on Processing.

Arduino also simplifies the process of working with microcontrollers, but it offers some advantages for teachers, students, and interested amateurs over other s/lms which are expensive, cross-platform, simple, clear programming environment, Open Source and extensible hardware etc.

The basic structure of the Arduino programming language is fairly simple and runs in at least two parts. These two required parts, or functions, enclose blocks of statements where `setup()` is the preparation, `loop()` is the execution. Both functions are required for the program to work. The `setup` function should follow the declaration of any variables at the very beginning of the program. It is the first function to run in the program, is run only once, and is used to set pinMode, initialize serial communication.

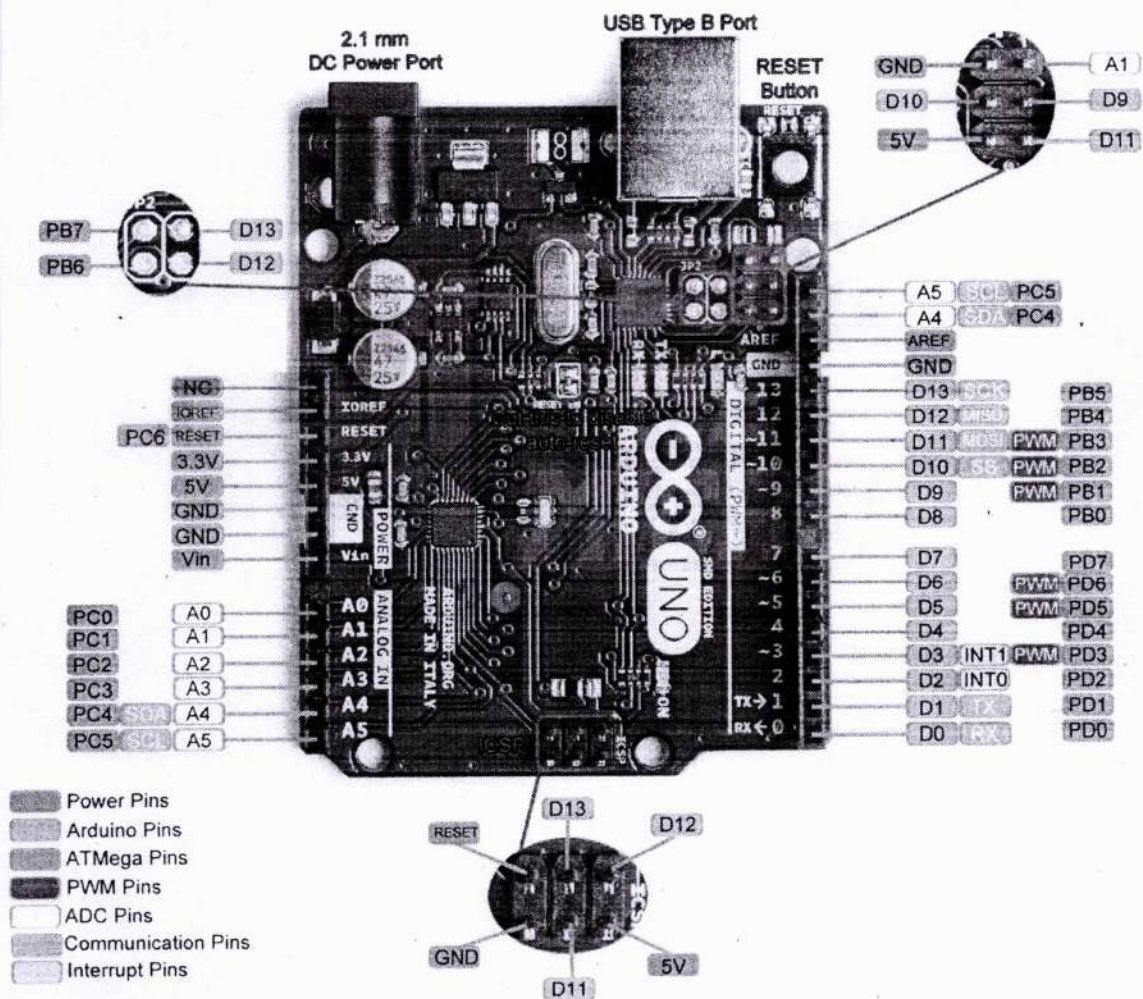

Pin Diagram of Arduino Uno

Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR


The loop function should follow the declaration of any variables at the very beginning of the program. It is the first function to run in the program, is run only once and is the loop function follows next and includes the code to be executed continuously - reading inputs, triggering outputs etc. This function is the core of all Arduino programs and does the bulk of the work. Curly braces (`{}`) define the beginning and the end of function blocks and statement blocks such as the `void loop()` function and the `for` and `if` statements.

Programming using Arduino IDE

Step 1 - Download Arduino IDE software: You can get different versions of Arduino IDE from the Download page on the Arduino Official website. You must select your software, which is compatible with your operating system (Windows, iOS, or Linux). After your file download is complete, unzip the file.

Step 2 - Power up your board: The Arduino Uno automatically draw power from either, the USB connection to the computer or an external power supply. Connect the Arduino board to your computer.

Step 3 - Launch Arduino IDE

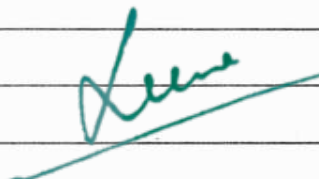
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Arduino Instruction Set

Structure

- + setup()
- + loop()

Control Structures

- + if
- + if...else
- + for
- + switch case
- + while
- + do...while
- + break
- + continue
- + return
- + goto

Further Syntax

- + ; (semicolon)
- + {} (curly braces)
- + // (single line comment)
- + /* */ (multi-line comment)
- + #define
- + #include

Arithmetic Operators

- + = (assignment operator)
- + + (addition)
- + - (subtraction)
- + * (multiplication)
- + / (division)
- + % (modulo)

Comparison Operators

- + == (equal to)
- + != (not equal to)
- + < (less than)
- + > (greater than)
- + <= (less than or equal to)
- + >= (greater than or equal to)

Boolean Operators

- + && (and)
- + || (or)
- + ! (not)

Pointer Access Operators

- + * dereference operator
- + & reference operator

Variables

Constants

- + HIGH | LOW
- + INPUT | OUTPUT
- + true | false
- + integer constants
- + floating point constants

Data Types

- + void
- + boolean
- + char
- + unsigned char
- + byte
- + int
- + unsigned int
- + word
- + long
- + unsigned long
- + float
- + double
- + string - char array
- + String - object
- + array

Functions

Digital I/O

- + pinMode()
- + digitalWrite()
- + digitalRead()

Analog I/O

- + analogReference()
- + analogRead()
- + analogWrite() - PWM

Advanced I/O

- + tone()
- + noTone()
- + shiftOut()
- + pulseIn()

Time

- + millis()
- + micros()
- + delay()
- + delayMicroseconds()

Math

- + min()
- + max()
- + abs()
- + constrain()
- + map()
- + pow()
- + sqrt()

Trigonometry

- + sin()
- + cos()
- + tan()

Random Number

- + randomSeed()
- + random()

Bits and Bytes

- + lowByte()
- + highByte()
- + bitRead()
- + bitWrite()
- + bitSet()
- + bitClear()
- + bit()



Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Step 4 - Open your first project : Once the software starts, you have two options -

- Create a new project
- Open an existing project example

To open an existing project example, select File → Example → Basics → Blink.



Here, we are selecting just one of the examples with the name Blink. It turns the LED on and off with some time delay. You can select any other example from the list.

Step 5 - Select your Arduino board : To avoid any error while uploading your program to the board, you must select the correct Arduino board name, which matches with the board connected to your computer.

Go to Tools → Board and select your board.

Step 6 - Select your serial port : Select the serial devices of the Arduino board. Go to Tools → Serial Port menu. This is likely to be COM3 or higher (COM1 and COM2 are usually reserved for hardware serial ports). To find out, you can disconnect your Arduino board and re-open the menu, the entry that ^{dis}appears should be of the Arduino board. Reconnect the board and select that serial port.

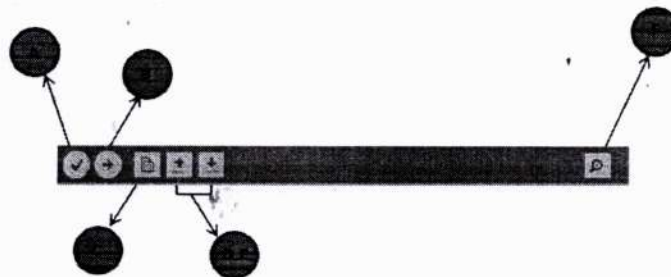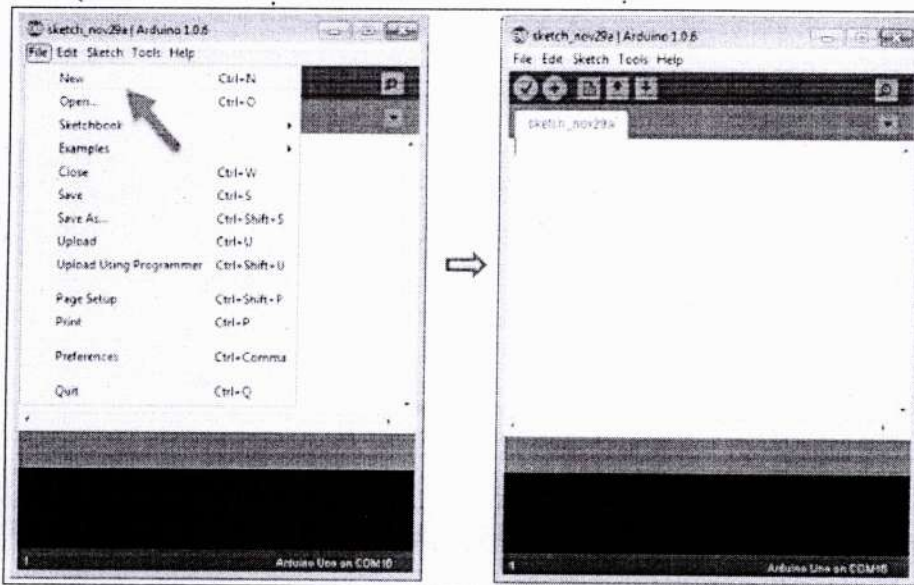Step 7 - Upload the program to your board. **Dr. LEENA A V** **PRINCIPAL** explaining how we can upload our program to the board. **SREE NARAYANA GURU COLLEGE OF ENGINEERING & TECHNOLOGY** **PAYANUR, KANNUR** must demonstrate the function of each symbol appearing in the



A – Check if there is any compilation error.

B – Upload a program to the Arduino board.

C – Shortcut to create a new sketch.

D – Open one of the example sketch.

E – Used to save your sketch.

F – Serial monitor for serial data transfer

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Arduino IDE toolbar. Now, simply click the "Upload" button in the environment. Wait a few seconds; you will see the RX and TX LEDs on the board, flashing. If the upload is successful, the message "Done uploading" will appear in the status bar.

RESULT :

Familiarized with Arduino IDE

Asst. Lab
HOD/EEE

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Connection Diagram:



Circuit for blinking of Internal LED (No External connection required)



Circuit for blinking of external LED on Pin 1

Sample Program for external LED blink on Pin-1:

```
void setup()                                // run once
{
  pinMode(1, OUTPUT);                       // sets pin 1 as output
}

void loop()                                 // run over and over again
{
  digitalWrite(1, HIGH);                    // turns the LED on
  delay(1000);                              // pauses for 1 second
  digitalWrite(1, LOW);                     // turns the LED off
  delay(1000);                              // pauses for 1 second
}
```


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

EXPERIMENT - 8

28/11/22

LED CONTROL USING ARDUINO


21

AIM

- Blinking inbuilt LED with different on off time delays
- Blinking externally interfaced LED with different on off time delays.

Hardware Required:

1. Arduino board	Arduino Uno	1
2. LED		1
3. Resistor	220 Ohm	1
4. Bread board and connection wires		

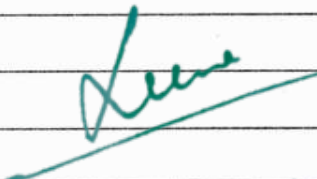
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR


RESULT

Performed LED Control using Arduino

Atin
HODEEE

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Connection Diagram:

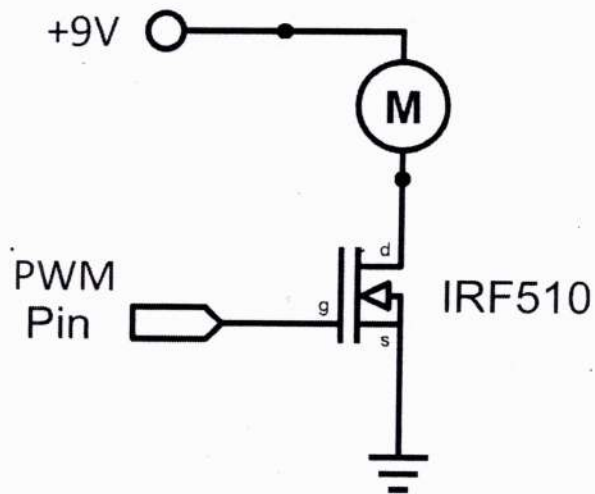

Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

EXPERIMENT - 9

05/12/22 DC MOTOR SPEED CONTROL USING ARDUINO

23

AIM :


To control the speed of a DC motor using MOSFET driven by PWM signal from Arduino module

Hardware Required :

- | | | |
|--|-------------|---|
| 1. Arduino board | | |
| 2. MOSFET or MOSFET based motor driver board | Arduino Uno | 1 |
| | IRF 510 | 1 |
| 3. DC Motor | 9V | 1 |
| 4. Bread board and connection wires | | |

STUDY :

To control a load with more than 40ma current requirement using the Arduino, a MOSFET or transistor could be used to switch higher current loads. Also motor speed control requires voltage variation, which could be achieved by using the PWM variable voltage signal available from the PWM enabled digital pins of the Arduino.

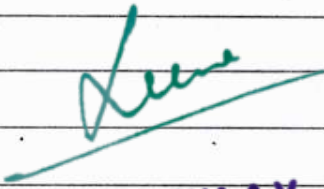
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Sample Program for DC motor speed control:

```
void setup()
{
  pinMode(5, OUTPUT);           // sets PWM Pin 5 as output
}

void loop()
{
  for (int i=0; i<255; i++)      // Motor speed increasing
  {
    analogWrite(5, i);           // turns MOSFET on
    delay(250);                  // pauses 1/4 second
  }
  delay(1000);                   // pauses 1 second

  for (int i=255; i>0; i--)      // Motor speed decreasing
  {
    analogWrite(5, i);           // turns MOSFET on
    delay(250);                  // pauses 1/4 second
  }
  delay(1000);                   // pauses 1 second
}
```


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR



RESULT

Controlled the speed of a DC motor using MOSFET driven by PWM signal from Arduino module

A. Srinivas
H0DEEE

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

Connection Diagram:

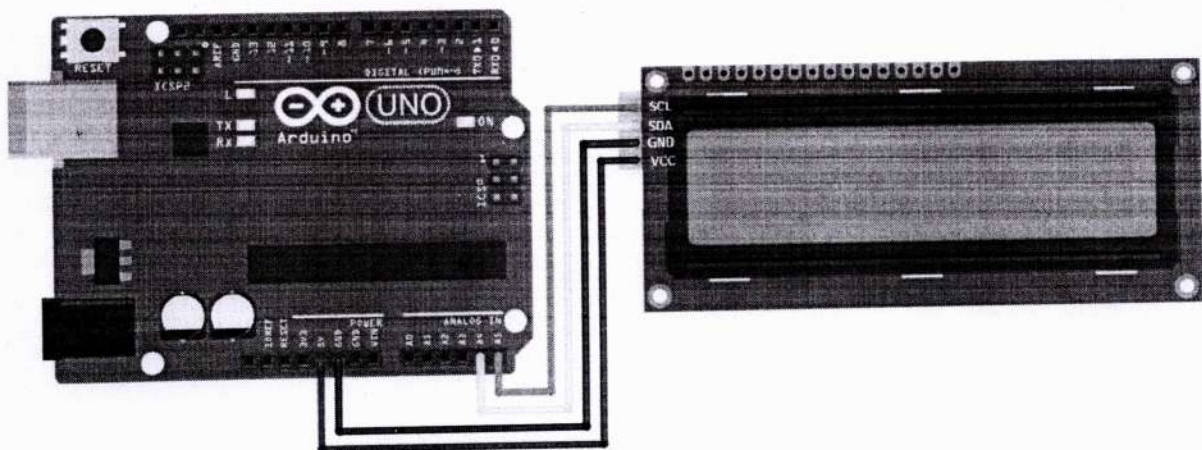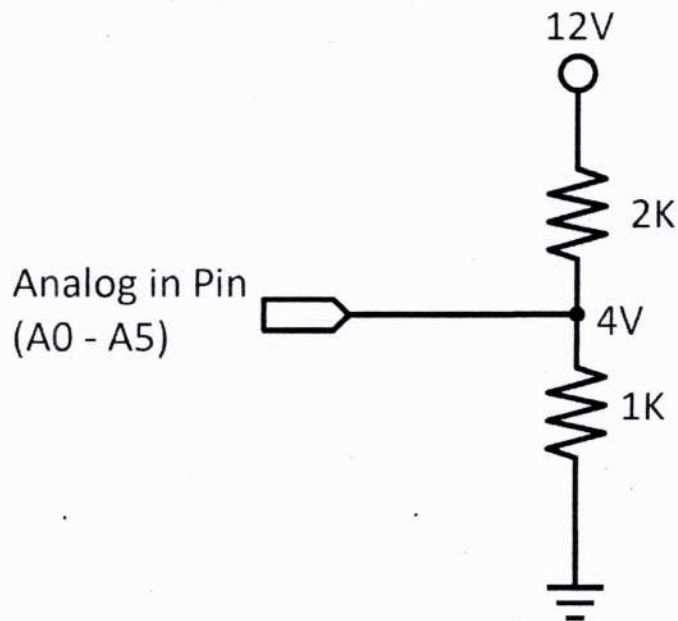

I2C Line	Pin in Arduino
SDA	A4, SDA
SCL	A5, SCL

Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

EXPERIMENT - 10

12/12/22 VOLTAGE MEASUREMENT USING ARDUINO

25

AIM:

Arduino based voltage measurement of 12V solar PV module or 12V battery and displaying the measured value using 12C LCD display.

Hardware Required:

1. Arduino board	Arduino Uno	1
2. LCD display with 12C adapter	16x2 (1602) Character (5x7 Dot Matrix Character and cursor) Green Backlight LCD Display with attached 4 pin 12C adapter	1
3. Voltage source	9V Battery	1
4. Resistor	1K, 2K	1 each
5. Bread board and connection wires		1

THEORY:

Arduino can only measure a maximum of 5V on the analog pins, and hence a potential divider arrangement using resistors is used to reduce the voltage to be measured and later a multiplication factor is used in the program to scale the obtained value to actual voltage value.

LCD 16x2 :

An electronic device that is used to display data and the message is known as LCD 1602. It includes 16 columns and 2 Rows so it can display 32 characters in total. Every character will be made with (5x8) (40) Pixel.

Dr. LEENA A V

PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

Sample Program:

```
#include <Wire.h>           // library for I2C
#include <LiquidCrystal_I2C.h> // Arduino library for I2C LCD displays
LiquidCrystal_I2C lcd(0x27,20,4); //Set the LCD address to 0x27 (default)

void setup()
{
    lcd.init();           // Initialize the lcd
    lcd.backlight();      // Turn on backlight of lcd
    lcd.setCursor(2,0);    //Setting display cursor position (Col 2, Row 0)
    lcd.print("VOLTMETER"); // Show on LCD display from cursor position
}

void loop()
{
    lcd.setCursor(0,1);    // Set Cursor to (Column 0, Row 1)
    lcd.print("VOLT =");  // Display the characters
    float mf = 3;          // Multiplication factor corresponding to resistors
    int x = analogRead(A0); // Read input Voltage from A0
    float value = (x*mf*5)/1024; // Convert input to actual voltage value
    lcd.setCursor(6,1);    //Set Cursor to (Column 6, Row 1)
    lcd.print(value);      // Display the voltage
    delay(500);            // Delay 0.5s
}
```


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR


Dots and the the total pixels within this LCD, can be calculated (by) 32×40 or 1280 pixels. The data register inside the display is used to save the data to exhibit on the LCD.

I2C Protocol:

The Inter-Integrated Circuit (I2C) Protocol is a protocol intended to allow multiple peripheral digital integrated circuits to communicate with one or more controller chips. I2C requires only two wires to communicate (with) in serial mode, but those two wires can support up to 1008 peripheral devices, each having an address. Each I2C consists of two signals: SDA (Serial Data) - The Data signal and SCL (Serial clock) - the clock signal. The clock signal is always generated by the Master or the current bus controller.

RESULT:

Measured the voltage of 12V solar PV module and displayed the measured value using I2C LCD display.

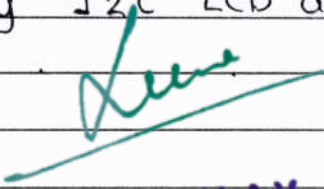
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROGRAM ADDITION

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENTS
4100	C3		CLR C	Clear C
4101	74 20		MOV A, # DATA	Move the data to A register
4103	24 10		ADD A, # DATA	Add the data with A
4105	90 45 00		MOV DPTR, # 4500	Set the pointer to 4500
4108	F0		MOVX @DPTR, A	Store the results in memory
4109	80 FE	END	SJMP END	Stop the program.

SUBTRACTION :

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENTS
4100	C3		CLR C	Clear the carry flag
4101	79 20		MOVA, # DATA	Move the lower nibble of data to A register
4103	94 10		SUBB A, # DATA	Subtract the data with A register
4105	90 45 00		MOV DPTR, # 4500	Set the pointer to 4500
4108	F0		MOVX @DPTR, A	Store the result in memory
4109	80 FE		SJMP END	Stop the program

HODEEE

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

EXPERIMENT - 11

19/12/22 ARITHMETICS OPERATIONS USING 8051


27

AIM:

To write an assembly language program (AIP) for performing arithmetic operations such as addition, subtraction, multiplication and division using 8051.

ALGORITHM:

1. Start the program.
2. Load the two inputs into the memory.
3. Perform addition, subtraction, multiplication and division.
4. Stop the program.

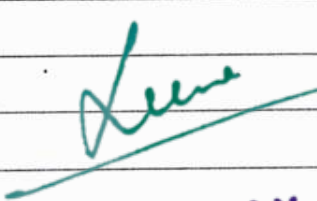
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

MULTIPLICATION

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENTS
4100	74 65		MOV A, #DATA	Move the data to A register
4102	75 F0 08		MOV B, #DATA	Move the data to B register
4105	A4		MUL AB	Multiply A and B
4106	90 45 00		MOV DPTR, #4500	Load the address of data in DPTR
4109	F0		MOVX @DPTR, A	Store the lower byte of product.
410A	A3		INC DPTR	Increment data pointer
410B	F5 F0		MOV A, B	Move the content of B register to A register
	F0		MOVX @DPTR, A	Move the data to DPTR
410E	80 FE	END	SJMP END	


Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PAYYANUR, KANNUR


DIVISION

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENTS
4100	74 65		MOV A, # DATA	Move the data to A
4102	75 F0 08		MOV B, # DATA	Move the data to B
4105	84		DIV AB	Divide A and B
4106	90 45 00		MOV DPTR, # 4500	Load the address of data in DPTR
4109			MOVX @DPTR, A	Store the lower byte of Product
410A	A3		INC DPTR	Increment data pointer
410B	E5 F0		MOV A, B	Move B to A
410D	F0		MOVX @DPTR, A	Store the A value
410E	80 FE		SJMP END	Stop

OBSERVATION

8 BIT Addition			8 BIT Subtraction		
INPUT	OUTPUT		INPUT	OUTPUT	
DATA	ADDRESS	DATA	DATA	ADDRESS	DATA
0.3 0.2	4500	0.5	0.8 0.2	4500	0.6

8 BIT Multiplication			8 BIT DIVISION		
INPUT	OUTPUT		INPUT	OUTPUT	
DATA	ADDRESS	DATA	DATA	ADDRESS	DATA
0.2 0.4	4500 4501	08 00	08 04	4500 4501	02 00

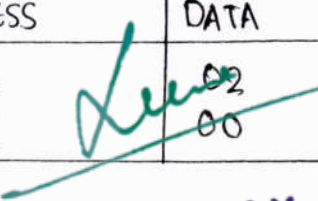
Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PAYYANUR, KANNUR

RESULT :

Executed assembly language program (ALP) for performing arithmetic operations such as addition, subtraction, multiplication and division using 8051.

H. D. E. E.
H. D. E. E.

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROGRAM

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENTS
2100			ORG 2100H	Specify the program starting address
2100	90 24 00		MOV DPTR, #2400H	Set DPTR as pointer for array
2103	F0		MOVX A, @DPTR	Get the count value in A
2104	F8		MOV R0, A	Set R0 as counter for N-1 comparison
2105	18		DEC R0	
2106	A3		INC DPTR	Let DPTR point to first element of array
2107	E0		MOVX A, @DPTR	
2108	FC		MOV R4, A	Let first element as largest and save it in R4
2109	A3	AGAIN	INC DPTR	Make DPTR point next element of array
210A	E0		MOVX A, @DPTR	Get next element of array in A
210B	FA		MOV R2, A	Save it in R2
210C	C3		CLR C	Clear carry flag
210D	9C		SUBB A, R4	Subtract the current largest from A
210E	40 02		JC AHEAD	Check for carry, if carry is set go to AHEAD
2110	EA		MOV A, R2	IF carry is not set
2111	FC		MOV R4, A	Then save the content of R2 as current largest
2112	D8 F5	AHEAD	DJNZ R0, AGAIN	Decrement count and go to AGAIN if count is not zero

EXPERIMENT - 12

03/01/23

SEARCH FOR LARGEST DATA IN AN ARRAY


30

AIM:

Write an Assembly language program to search the largest data in an array of data stored in memory.

ALGORITHM:

1. Set DPTR as pointer for data array
2. Load the count value N in A and save in R0
3. Decrement R0 to set count for N-1 comparison
4. Increment DPTR
5. Load the first data of array in A and save it as current target in R4 register
6. Increment DPTR
7. Get a data and array in A register and save it in R2 register
8. Clear carry flag and subtract the current lagged in R4 from A
9. Check carry flag. If carry is set, then go to step II, otherwise goto next step
10. If carry is not set, then the content of R2 is larger than R4 and so move R2 to R4 via A.
11. Decrement R0 and check whether it is zero. If R0 is not zero, then go to step II, otherwise go to next step.
12. Load the address of the memory where largest data is to be stored.
13. Move the largest data from RA to A and save in memory pointed by DPTR

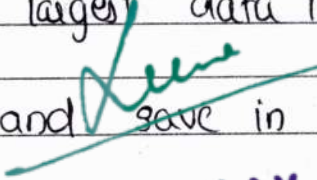
DR. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENTS
2114	90 25 00		MOV DPTR, # 2400 _H	Load the address of result in DPTR
2117	EC		MOV A, R4	Move the largest data to A
2118	FD		MOVX @DPTR, A	Save in external memory
2119	80 FE		SJMP HALT	
211B			END	Assembly END

OBSERVATION

INPUT		OUTPUT
Count	Array	Largest Data
06	2401 - 7F 2402 - 1C 2403 - 42 2404 - 57 2405 - 13 2406 - FE	2500 - FE


Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PAYYANUR, KANNUR

RESULT :

Obtained an assembly language program to search the largest data in an array of data in the memory.

HODEEE
HODEEE

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

PROGRAM

ADDRESS	OPCODE	LABEL	MNEMONICS	COMMENTS
4100	90 45 00		MOV DPTR, #4500	Load the source data address in DPTR
4103	E0		MOVX A, @DPTR	Movedata from external memory to A register
4104	75 F0 64		MOV B, #64	Move data to B
4107	84		DIV AB	Divide A and B
4108	90 45 01		MOV DPTR, #4500	Load the address of data in DPTR
410B	F0		MOVX @DPTR, A	Store the lower byte of product
410C	E5 F0		MOV A, B	Move B to A
410E	75 F0 0A		MOV B, #04	Move data to B
4111	84		DIV AB	Divide A and B
4112	A3		INC DPTR	Increment data pointer
4113	F0		MOVX @DPTR, A	Store the higher byte
4114	A3		INC DPTR	Increment data pointer
4115	E5 F0		MOV A, B	Move B to A
4117	F0		MOVX @DPTR, A	Store the higher byte
4118	80 FE	END	SJMP	Stop


Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PAYYANUR, KANNUR

EXPERIMENT - 13

09/01/23 HEXADECIMAL TO DECIMAL CONVERSION


32

AIM:

To perform hexadecimal to decimal conversion

ALGORITHM:

1. Load the number to be converted into the accumulator
2. If the number is less than 100 (64H), go to the next step; otherwise, subtract 100 (64H). Here the subtraction repeatedly until the remainder is less than 100 (64H). Have the current (100's value) in separate register which is the carry.
3. If the number is less than 10 (0AH), go to next step; otherwise subtract 10 (0AH), go to repeatedly until the remainder is less than 10 (0AH). Have the count (item's value) in separate registers
4. The accumulator now has the units.
5. Multiply the ten's value by 10 and add it with the units.
6. Store the result and carry in the specified memory location.

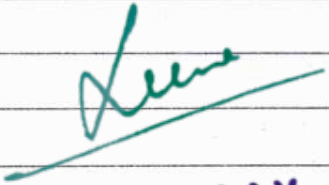
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

RESULT :

Obtained an assembly language for conversion for hexadecimal to decimal.

Abhinav
HOD/EEE

Leena
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR



13

Completed all
experiments

Vn


03/01/23

A Vaisakh. M. Noyens
APEEE




Leena

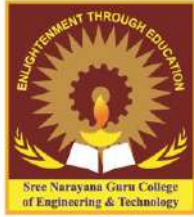Dr. LEENA A. V.
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY, PAYYANUR
KANNUR



Sree Narayana Guru College of Engineering & Technology

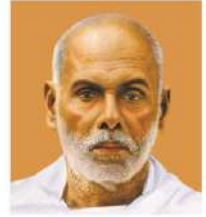CHALAKKODE P.O., KOROM, PAYYANUR, KANNUR-670 307



DEPARTMENT OF MECHANICAL ENGINEERING

CERTIFICATE

Date: 10 / 8 / 2023

This is to certify that Mr./Ms. ASHWIN JOHN

of Class 56 Division _____ Roll No. SNC20ME003

has satisfactorily completed the course experiments in practical

MEL-332 Computer Aided Design and Analysis Lab

in the academic year of 2022 / 20 23

in the Institution SNGCET


Teacher


Examiner


Principal


Dr. LEENA A. V.
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY, PAYYANUR
KANNUR

Institution Rubber Stamp

INDEX

[illegible]

SOLID WORKS

Solid work is a 3D mechanical CAD programme and is being developed by Dassault system.

5 Solid works is a mechanical design software to build programming models of parts and assemblies. It ~~is~~ also includes various analysis and synthesis process. A solid is the computer type of geometric module used in ~~3D~~ CAD system. It contains all the mix of frame and surface geometry to fully describe the edge and the face of
10 mold.

Solid works includes many enhancements most in a CAD system. It contains all the enhancements most in desired response to ~~the~~ customer request.

The top enhancements for solid works ~~2013~~ 2013 provides
15 improvements to existing products and innovative new functionality.

MODELING METHODOLOGY

Parameters refers to constrain where the value determines the shape of geometry of the model or assembly. ~~for~~ Parameters are be either
20 numeric parameters such as line length or circle diameter of geometric parameters, such as tangent parallel horizontal or vertical etc.

Design ~~intend~~ Intent is how the circles of the part wants to be respond to changes and updates, for example you would want the hole at the top of a beverage can to stay at the top surface
25 regardless of the height or size ~~of~~ of the can.

Features refers to bounding blades of the part ~~are the~~ Shaper and operations that construct the part shape based ~~function~~ typically.

Teacher's Signature:

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

begin with 2D or 3D sketch of shapes such as holes slots etc. operation based features are not sketch based and include features such as fillets, chamfers etc!

Building a model in Solidworks usually start with a 2D sketch.

5 The consist of geometry such as points, line and corners. Dimensions are added to the sketch to define the size and location of the geometry. Relations are used to specify the attributes such as tangency, Parallelism, perpendicular. The parametric nature of Solid works means that dimensions and relation drive the geometry, no way either
10 Grend.

In an assemble the analog to sketch relations are mates just as sketch relation define conditions such as tangency, parallelism with respect sketch geometry, assembly mates define equivalent relations with respect to the individual Solid works including additional advanced mate features

15 Such as gear and cam following routine.

finally, drawings can be created either from parts or assemblies.

views are automatically generated from Solid model and notes, dimensions and tolerance can be easily added to the drawing as need. The drawing module includes

20 1. Drawing and elevating

2. Assemblies

3. Motion Study

4. Parts and function

5. ROLING

25 6. Short metal

7. Simulation.

Teacher's Signature:

Dr. LEENA A V

PRINCIPAL

SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

User Interface

Main elements at the Solid Works user interface are

1. Member

5 2. Command manager

3. Property manager

4. Feature manager

5. Configuration manager

6. Search assistant

10 7. Status bar

8. Task pane

9. Tool bar

Basic Concepts:

15 The Solid Works model consists of 3D solid geometry in a part or assembly document. Drawings are created from model or by drafting view in a drawing document. We begin with a sketch, create a basic feature and then add more features to our model. It is possible to edit our design by adding, editing or deleting features. Association between
20 part, assemblies and drawings assumes that changes made to one document or file are automatically made to all other documents and views.

Assemblies:

25 In Solid Works, we can create assemblies containing as many component which can be part of other assemblies called sub assemblies. To create an assembly from parts:

Teacher's Signature:

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

1. ~~click~~ click make assembly from part/assembly or file → assembly part
Assembly open with the insert component property manager device
2. Click in the graphics area to add the part to the assembly. There are many ways to add the component to the new or existing assembly
- 5 a) Use the Insert ~~from~~ component
b) Drag from the 'file explore' tab in the task pane
c) Drag from open documents windows
d) Drag from design library in one task placed.

10 Mates:

Mates create geometrical relationship between assembly components
eg: A coincident mate force two planes force to become coplanar

Types of mates

- 15 * Angle mate
* coincident mates
* Distance mate
* Lock mate
* Parallel and perpendicular

20 FLOXPRESS


Solid works floxpress is a fluid dynamics application that calculation that calculate how fluid ~~find~~ flow through operator assembly module based on the calculated velocity fluid. ~~we can find~~ problem areas
25 in our device and ~~then~~ improve them before manufacturing


Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

Teacher's Signature:

Steps

1. Preparing the model for analysis enclose the inlet and outlet opening with hole
- 5 2. Start Solid works flexprep
Click tools → Solid works flexprep
3. check geometry
4. Select & thread
5. Selecting the flow inlet connection
- 10 6. Selecting the flow outlet connection
7. Solving the model
Click solve
8. Viewing the results.

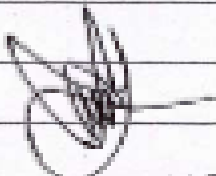
HSD ME

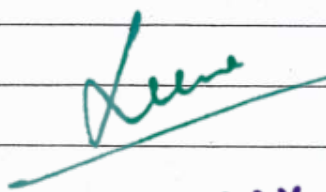
DR. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

EXPERIMENT NO : 1

ORTHOGRAPHIC VIEWS FROM 3D MODELS

Aim: To familiarize the 3D modelling of various design of objects and to generate 2D drawings for shop floor.

Equipments Required:

1. A personal computer loaded with any one of the following application software
Solidworks, CATIA, PRO-E
2. A3 or A4 Plotter or Printer.

Procedure:

1. Execute the application software ie SOLIDWORKS
2. Set unit "mmgs"
3. Select new part
4. Select Suitable 3D commands (Extrude, Revolve, Loft and Sweep).
5. Select the required Plan (Top, front, and side) and Sketch the 2D profile to be converted in 3D with required exact dimensions.
6. Exit the 2D sketch and execute the Selected 3D command
7. Repeat the above steps from 4th until the desired object is completed.
8. 3D modifying commands are also can be used as and when required (Fillet, chamfer, mirror, pattern etc)
- 9) on completion of 3D modelling, save and close the file and open the new module 2D drafting and generate 2D drawing of the 3D model created previously
10. 2D drafting file is an another file that can be saved and closed.

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR



Procedure	5
Conduction	5
Result	5
Viva	10
Record	5

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

EXPERIMENT NO : 2

ORTHOGRAPHIC VIEWS FROM 3D MODELS

Aim :- To familiarize the 3D modelling of various design of objects and to generate 2D drawings for shop floor.

Equipments required;

1. A Personal Computer loaded with any one of the following application Software.

SOLIDWORKS, CATIA, PRO-E

2. A3 or A4 Plotter or Printer

PROCEDURE:

1. Execute the application Software ie SOLIDWORKS.

2. Set unit "mmgs"

3. Select New Part

4. Select Suitable 3D command (^{de}Extrude, Revolve, Loft, and Sweep).

5. Select the required Plan (Top, front, and side) and sketch the 2D profile to be converted in 3D with required exact dimensions.

6. Exit the 2D Sketch and Execute the selected 3D command

7. Repeat the above steps from 4th until the desired object is completed

8. 3D modifying commands are also can be used as and when required (fillet, chamfer, mirror, Pattern etc)

9. On completion of 3D modelling, save and close the file and open the new module 2D drafting and generate 2D drawing of the 3D model created previously

10. 2D drafting file is an another file that also to be saved and closed.

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR



Procedure	S
Conduction	S
Result	S
Viva	9
Record	S

29

Dr. LEENA A V
PRINCIPAL

EXPERIMENT No 3

3D MODELLING AND ASSEMBLING OF GIB AND COTTER JOINT

Aim: To familiarize the 3D modelling of various design of objects and to assemble together to form a product having some engineering functions

Equipments required:

1. A personal computer loaded with any one of the following application Software
~~Solid~~ SOLIDWORKS, CATIA, PRO-E

2. A3 or A4 Plotter or Printer

Procedure:

1. Execute the application software ie SOLIDWORKS

2. Set unit 'mmgs'

3. Select new part

4. Select suitable 3D commands (Extrude, Revolve, Loft and Sweep).

5. Select the required plan (Top, front and side) and sketch the 2D profile to be converted in 3D with required exact dimension

6. Exit the 2D Sketch and execute the selected 3D command

7. Repeat the above step from 4th until the desired object is completed.

8. 3D modifying commands are also can be used as and when required.
(Fillet, chamfer, mirror, pattern etc)

9. On completion of 3D modelling, save and close the file and open the new files for each model and model every part in the assembly and save them separately with their part name and close all file files.

10. Open new assembly and open the base part for the assembly

11. Insert all the parts in the assembly, and open the base part

DR. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

Teacher's Signature:

for the assembly

11. Insert all other parts as per the assembly sequence and make the assembly relationship with the base part or other parts inserted using mate command.

12. Save the assembly file with suitable name, and close.


13. It is possible to generate 2D drawing of assembly whenever required with 2D drafting module.

10

15

20

25

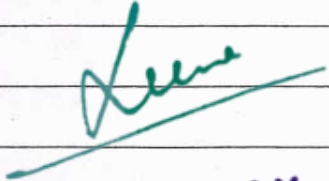
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Teacher's Signature:

EXPERIMENT NO : 4

3D MODELLING AND ASSEMBLING OF FLANGED COUPLING

Aim: To familiarize the 3D modelling of various design of objects and to assemble together to form a product having some engineering functional.

Equipments Required:


1. A personal computer loaded with any one of the following application software
SOLIDWORKS, CATIA, PRO-E

Procedure

1. Execute the application software i.e. SOLIDWORKS
2. Set unit "mmgs"
3. Select new part
4. Select suitable 3D commands (Extrude, revolve, Loft and Sweep)
5. Select the required planes (Top, front and side) and sketch the 2D profile to be converted to 3D with required exact dimensions.
6. Exit the 2D sketch and execute the selected 3D command
7. Repeat the above steps from 4th until the desired object is completed
8. 3D modifying commands are also can be used as and when required (fillet, chamfer, mirror, pattern etc.)
9. On completion of 3D modelling, save and close the file and open the new file for each model and model every part in the assembly and save them separately with their part name and close all the files.
10. Open new assembly and open the base part for the assembly
11. Insert all the parts in the assembly sequence and make the

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Teacher's Signature:

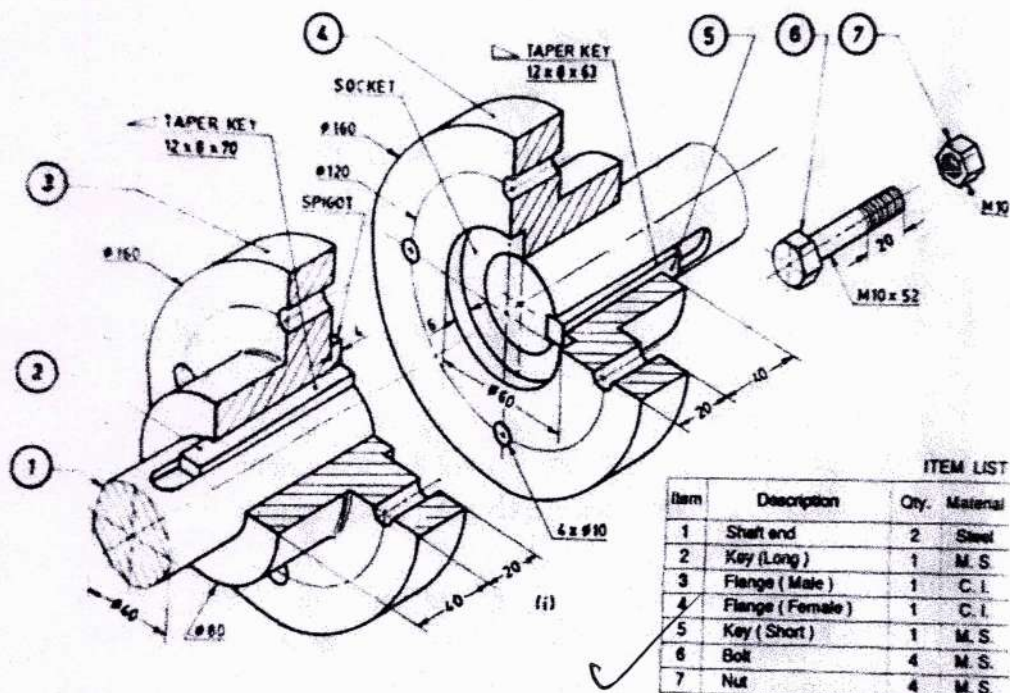

ITEM LIST			
Item	Description	Qty.	Material
1	Shaft end	2	Steel
2	Key (Long)	1	M.S.
3	Flange (Male)	1	C.I.
4	Flange (Female)	1	C.I.
5	Key (Short)	1	M.S.
6	Bolt	4	M.S.
7	Nut	4	M.S.

Procedure	S
Conduction	S
Result	S
Viva	8.5
Record	S

28/2

Leena
Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PAYYANUR, KANNUR

assembly relationship with the base part or other part inserted using mate command.

12. Save the assembly file with suitable name and close.


13. It is possible to generate 2D drawing of assembly whenever required with 2D drafting module.

10


15

20

25

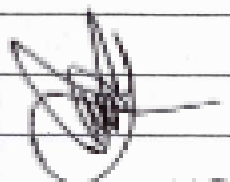

HOS ME

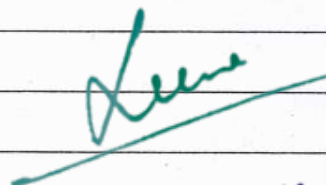

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Teacher's Signature:

EXPERIMENT NO: 5

3D MODELLING AND ASSEMBLING OF KNUCKLE JOINT

Aim: To familiarize the 3D modelling of various design of objects and to assemble together to form a product having some engineering functions.

Equipments required:

1. A personal computer loaded with any one of the following application softwares.

SOLIDWORKS, CATIA, PRO-E

2. A3 or A4 Plotter or printer

Procedure:

1. Execute the application software i.e. Solidworks

2. Set unit 'mmgs'

3. Select new part

4. Select suitable 3D command (Extrude, Revolve, Loft and Sweep)

5. Select the required plan (Top, front, and Side) and sketch the 2D profile to be converted in 3D with required exact dimensions

6. Exit the 2D sketch and execute the selected 3D command


7. Repeat the above steps from 4th until the desired object is completed.

8. 3D modifying commands are also can be used as and when required (fillet, chamfer, mirror, pattern etc)

9. On completion of 3D modelling save and close the file and open the new files for each model and model every part in the assembly and save separately with their part name and close all files.

DR. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

Teacher's Signature:

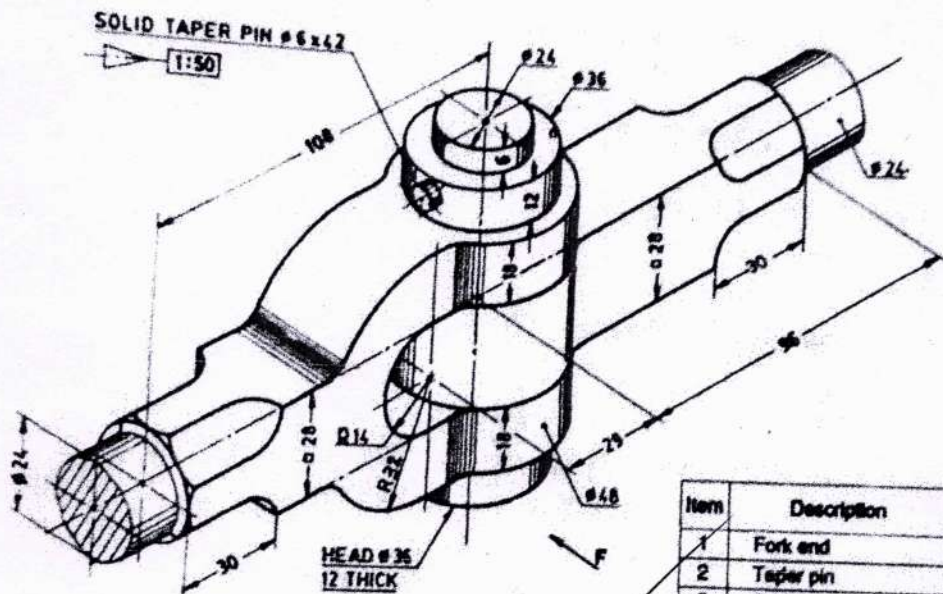

ITEM LIST			
Item	Description	Qty.	Material
1	Fork end	1	M. S.
2	Taper pin	1	M. S.
3	Collar	1	M. S.
4	Pin	1	M. S.
5	Eye end	1	M. S.

Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Procedure	5
Conduction	5
Result	5
Viva	8½
Project	5
	28½


10. Open new module of assembly and open the base part for the assembly

11. Insert all other parts as per the assembly sequence and make the assembly relationship with the base part or other parts inserted, using mate command

12. Save the assembly file with suitable name and close

13. It is possible to generate 2D drawing of assembly whenever required with 2D drafting module.

HOD ME

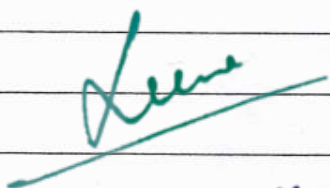
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Teacher's Signature:

EXPERIMENT NO. 6

3D MODELLING AND ASSEMBLING OF PLUMMER BLOCK

5 Aim: To familiarize the 3D modelling of various design of objects and to assemble together to form a product having some engineering functions.

Equipments Required:

- 10 1. A personal computer loaded with any one of the following application software
SOLIDWORKS, CATIA, PRO/E
2. A3 or A4 Plotter or Printer.

Procedure:

- 15 1. Execute the application software i.e. SOLIDWORKS
2. Set unit "mmgs"
3. Select new part
4. Select Suitable 3D Commands [Extrude, Revolve, Loft and Sweep].
5. Select the required plan (Top, front and side) and sketch the 2D profile
- 20 to be converted in 3D with required exact dimensions.
6. Exit the 2D sketch and execute the selected 3D command
7. Repeat the above steps from 4th until the desired object is completed.
8. 3D modifying commands are also can be used as and when required (fillet, chamfer, mirror, pattern etc)
- 25 9. On completion of 3D modelling, save and close the file and open the new file for new models and model every part in the assembly and save each model with their part name and close all files.

DR. LEENA A.V.
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PATTANUR, KANNUR

Teacher's Signature: _____

10. Open new module of assembly and open the base part for the assembly

11. Insert all other parts as per the assembly sequence and make the assembly relationship with the base part or other parts inserted, using mate command

12. Save the assembly file with suitable name, and close


13. It is possible to generate 2D drawing of assembly whenever required with 2D drafting module.


10

15

20

25

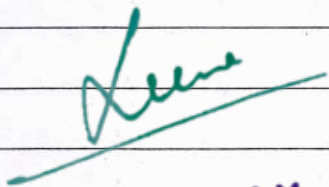
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

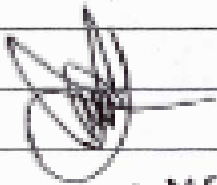
HOD ME

Teacher's Signature:

EXPERIMENT NO. 7

STRUCTURAL ANALYSIS ON CANTILEVER BEAM

Aim: To familiarize the structural analysis on ANSYS software

Equipment required:

1. A personal computer loaded with any one of the following application software.

SOLIDWORKS, ANSYS

2. A4 Printer

PROCEDURE;

1. Execute the application software i.e ANSYS (mechanical APPL)

2. Set preference of study

3. model the 2D elements to be studied, as per the requirements

4. Set the material type

5. Assign the material properties

6. Create the meshing of the modelled part.

7. Assign the boundary conditions, by applying degree of freedom and external loads at required position

8. Solve problem with given boundary conditions


9. Open the result of deformation, stress and strain plot

10. Generate the report.

Dr. LEENA A V
PRINCIPAL

SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Teacher's Signature:

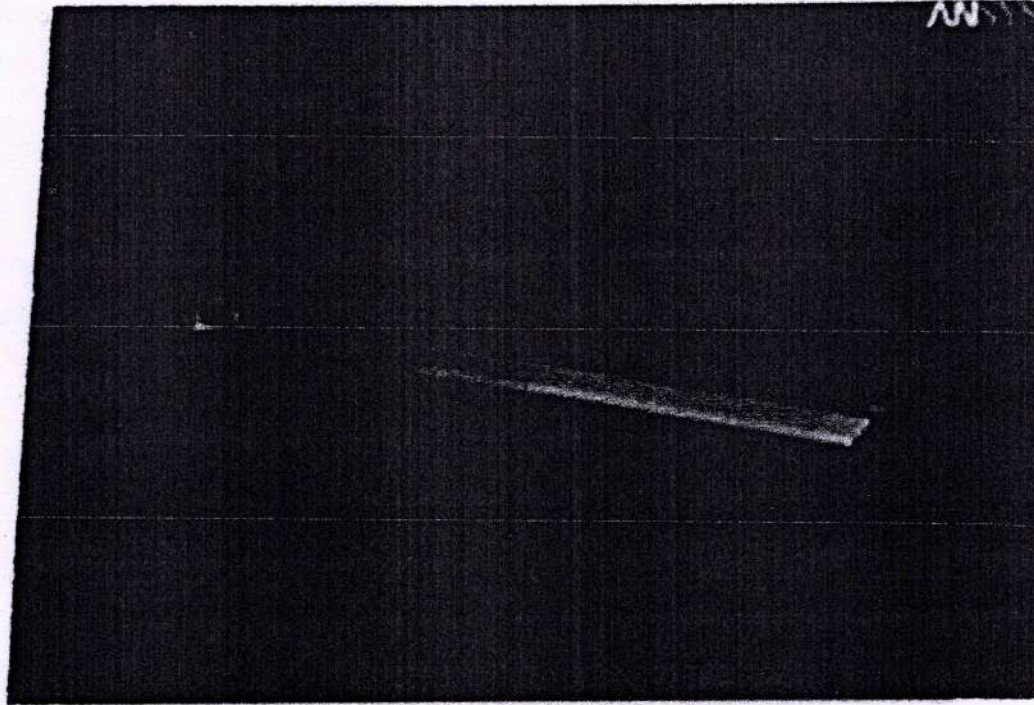

Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Procedure	S
Conduct	S
Result	S
va	96
ord	S

29/2

[Signature]
HOD ME

EXPERIMENT NO. 8 STRUCTURAL ANALYSIS ON 2D TRUSS

Aim: To familiarize the structural analysis on ANSYS software.

Equipments required:

1. A personal computer loaded with any one of the following application software

ANSYS

2. A4 Printer.

Procedure:

1. Execute the application software i.e. ANSYS (mechanical APDL)

2. Set preference of study

3. Model the 2D elements to be studied, as per the requirements.

4. Set the material type.

5. Assign the material properties.


6. Create the meshing of the modelled part.

7. Assign the boundary conditions, by applying degree of freedom and external loads at required positions


8. Solve problem with given boundary conditions

9. Open the result of deformation, stress and strain plot

10. Generate the report.

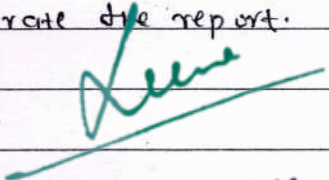
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Teacher's Signature:

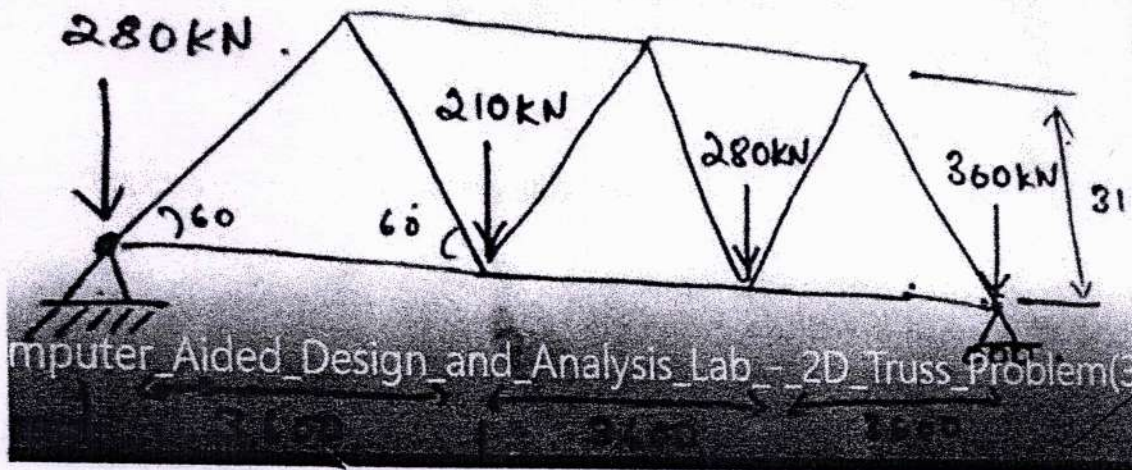

Procedure	S
Conduct	S
Result	S
va	9 1/2
ard	S

29 1/2

Leena
Dr. LEENA A V
 PRINCIPAL
 SREE NARAYANA GURU COLLEGE OF
 ENGINEERING & TECHNOLOGY
 PAYYANUR, KANNUR

[Signature]
 HOD ME

EXPERIMENT NO. 9

STRUCTURAL ANALYSIS ON 3D PART

Aim: •

5 To familiarize the structural analysis on SOLIDWORKS Software

Equipment required

1. A personal Computer loaded with any one of the following application Software

10 SOLIDWORKS

2. A4 Printer

Procedure:

1. Execute the application software i.e. SOLIDWORKS and add in Solidworks
15 Simulation

2. create new study (Static)

3. Insert the 3D model

4. Set the material type

5. Assign the material properties


20 6. Assign the boundary conditions, by applying degree of freedom and external loads at required position

7. create the meshing of the modelled part

8. Solve problem with given boundary conditions

9. open the result of deformation, stress and strain plot

25 10. Generate the report.

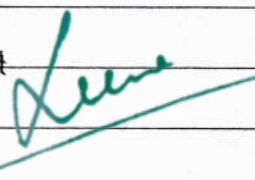
Dr. LEENA A V
PRINCIPAL
BREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

EXPERIMENT NO. 10

MOTION STUDY OF SCREW AND NUT

Aim: To familiarize the motion study on ^{SOLIDWORKS} ~~SolidWorks~~ soft. Software

Equipment required;

1. ^A Personal computer loaded with any one of the following Application Software

SOLIDWORKS

2. A4 Printer.

Procedure:

1. Execute the application software ie SOLIDWORKS and add in Solidwork sim-
ulations.

2. Create new study (Static)

3. Insert the 3D model

4. Set the material type


5. Assign the material properties

6. Assign the boundary conditions, by applying degree of freedom

7. Play the motion study.

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Teacher's Signature: _____

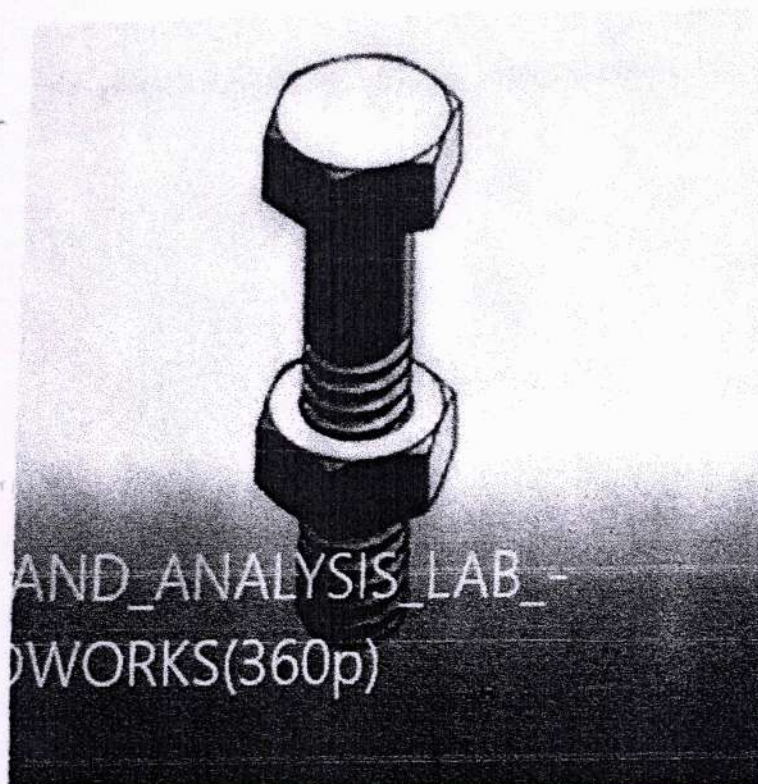

AND_ANALYSIS_LAB_-
WORKS(360p)

Procedure	S
Conduction	S
Result	S
Viva	9
Record	S

Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

29

[Signature]
HOD ME

EXPERIMENT No. 11

THERMAL PROBLEM ON MIXED BOUNDARY ANALYSIS

Aim : To familiarize the structural analysis on ANSYS software

Equipments required

1. A personal Computer loaded with any one of the following application Software.

SOLIDWORKS, ANSYS

2. A4 Printer.

PROCEDURE:

1. Execute the application Software i.e ANSYS (Mechanical APDL)

2. Set the Preference of Study

3. Model the 2D elements to be studied, as per the requirements

4. Set the material type.

5. Assign the material properties


6. Create the meshing of the modelled part.

7. Assign the boundary conditions.

8. Solve problem with given boundary conditions


9. Open the result of deformation, Stress and Strain plot.

10. Generate the report.

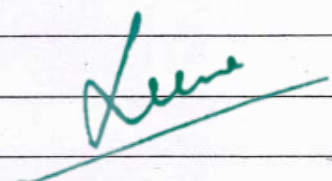
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYYANUR, KANNUR

Teacher's Signature:

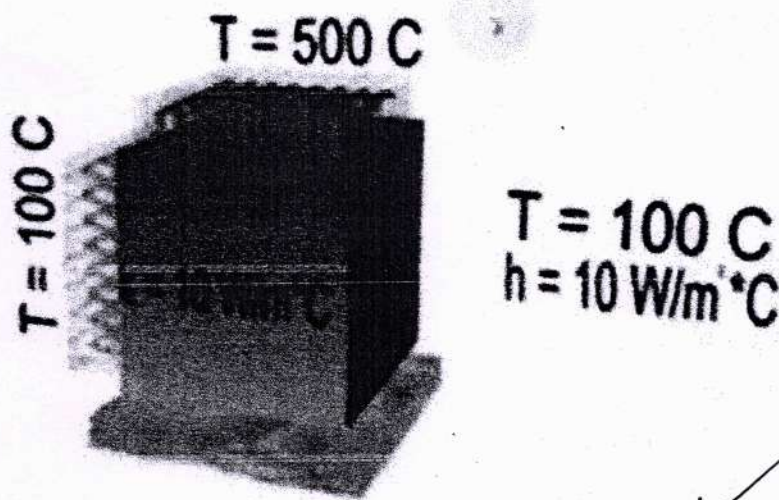Example is contained as shown in the following figure (Note that the section



Procedure	S
Conduction	S
Result	S
Viva	8 1/2
Record	S

28 1/2

HOD ME

Leena

Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

EXPERIMENT No : 12

FLUID FLOW ANALYSIS

Aim:

- 5 To familiarize the fluid flow analysis of Solidworks software


Equipment required:

1. A personal computer loaded with any one of the following application software
- 10 SOLIDWORKS
- 2- A4 printer


Procedure:

1. Execute the application software i.e. Solidworks and add in CFD
- 15 Simulation.
- 2- create new study (CFD)
- 3- Insert the 3D model
4. Set the material type
5. Assign the material properties
- 20 6. assign the boundary conditions, by applying degree of freedom
- 7- Run the CFD
- 8- View the various results
- 9- Generate the report.

25

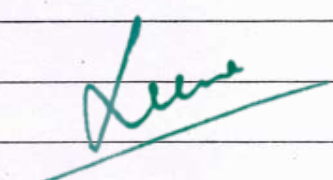
Dr. LEENA A V
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY
PAYANUR, KANNUR

Teacher's Signature: _____

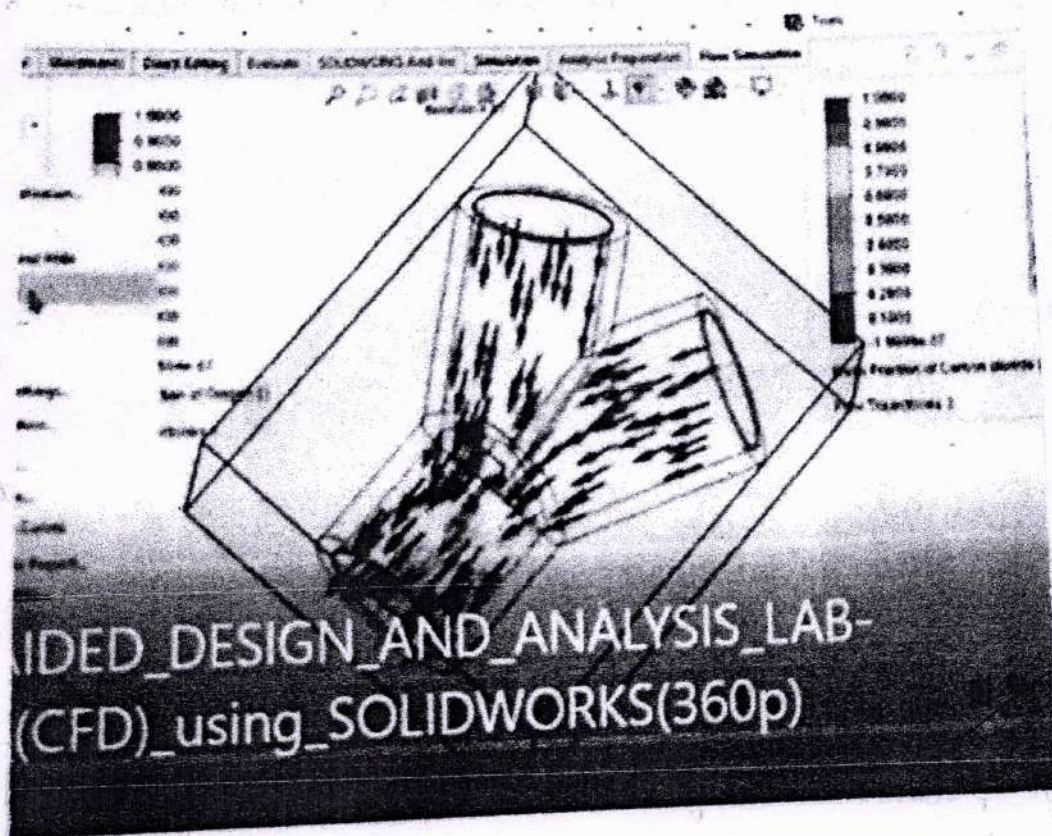

VIDED DESIGN AND ANALYSIS LAB-
(CFD)_using SOLIDWORKS(360p)

Procedure	5
Conduction	5
Result	5
iva	96
cord	5

296

HOD ME

Leena
Dr. LEENA A. V.
PRINCIPAL
SREE NARAYANA GURU COLLEGE OF
ENGINEERING & TECHNOLOGY, PAPPANUR
KANNUR